

Electronics Today



July 1984

\$2.95
MM70924



Canada's Magazine for Electronics & Computing Enthusiasts

Principles of Metal Detection

Treasure from the park?

Sinclair's QL 
UK computer success

Motor Controller
Rev it up

Stylus Timer 
Counting the hours



**Computer
Review**
Sony SMC-70



EXCELTRONIX (416) 921-8941 1-800-268-3798

Bulletin Bd. (416) 624-5574 Telex 065-24218

319 College St., (416) 293-1796 Toronto, Ont. M5T 1S2

Catalogue shipping rates are incorrect. Please call us for correct charges. Prices in catalogue are fluctuating. Use as guideline.

TWO NEW EXCELTRONIX LOCATIONS!

NOW OPEN

Ottawa	Hamilton
217 Bank Street	72 James St. North
(613) 230-9000	

Store hours 9:30 to 6:00 Monday-Saturday; to 9:00 p.m. Friday.

PRINTERS

Star Gemini 10X	\$359
Gemini 15X	\$599
Delta 10 (160 cps)	\$739
Epson MX100	\$995
Epson RX80 (Replaces MX80)	\$495
Epson FX80 (New)	\$798
Epson FX100 (New)	\$1069
TTX (Daisy Wheel)	\$649
Microtek	\$139

MONITORS

Zenith ZVM-122 Amber	\$139
Amdek Green	\$129
Zenith ZVM-123 Green	\$129
Amdek Colour 1	\$445
Roll and DG	\$419

New Macintosh with printer \$4,295

Apple 2C with monitor \$1,885

New Macintosh, based on 68000 with 3" Disk Drive (smaller version of Lisa™). Diskette Software now available \$3,195

APPLE CARDS

16K card - Multiflex	\$58.00
128K card	\$210.00
Proto Board	\$15.00
80-Column Card	\$84.00
Z80 Card	\$59.00
EPROM Programmer	from \$69.00
(for 2716, 2732, 2732A, 2764, with software) Parallel Printer Card with cable	\$69.00
Wizard Parallel Card	\$95.00
Serial Card	\$99.00

MODEMS

EPM 310 Smart Modem	\$99
(300 Baud, IBM Comp)	\$359
Apple a la Modem (300 Baud)	\$215
Micromodem (Apple Comp)	\$475
Signalman (300 & 1200 Baud)	\$495
Smart Modem 1200 Baud	\$899

FAMOUS MULTIFLEX Z80 STARTER KIT: SPECIAL \$299.00

Ideal Learning Tool, with EPROM programmer
see page 16 of catalogue

UNIVERSITY OF TORONTO/MULTIFLEX 6809 Board, great for learning about 6809 and computing in general with A & T \$499.00
Economy Terminal A&T \$369.00
Package Deal A&T \$849.00

Memory Chips

4164-150nS (1x64K single + 5V)	
Motorola	\$9.95
T.I.	\$7.95
4116-200ns (1x16k)	\$1.74
4116-150ns (1x16k)	\$1.99
2114L-200 ns (1kx4 static)	\$2.49
6116-150 ns (2kx8 static RAM)	\$8.94
(Pin compatible with 2716 uses negligible amount of power)	
2016-150 ns (2kx8 static)	\$8.74
2102L-200 ns (1kx1 static)	\$1.94
5101-CMOS RAM	\$3.84
2708-(1kx8 EPROM)	\$6.74
2716-(2kx8 EPROM single + 5V)	\$5.50
2732-(4kx8 EPROM single + 5V)	\$8.95
2532-(4kx8 EPROM single 5V)	\$8.74
2764-(8kx8 EPROM single 5V)	\$12.95
HUGE STOCK OF LS	

Diskettes

5 1/4" Diskettes. Boxes of 10	
Maxell MD1	\$34.00
Maxell MD2	\$52.95
Verbatim	\$34.00
CDC	\$26.95
3M	\$32.95
Accutrak	\$26.95
2 Ectype Diskettes in a plastic binder sheet	\$5.89
Flip N File 50	\$44.95
Diskminder (75)	\$33.95
Dysan	\$39.00
BASF	\$34.00
BASF with case	\$35.00

Special!

Featuring the Multiflex Apple™ Compatible Drive

only \$249



Package Deals:
A1 Drive & Controller \$310
B2 Drives & Controller \$549
Controller only \$69
with software \$119
VISTA DRIVE \$299
QUENTIN DRIVE \$299

1 year warranty

Controller \$89
With Apple™ Software \$119

NEW
Smith-Corona Printer
L1000
Bi-directional daisy-wheel
Serial/Parallel port
\$599

Joysticks

Economodel	\$19.95	TG Joystick	
Wico Red Ball	\$42.95	Deluxe Model	\$75.00
Self-Centering with two adjustable controls.		TG Paddles Deluxe Model	\$64.95
Super offer	\$64.00	Hayes Mach III	\$58.95
Kraft Joystick (Apple, PC)	\$64.95	Model Deluxe	
Kraft Paddles	\$48.95	Table Top	\$59.00
		Hayes Mach II	\$48.95

Siemens 8" disk drives	
S.S.D.D.	\$79.00
Buy 2 for	\$59.00 each
D.S.D.D.	\$89.00 single
Buy 2 for	\$69.00 each

Super Computer Case


Ideal for 8088 or 6502 boards
Unmatchable quality, all-Canadian made



\$87.00!

IBM Compatible Keyboard \$189.00

Maxiswitch or cherry

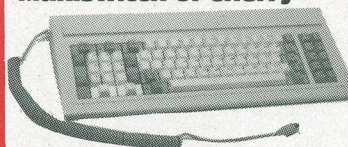

Superb Power Supply

Uncased Dual 12V:
(one at 2.8A, one at 2A).
—12V at 0.5A, +5V at 5A plus

\$69.00!

Cased model, with fan, cord and switch

\$139.00!

These supplies are ideal for IBM compatibles, they fit beautifully into IBM compatible cases.

IBM is registered trade mark of IBM Canada Limited.

Check our catalogue for far, far more than you see here. If you didn't get it in your May copy of ETI or CN!, send for your free copy.

CHARGE

Remember that at Exceltronix all prices are negotiable for quantity purchases. If you cannot afford large quantities on your own how about starting a Co-op.

PRICE POLICY

MAIL ORDERS
Send a certified cheque or money order (do not send cash). Minimum order is \$10 plus \$3 minimum for shipping. Ontario residents must add 7% provincial sales tax. Visa, Mastercard and American Express accepted: send card No., signature, expiry date and name of bank.



Head Office: 319 COLLEGE STREET, TORONTO, ONTARIO, CANADA. M5T 1S2 (416) 921-8941

Circle No. 27 on Reader Service Card.

SURPLUSTRONICS

we will not be undersold



Canadian Made

AS
Reviewed
in ETI
May 1983:
Send for a
FREE COPY



960-1350 OUR FAMOUS 6502 BOARD

NOW NEW & IMPROVED VIDEO SECTION

This 6502 board is a vast improvement on others available:

- 64K RAM (8-4164 chips)
- 80 x 24 video included on board
- Floppy Disk Controller included
- FIVE additional slots
- Z80 blank PCB included
- Powerful power supply (5V 5A, +12V 2 up to 3A peak, -5V 0.5A, -12V 0.5A)
- Hydro-approved whereas many others are not!
- Superb quality plastic case
- Excellent keyboard including numeric keypad
- EPROMS (blank) included
- Available preassembled by special order only.
- Ideal for educational applications.

\$669

Our prices are low due to our mass production assembly, which makes it hard for others to compete.

NOW you receive a **FREE** Z80 PC BOARD **AND** **FREE** 128K RAM DISK PC BOARD when you order the complete package (BLANK)

Our boards are professionally made, flow soldering & cleaned & use only high quality prime parts.

You can now get an IBM compatible without wasting your investment in a 6502 system. Talk to us about our generous trade-in scheme.


BEST PRICE

8088 System \$1,989

Best Prices in Canada

Complete System with 64K, expandable to 256K. Comes with Colour Graphics, Floppy Controller and one DS, DD 5 1/4" Disk Drive, Keyboard, Case and Extra Heavy-Duty, Fan Cooled Power Supply.

System comes with 5 peripheral slots. Optional 8087 arithmetic processor available. Floppy controller can handle up to 4 drives and as an option can a serial port and real-time clock. Completely built and tested and sold with a blank EPROM. Compatible with You-Know-Who. Systems are now in stock but due to extraordinary demand at time of going to press, order now to prevent delays. Please Note: We do not sell any proprietary software.

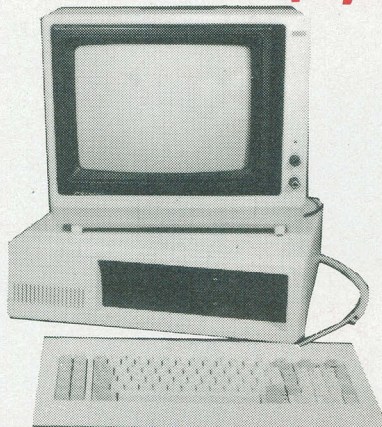

Peripheral Boards for your IBM PC

Prototyping Card \$33.00
Floppy Controller Card \$289.00
Colour Video Card \$299.00
Parallel & Game Port Card \$149.00
EPROM Programmer. Starts at \$149.00
Expansion Card
with many options \$Call

Attractive Case (as shown above) \$85.00
Keyboard (as shown above) . . . \$187.00

Super Power Supply, made to fit above case, with cooling fan \$135.00

8088 Board, with 64K on board (provision for 256K), as described in our 8088 System.

Assembled and tested \$499.00

Form a Buyers Group. Buy in groups of 5 or more and you can save hundreds of dollars each.

Huge variety of Surplus stock at low, low prices. New shipments arriving. No reasonable offers refused. Prices subject to change without notice!

Surplustronics, 310 College Street, Toronto, Ontario, M5T 1S3

Monitors

ZVM-122 Amber \$139.00
ZVM-123 Green \$129.00
Roland Colour 1 \$395.00
Amdek Green \$129.00

EPS Keyboard \$399.00

Apple Compatible. IBM Module available. Distributor for Ogivar

Apple Peripherals Assembled and Tested

Serial Card \$ 85.00
Z80 Card \$ 58.00
80 x 24 \$ 84.00
16K RAM \$ 58.00
Prototyping Board \$ 14.50
Parallel Printer Card \$ 59.00
... with cable & connector . . . \$ 69.00
128K Board (No IC's) \$ 49.00
...with IC's & 64K RAM \$129.00
...with IC's & 128K RAM \$210.00
Crazy Card \$ 58.00
Eprom Programmer \$ 68.00

Disk Drives

Apple Compatible \$249.00
Controller \$ 59.00
...w/software \$119.00

One year warranty

All prices subject to change

Printers

A. Gemini 10x \$359.00
B. Special Multiflex parallel card with cable. Shop and compare . . . \$ 69.00
Package price of A and B . . . \$415.00
Gemini 15x \$598.00

**5" Green Screen
Monitors. \$59**

**Telex No.
065-24218**

Mail Orders add \$5.00 minimum for shipping & handling. Ontario residents add 7% P.S.T. Visa, Mastercard and American Express cards accepted: send card number, expiry data, name of bank and signature. Send certified cheque or money order, do not send cash.

Circle No. 29 on Reader Service Card
More lines to serve you better
(416) 960-1350

Intelligent Robots You Build Yourself

...a new world of educational fun

**Electronic
Control**


MOVIT

AVOIDER

MV-912 (blue)
(Sensor/control PC board ready assembled)

An intelligent robot which knows how to avoid hitting walls. This robot emits an infra-red beam which detects an obstacle in front.

\$69.95

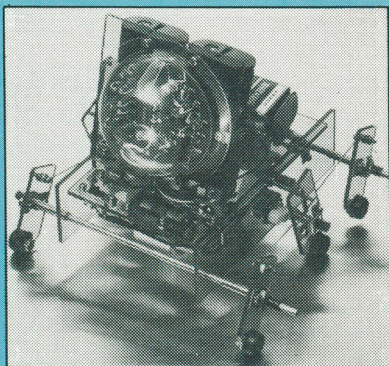

- * Movement : 3 legs on each side by crank motion.
- * Control : Infra-red sensor including infra-red diode/photo diode/IC
- * Power source (Not included) : Battery type 1.5V "AA" x4 9V x1

**Electronic
Control**


MOVIT

MONKEY

MV-919 (yellow)
(Sensor/control PC board ready assembled)

Order your MONKEY to "Move" with a loud voice or clap to your hands and the robot starts romping along a rope and stops after a while by itself.

\$39.95

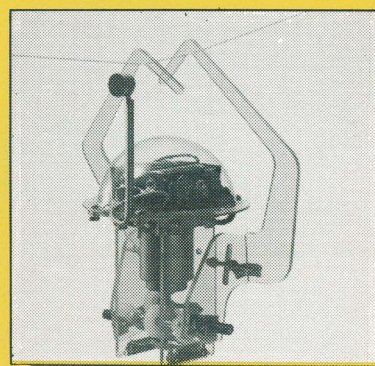

- * Movement : Two alternatively moving gripper arms driven by crank motion.
- * Control : Sound sensor, including condensor microphone/transistor.
- * Power source (Not included) : Battery type 1.5V "N" x2

**Electronic
Control**


MOVIT

LINE TRACER II

MV-913 (yellow)
(Sensor/control PC board ready assembled)

Guided by an infra-red light sensor this robot will automatically follow any black line drawn on white paper.

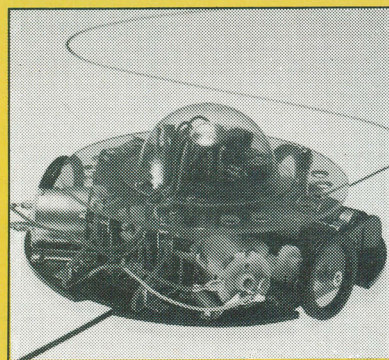- * Movement : 3 wheels driven by 2 DC motors.
- * Control : Infra-red sensor including infra-red diode/photo diode/IC
- * Power source (Not included) : Battery type 1.5V "AA" x2 9V x1



- * How to play : Draw a black line on white paper board. Line width should be 10 mm minimum wide. Narrowest turning radius must be at least 15 cm.

\$64.95

**Electronic
Control**


MOVIT

PIPER-MOUSE

MV-915 (blue)
(Sensor/control PC board ready assembled)

This is a Supersonic-Robot controlled by a Supersonic sound sensor and an electronic circuit (1 channel). Use the whistle attached to this kit and Piper Mouse will follow your commands immediately turning to the left, stop, turning to the right, stop, advance and stop.

\$69.95

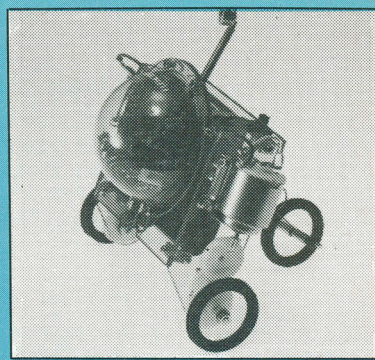

- * Movement : 3 wheels driven by 2 DC motors.
- * Control : Supersonic sound sensor including condensor microphone and printed circuit board.
- * Power source (Not included) : Battery type 1.5V "AA" x2 9V x1

**Electronic
Control**


MOVIT

Sound Skipper

MV-917 (yellow)
(Sensor/control PC board ready assembled)

Order the SOUND SKIPPER to "Walk" with a loud voice or clap your hands, this robot starts walking and stops after a while by itself.

\$39.95

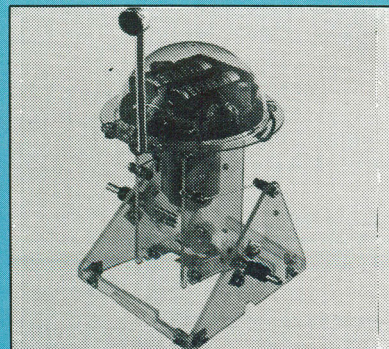

- * Movement : Two alternatively moving legs driven by crank motion.
- * Control : Sound sensor including condensor microphone/transistor.
- * Power source (Not included) : Battery type 1.5V "N" x2

NOW AVAILABLE FROM:

A.J.K. HOBBY ELECTRONICS
ASSEF TV & STEREO
FOCUS SCIENTIFIC
GLADSTONE ELECTRONICS

MASTERMIND EDUCATIONAL TECH.
MICRO COMPUTER CLINIC
ORION ELECTRONICS
SCIENCE TECH
THE SOFTWARE SHOP

Joyceville, Ont. (613) 548-8336
Windsor, Ont. (519) 948-4171
Ottawa, Ont. (613) 236-7767
Toronto, Ont. (416) 787-1448
(Toll free) (800) 268-3640
Toronto, Ont. (416) 487-7177
Nanaimo, B.C. (604) 753-0983
Kitchener, Ont. (519) 576-9902
Montreal, P.Q. (514) 844-6443
Willowdale, Ont. (416) 223-9611

EDG Electronic Distributors Inc.
3950 Chesswood Dr., Downsview, Ont. M3J 2W6
Dealers Inquiries Invited **(416) 636-9404**

Electronics Today




Audit Bureau
of Circulation

July 1984

INTERNATIONAL

Vol. 8. No. 7 ISSN 07038984

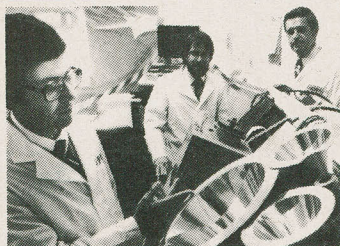

60

Features

11

Principles Of Metal Location

You'll be amazed at all the stuff buried beneath your feet.

24

A Look At The Sinclair QL

A British computer success, soon to be available here.

26

Coping With Components

Part Two. How to tell a component from a door knocker.

32

Computer Review

The Sony SMC-70 is the graphics fan's delight.

39

Machine Language, Part Two

Conversing directly with your CPU.

41


Computing Today

John Rudzinski provides some computer utilities via 6502 assembler.

45

Circuit Ideas

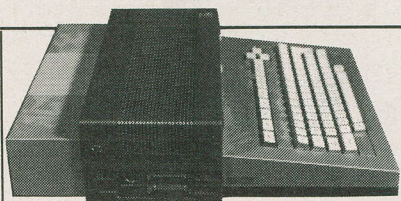Replacing Tech Tips, our new feature looks at camera control.



32

55

Designer's Notebook

Exar Super Timer.

60

VLFs And The Magnetosphere

If you need a bigger VLF, put it in the magnetosphere, says Roger Allan.

63

Armstrong

A pioneer in the development of AM and FM receivers.

Projects

18

Motor Controller

Run fans and vacuum cleaners at pointlessly slow speeds.

47

Stylus Timer

Measures the hours until it self-destructs along with your records.

Columns, News and Information

For Your Information	7
Order Form	53
Binders	54
Book of the Month	54
Subscriptions	54
ETI Bookshelf	50
Next Month	53
Product Mart	58

Our Cover

Visions of treasure dance in Ed's head; see page 11. Photo by Bill Markwick. The Sony SMC-70 is reviewed on page 32; photo courtesy of Sony.

Electronics Today is Published by:

Moorshead Publications

Editorial and Advertising Offices
Suite 601, 25 Overlea Boulevard,
Toronto, Ontario, M4H 1B1
Telephone (416) 423-3262

Editor:

Editorial Assistant:

Director of Production:

Creative Manager:

Production:

William Markwick

Edward Zapletal

Erik Blomkwist

Ann Rodrigues

Douglas Goddard

Neville Williams

Naznin Sunderji

Lisa Salvatori

Omar Vogt

Rick May

Circulation Manager:

Advertising:

Advertising (Que.): John McGowan & Associates
(514) 735-5191

Publisher: H.W. Moorshead; Executive Vice-

President: V.K. Marskell; General Manager:

S. Harrison; Controller: B. Shankman; Accounts:

P. Dunphy; Reader Services: C. Wyatt, S.

Halladay, H. Brooks, K. Adams; Advertising

Services: C. Zyvitski, Dealer Services: A. Nagels.

Newsstand Distribution:

Master Media, Oakville, Ontario

Subscriptions

\$19.95 (one year), \$34.95 (two years). For US add \$3.00 per year, other countries add \$5.00 per year. Please specify if subscription is new or a renewal.

Postal Information

Second Class Mail Registration No. 3955. Mailing address for subscription orders, undeliverable copies and change of address notice is:

Electronics Today International, Suite 601, 25 Overlea Blvd., Toronto, Ontario, M4H 1B1.

Advertisers' Index

Active Components Sales Corp.	68
Allan Crawford and Associates	42, 43
Audiovision	65
BCS Electronics Limited	31, 67, 70
Biplex Systems Inc.	61
Brunelle Instruments Inc.	64
Circuitronics	34
Compu-Order	64
Computer Mail Order	6
Computer Parts Galore Inc.	8, 9
Daetron	31
Electronic Control Systems	64, 66
Electronic Distributors Inc.	4
Electronic Packaging Systems Ltd.	61
Exceltronix	2, 72
Gentec Computers Inc.	34
J.A.C. Electronics	30
Kaientai Electronics Merchants Ltd.	31
Locust Computer Systems Corporation ...	61
Mark Gee Enterprises	61
McGraw-Hill	29
Metermaster	44
Orion Electronics Supplies Inc.	71
Pacific Rim	69
Surplustronics	3
Tradeport Electronics	64, 66

= COMPUTER MAIL ORDER =

= CANADA =

ONTARIO/QUEBEC
1-800-268-3974

TORONTO
828-0866

OTHER PROVINCES
1-800-268-4559

We Carry a Wide Selection of Software From:

Artworx, Broderbund, Commercial Data, Creative Software, Epyx, Atarisoft, Hes, Sirus, Microspec, Synapse, Thorn, Spinnaker, Timeworks + Many More. Call us for prices!

(All equipment under full warranty in Canada.)

Price subject to change without notice.

(All orders Shipped within 48 hrs, upon payment.)

COMPUTERS

APPLE	CALL
COLUMBIA	CALL
COMPAQ	CALL
EAGLE	CALL
FRANKLIN	CALL
HEWLETT PACKARD	CALL
IBM	CALL
SANYO	CALL

DISK DRIVES

CDC (for IBM)	\$339.00
INDUS	
GT ATARI Drive	549.00
MSD	
MSD-1 C64 Drive	519.00
MSD-2 C64 Drive	855.00
PERCOM	CALL
RANA	
1000 (Atari)	479.00
Elite 1	389.00
Elite 2	579.00
Elite 3	799.00
SANTA CLARA	CALL
TALLGRASS	CALL
TANDON	
TM-100-2 DS/DD	339.00
TM-50-2 DS/DD	349.00
TRAK	
ATD-2	565.00

MODEMS

ANCHOR	
Mark I (RS232)	129.00
Mark II (Atari)	129.00
Mark III (TI-99)	179.00
Mark IV (CBM/PET)	199.00
Mark V (Osborne)	159.00
Mark VI (IBM)	279.00
Mark VII (AA/AD)	193.00
Mark XII (1200 Bd.)	489.00

HAYES

Smartmodem 300	356.00
Smartmodem 1200	799.00
Smartmodem 1200B	749.00
Micromodem II	432.00
Micromodem II +	489.00
Micromodem II e	439.00

NOVATION

J-Cat	163.00
Smartcat 103	289.00
Smartcat 103/212	649.00
Autocat	356.00
212 Apple Cat	929.00
PC-Cat	549.00

MONITORS

AMDEK	
Video 300	\$229.00
Video 300 A	239.00
Video 310A IBM	249.00
Colour 1 +	429.00
Others	CALL
BMC	
12" Green	125.00
12" Amber	135.00
GORILLA	
12" Green	139.00
12" Amber	149.00
NEC	CALL
PANASONIC	CALL
PRINCETON GRAPHICS	
HX-12	819.00
QUADRAM	
Quadcolor RGB	809.00
SAKATA	CALL
TAXAN	CALL
USI	CALL
ZENITH	
Amber	159.00
Green	149.00
Colour	699.00

CARDS

AST RESEARCH	CALL
QUADRAM	CALL
HERCULES	
Graphic card	598.00
PLANTRONICS	
Colorplus	699.00

ACCESSORIES

KEYTRONIC	
KEYBOARDS	CALL
KOALA PAD	
All Computers	CALL

INTERFACES

Batteries Included	
Bus Card	CALL
80 Col. Card	CALL
CARDCO	
Par Printer Inter	75.00
Int/Graphics	119.00
TYMAC	
C64 to EPSON OKI	148.00
MPC	
Apple Dumping GX.	CALL
PKASO	
Universal Card	225.00

PRINTERS

BMC	
401 Letter Quality	\$923.00
BX-80 Dot Matrix	399.00
C. ITOH	
Gorilla Banana	299.00
Prowriter 8510P	550.00
Prowriter 1550P	899.00
F10-40	1529.00
F10-55	1999.00
DAISYWRITER	
2000	1499.00
COMWRITER	
CW2. LQ 12CPS	749.00
EPSON	
RX80	449.00
RX80FT	525.00
FX80	749.00
FX100	1049.00
JUKI	
6100	769.00
OKIDATA	
82	475.00
83	899.00
84 Par	1499.00
84 Ser	1650.00
92	695.00
93	1159.00
MANNESMANN TALLY	
Spirit 80	469.00
160L	895.00
180L	1229.00
SMITH CORONA	
L1000	589.00
STAR	
Gemini 10X	CALL
Gemini 15X	CALL
BROTHER	
HR 15	CALL
TTX	CALL
DISKETTES	
BASF	
BA1D SS/DD W/Case	28.99
BA2D DS/DD W/Case	35.99
ELEPHANT	
EL1 SS/DD	27.99
EL2 SS/DD	29.99
EL3 DS/DD	39.99
MAXELL	
MXD1 SS/DD	37.99
MXD2 DS/DD	54.99
NASHUA	
ND1D SS/DD W/Case	26.99
ND2D DS/DD W/Case	38.99
VERBATIM	
VE1 SS/DD	31.99
VE2 DS/DD	43.99
VE1C SS/DD W/Case	34.99
VE2C DS/DD W/Case	46.99

Dealer Enquiries Invited

Write or telephone for our FREE catalog

To order: Send money order, certified cheque, personal cheques must clear our bank, VISA or MASTERCARD. (Include card # and expiry date & signature) Add 5% for shipping and handling. Minimum \$5.00 per order.

Ontario residents add 7% P.S.T.

Computer Mail Order Canada 2505 Dunwin Drive, Unit 3 • Mississauga, Ontario L5L 1T1



for your information

Copyright

All material is subject to worldwide copyright protection. All PCB patterns are copyright and no company can sell boards to our design without our permission.

Liability

While every effort has been made to ensure that all constructional projects referred to in this magazine will operate as indicated efficiently and properly and that all necessary components are available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate efficiently or at all whether due to any fault in the design or otherwise and no responsibility is accepted for the failure to obtain component parts in respect of any such project. Further no responsibility is accepted in respect of any injury or damage caused by any fault in design of any such project as aforesaid.

Editorial Queries

Written queries can only be answered when accompanied by a self-addressed, stamped envelope. These must relate to recent articles and not involve the staff in any research. Mark such letter ETI Query. *We cannot answer telephone queries.*

Binders

Binders made especially for ETI are available for \$9.25 including postage and handling. Ontario residents please add provincial sales tax.

Back Issues and Photocopies

Previous issues of ETI Canada are available direct from our office for \$4.00 each; please specify by month, not by feature you require. See order card for issue available.

We can supply photocopies of any article published in ETI Canada; the charge is \$2.00 per article, regardless of length. Please specify both issue and article.

Component Notation and Units

We normally specify components using an international standard. Many readers will be unfamiliar with this but it's simple, less likely to lead to error and will be widely used everywhere sooner or later. ETI has opted for sooner!

Firstly decimal points are dropped and substituted with the multiplier: thus 4.7uF is written 4u7. Capacitors also use the multiplier nano (one nanofarad is 1000pF). Thus 0.1 uF is 100nF, 5600pF is 5n6. Other examples are 5.6pF = 5p6 and 0.5pF = 0p5.

Resistors are treated similarly: 1.8Mohms is 1M8, 56kohms is the same, 4.7kohms is 4k7, 100ohms is 100R and 5.6ohms is 5R6.

PCB Suppliers

ETI magazine does NOT supply PCBs or kits but we do issue manufacturing permits for companies to manufacture boards and kits to our designs. Contact the following companies when ordering boards.

Please note we do not keep track of what is available from who so please don't contact us for information on PCBs and kits. Similarly do not ask PCB suppliers for help with projects.

K.S.K. Associates, P.O. Box 266, Milton, Ont. L9T 4N9.

B—C—D Electronics, P.O. Box 6326, Stn. F, Hamilton, Ont. L9C 6L9.

Wentworth Electronics, R.R. No. 1 Waterdown, Ont. L0R 2H0.

Danocinths Inc., P.O. Box 261, Westland MI 48185, USA.

Arkon Electronics Ltd., 409 Queen Street W., Toronto, Ont., M5V 2A5.

Beyer & Martin Electronic Ltd., 2 Jodi Ave., Unit C, Downsview, Ontario M3N 1H1.

Spectrum Electronics, 14 Knightswood Crescent, Brantford, Ontario N3R 7E6.



Franklin CX Series

Franklin Computer of New Jersey has unveiled their new four-model CX line of computers. The biggest feature is compatibility with various operating systems — the top-of-the-line 2M, for instance, can run Apple DOS, CP/M, and MSDOS; it also can read Kaypro and Osborne formats. Other features are one or two DSDD drives, business software by Artsci, a minimum of 64K RAM, and a seven inch monitor. Available in Canada shortly, the U.S. models start at \$1,395.

Circle No.60 on Reader Service Card

Cesco Electronics, 4050 Jean Talon W., Montreal, Que. H4P 1W1 (514) 735-5511, has a new catalogue of components and accessories; it's free by phoning, writing, or visiting. There are branches in Quebec City, Ottawa, and Toronto.

IBM has announced the success of an experimental one-megabit memory chip. It uses IBM's silicon-aluminum-metal oxide process (SAMOS), and operates from a single 5 volt supply. Access time is 150 nanoseconds. No mention was made of availability or price, but the prototypes were made on the same production line as their 64K-bit chips, so it shouldn't take too long to hear more about them.

Speaking of IBM, they have filed a lawsuit against Spirales Computers of Montreal; they're seeking an injunction to prevent the importing and marketing of a Taiwanese computer which IBM says is infringing their copyright. Cloners beware.

Electronic Packaging Systems announced yet another dealer for their line of BICC Vero hardware: Montcalm Electroniques Inc., 97 Boul. des Laurentides, Ville de Laval, Quebec H7G 2T2.

Circle No.59 on Reader Service Card



Spud

Shamrock Computer Inc. has announced the introduction of the Shamrock professional Utility Drive (SPUD).

Shamrock Computer Inc. is a Canadian company which has been manufacturing disk drives for Apple and Apple compatible computers for over a year. The Shamrock SPUD 3.5" Apple II compatible disk drive, offering 328K storage on 80 tracks, was introduced at both the Ottawa

High Technology and Toronto Computer Fair shows. The SPUD 3.5" drive plugs into the existing Apple controller card and is supplied with a menu driven 5-1/4" utility diskette that allows users to configure their Apple II system and to copy their existing 5-1/4" software onto the more convenient 3.5" plastic-encased diskettes. Contact them at 89 Telson Rd., Markham, Ont. L3R 1E4 (416) 474-0113.

Circle No.58 on Reader Service Card

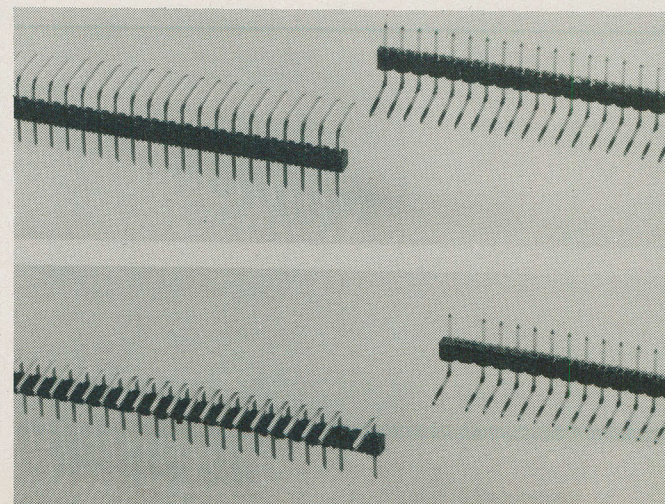
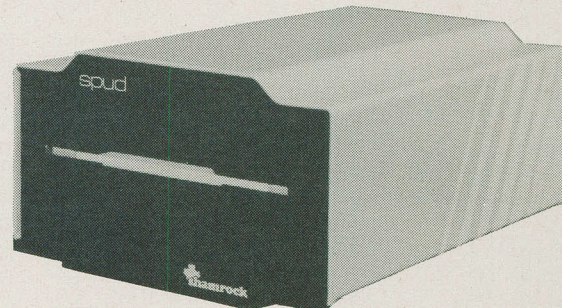


New Header Pins



Apronics Corporation announces fast delivery on their full line of 295 Series Headers. 295 Headers are available in both straight and right-angle configurations. They are directly interchangeable replacements for other industry-standard .295" Headers. 295 Series Headers are available in full or polarized rows. Standard polarized headers have second circuit voided (post removed). Headers feature standard .025" square posts, .100" spacing between posts, and are available with up to 30 contact posts per row. At Apronics dealers, or contact Lenbrook Electronics, 111 Esna Park Dr., Unit 1, Markham, Ont. L3R 1H2 (416) 477-7722.

Circle No.57 on Reader Service Card

COMPUTER

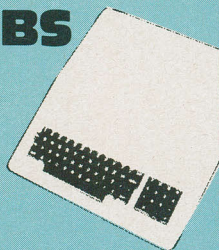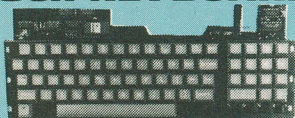PARTS GALORE INC.316 College St.
Toronto, Ontario M5T 1S3**SOLID ABS
CASE
NUMERIC
\$59.95****OUR 6502 BOARD**
Now only \$29.95 still with
all the versatility of the
original and a full 8 slots.**ASCII KEYBOARDS**Now, we have a new keyboard, micro
controlled with 3 levels of pre-coded
functions for Basic, CPM etc. and at the
same old price as beforeFunction Keyboard, Numeric . . . \$99.00
Function Keyboard, Standard . . . \$89.00**Toll Free Orders Only
1-800-387-1385**Order Checking (416)925-8291
Technical Data (416)925-1105**MODEM**At last, an affordable Modem, we
have cloned a board similar to the
SSM Modem that features:

- APPLE II & APPLE IIe COMPATIBLE
- 40/80 COLUMN SUPPORTED
- FULL/HALF DUPLEX
- AUTO ANSWER/AUTO DIAL
- TOUCH TONE OR PULSE DIALING
- AUDIO MONITOR CHANNEL
- IN PLACE FIRMWARE
- HAYES MICRO MODEM II COMPATIBLE
- RUNS ASCII EXPRESS AND MOST OTHER PROGRAMS
- DIRECT LINE CONNECTION

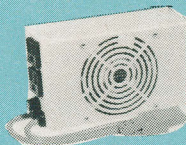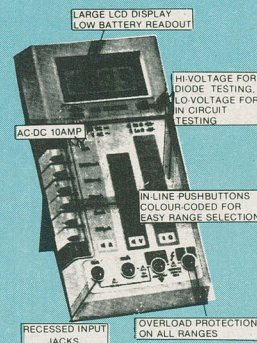We have tried it out and it is very
good and very reasonably priced
for it's quality \$229.00
Bare PCB only \$ 24.95**POWER
SUPPLY**Our Famous "BLACK BEAUTY" power supply, now
reduced in price but not in quality. Our ratings are
5V-5A; 12V-2.5A; 5A-1/2A; 12V-1/2A for real \$79.95**GREAT
DEAL****THE GREAT DEAL
CARRIES ON FOREVER AND GETS BETTER**Our proven 6502 motherboard plus a numeric case plus
a black beauty powersupply plus a numeric keyboard
plus any 4 bare pcb for \$225.00**SYSTEM
SAVIOR**2 grounded 3 wire switched sockets, pilot light, surge
protector and on-off switch to turn off your system and
two plugged in items \$45.00**DIGITAL
MULTI-METER
AMAZINE QUALITY AT LOW COST
\$69.96****EXTRA FEATURE**

- Diode test circuit • Lo voltage ohms, 0.5v • Lo battery indicator • Auto-Zero • Auto polarity • Overload protection, all ranges • ABS case (will not crack) • One hand push buttons.

HARD TO GET PARTS

14.318 MHZ XTAL	\$ 2.95
17.43 MHZ XTAL	\$ 4.95
1.8432 MHZ XTAL	\$ 4.95
MPSA13 TRANSISTOR	\$ 0.75
2N3904	\$ 0.35
2N3906	\$ 0.45
2N4258	\$ 0.75
MPSU51	\$ 1.00
1K, 9 PIN SIP	\$ 0.75
1K, 8 PIN SIP	\$ 0.75
10K, 10 PIN SIP	\$ 0.75
4 POS DIP SWITCH	\$ 1.75
20 PIN MALE RT ANGLE	\$ 2.95
20 PIN FEMALE, FOR ABVS.	\$ 2.00
6 PIN POWER CONNECTOR	\$ 1.00
RCA JACK, PCB MOUNT.	\$ 0.75
50 P1 TRIMCAP.	\$ 1.00
220 OHM TRIMPOT.	\$ 0.75
68A45, VIDEIC IC.	\$ 16.00
MC3242, 128K IC	\$ 16.00

6502 STUFF


BB POWER SUPPLY	\$ 79.95
ABS NUMERIC CASE	\$ 59.95
ASCII NUM KEYBOARD	\$ 99.00
SYSTEM SAVIOUR FAN	\$ 45.00
GREAT DEAL	\$225.00
Z-80 WIRED	\$ 55.00
80 COLUMN WIRED	\$ 75.00
16K WIRED	\$ 59.95
WILDCARD WIRED	\$ 45.00
SAM TALKER WIRED	\$ 45.00
128K WIRED, NO IC'S	\$ 39.95
128K WIRED, 64K	\$119.00
128K WIRED, 128K	\$199.00
DISK(3) FOR 128K	\$ 20.00

BARE PCB


(A) REAL TIME CLOCK PCB	\$14.95
(B) QUAD DRIVE CARD (RANA)	\$24.95
(C) 9 VOICE MUSIC PCB.	\$14.95
(D) BUFFER PRINTER PCB.	\$19.95
(E) GRAPPLER PCB.	\$19.95
(F) CABLE FOR D, E, SPECIFY.	\$24.95
(G) 80 COLUMN, SOFTSWITCH	\$14.95
(H) DISC CONTROLLER PCB	\$12.95
(I) Z-80 PCB	\$12.95
(J) SSM MODEM PCB.	\$24.95
(K) MOUNTAIN MULTIFUNCTION	\$24.95
(L) 128K (SATURN) PCB	\$19.95
(M) RGB COLOR PCB	\$24.95
(N) EPROM PROGRAMMER PCB	\$12.95
(O) PIA PCB	\$14.95
(P) WILD CARD PCB	\$12.95
(Q) SAM TALKING CARD	\$12.95
(R) RS-232 PRINTER PCB.	\$12.95
(S) RS-232 MODEM (COMM) PCB	\$12.95
(T) RS-232 ASYNCHRONOUS PCB.	\$14.95
(U) SPRITE GRAPHICS PCB	\$17.95

BARE PCB FIRMWARE ETC.

(A) REAL TIME CLOCK DISK.	\$ 8.00
(B) 9 VOICE MUSIC, 2 DISKS.	\$16.00
(C) GRAPPLER EPROM	\$ 8.00
(D) 80 COLUMN, 3 EPROMS	\$24.00
(E) SSM MODEM EPROM	\$ 8.00
(F) MULTIFUNCTION EPROM	\$ 8.00
(G) 128K, 3 DISKS	\$20.00
(H) RGB CARD PROM	\$ 9.00
(I) RGB CARD DISK	\$ 8.00
(J) EPROM PROG. EPROM	\$ 8.00
(K) WILD CARD EPROM	\$ 8.00
(L) WILD CARD DISK	\$ 8.00
(M) SAM TALKER DISK	\$ 8.00
(N) SPRITE DISK	\$ 8.00

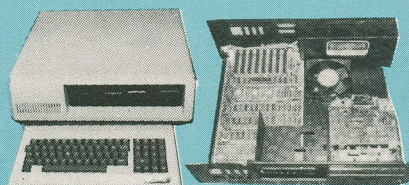**IBM PC™
LOOK-A-LIKE CASE**Make your Apple™ or 6502 machine look like an IBM
PC™. This attractive metal case with ABS front bezel
looks just like you-know-who, but is punched internally
to take all the 6502 Mother boards, power supplies etc
that are now sold. \$69.95
• Keyboard Case \$ 19.95**MAIL ORDERS**We accept: Personal Cheques, Postal Money Orders,
Certified Cheques, Travelers Cheques, Visa, American
Express, Mastercard, Bank Draft. We ship C.O.D. only
by CANPAR and Truck. We do not use Canada Post
C.O.D. We will send your goods via CANPAR or Canada
Post unless you say otherwise. You will be charged a
min. \$3.00 for delivery and handling or more if your
goods are heavier than the \$3.00 weight or if you specify
another delivery service that charges more. All
Ont. res + 7% sales tax. We sell wholesale to any
retail store or other reseller with a sales tax exemption
no. as long as a realistic quantity is bought. We ship
within a week if in stock and we will cancel any back-
orders over 4 weeks unless otherwise instructed. 20%
Restocking Charge.**MEGA BOARD PARTS**

(A) MAXI SWITCH KB	\$179.95
(B) IBM CASE	\$ 89.95
(C) ALL THE 82 IC's & 8088	\$159.00
(D) 8253-5	\$ 11.95
(E) 8259A	\$ 11.50
(F) 8237A-5	\$ 34.95
(G) 8255A-5	\$ 7.95
(H) 8288	\$ 37.50
(I) 8284	\$ 7.95
(J) 8088	\$ 34.95
(K) 100 NS DELAY	\$ 14.95
(L) 7 NS DELAY.	\$ 14.95
(M) BUS, BARS, SET OF 2	\$ 4.95
(N) 6-35 pf trimcap	\$ 1.50
(O) 62 PIN EDGE CONNECTORS\$	\$ 4.95
(P) 5 PIN DIN CONN, KB	\$ 3.50
(Q) POWER CONNECTOR, M/F	\$ 2.50
(R) 4.7K x6 SIP	\$ 0.75
(S) 4.7K, 16 PIN RES NTWK.	\$ 1.50
(T) 8.2K, 16 PIN RES NTWK.	\$ 1.50
(U) 33 OHM, 16 PIN RES NTWK.	\$ 2.50
(V) TBP 24s10 PROM	\$ 8.95

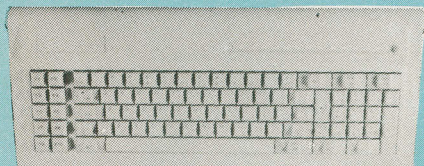**NEW FROM
MAXISWITCH™**

The finest most cost effective keyboard for the IBM™ PC or the APPLE™ that we have ever seen. The IBM model has all of the standard features of the IBM KB plus an improved return key for true typewriter emulation (For word-processing) Full N key roll-over, auto-repeat and more. The APPLE version has a lot more than the run of the mill APPLE keyboard, 10 function keys, cursor pad, numeric pad, and 21 preprogrammed commands to save a lot of typing. Just like the picture and just as pretty.

ONLY \$179.95

Please specify APPLE, or IBM PC, XT
NOTE: Complements our IBM look-alike case exactly.

**DEALERS AND OEM MANUFACTURERS
QUANTITY DISCOUNTS AVAILABLE**

Ideal for

- **COMPUTERISTS**
- **OEM MANUFACTURERS**
- **DEVELOPMENT LABS**
- **UNIVERSITIES**
- **INDUSTRIAL APPLICATIONS**

**THE ULTIMATE OEM/PC
COMPATIBLE SINGLE
BOARD COMPUTER**

- ☐ **MEGA-BOARD™** with full assembly instructions \$99.95
- ☐ **USERS MANUAL** with theory of operation, schematics, block diagram, application notes \$19.95
- ☐ **MEGA-BIOS™** fully compatible MS-DOS/PC-DOS BIOS \$29.95

ORDER NOW!!!


ONLY!
\$99.95
Evaluation Board Kit

MEGA-BOARD™ Evaluation Board Kit!
(Blank board with full assembly instructions and parts list.)

Includes highest quality PC board with gold plating, silk screen, solder mask

new! MEGA-BOARD™

IBM is a registered trademark of
International Business Machines

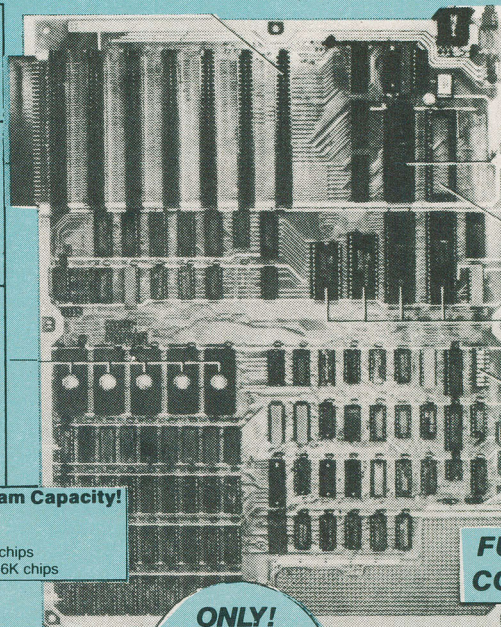**Eight Compatible
I/O Interface
Connectors**

(Full PC compatible)
(compatible with all
IBM-PC* plug-in cards)

**Special J1
Interface**

(Allows horizontal mounting of compatible expansion cards for easy bus expansion and custom configuring) (Board has 62 pin gold plated compatible connector)

**Extended ROM
Capability**


(Runs all compatible PC ROMS) (Jumper programmable to accommodate all popular 8K, 16K, 32K and 64K ROM chips and NEW EE ROMS! VPP power pin available for EP ROM burning!) (External VPP voltage required)

**Full Mega-Byte Ram Capacity!
On board!**

- (With parity)
- ☐ 256K Bytes using 64K chips
- ☐ 1 Mega Bytes using 256K chips

Standard Key-board Interface
(Full PC compatible)**Hardware Reset**
(Overcomes reset flaw in PC)**Power Connector**
(Full IBM* pinout compatible)**8088 Processor**
(Same as PC)**8087 Numeric Processor**
(Same as PC)**Peripheral Support Circuits**
(Same as PC)**Configuration Switches**
(Same as PC)**Speaker/Audio Port**
(Same as PC)**Wire Wrap Area**
To facilitate special custom applications!

**FULL IBM - PC*
COMPATIBILITY!**

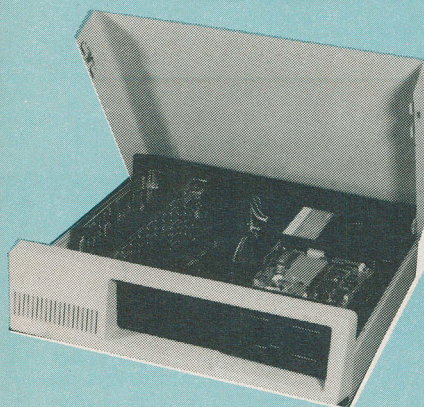NEW**IBM CASE**

At last, a nice new case for the IBM look-alike boards. Not cut for 6502. Fits the power supply types listed on this page and has cutouts for PC or XT (specify) card spacing, with card-guides and plastic Drive inserts and all mounting hardware, and with the greatest feature ever, a hinged lid that allows rapid and easy access to the insides. Spring clips hold it on at front so no screws need to be undone \$89.95

**WIRED N TESTED
MEGA-BOARD™**


- (a) Fully wave soldered and tested with all IC's and 64K of Ram on board, complete with bios, full manual, and schematic \$595.00
- (B) Fully wave soldered and socketed with all discrete and non-plug-in parts in place. Pre-tested on a bed-of-nails tester for any shorts and other faults. All you need are the plug-in parts and you are away \$319.00

**POWER SUPPLIES
FOR IBM PCB'S**

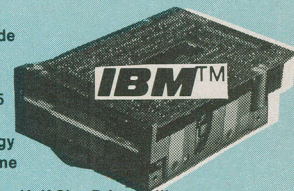
- (A) 100 Watts \$135.00
Has 2 drive connectors and plug to fit all IBM Clones.
+5V @ 10A +12V @ 3.5A
-5V @ 0.5A -12V @ 0.5A
- (B) 130 Watts \$179.00
Has 3 drive connectors and plug for all IBM Clones
+5V @ 14A +12V @ 4.5A
-5V @ 0.5A -12V @ 0.5A

WE'VE GOT EM!**5-1/4"
HALF SIZE DRIVES**

- 40 Track per side
- Double-sided, double density
- Same as SA455
- Latest head & drive technology
- Fast access time



Two of These Half Size Drives will
Fit in the Same Space as 1 Full Size Drive! **\$269.00**


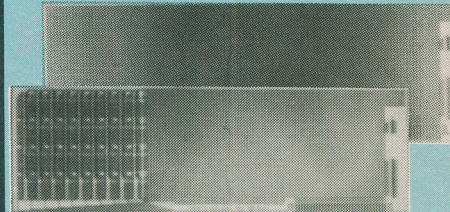
PROTOTYPING CARDS

- (A) **WIRE WRAP ONLY CARD.** An ideal card for high density wire wrap work. There are WW holes everywhere with a DB-25 and a DB-9 Footprint at one end \$29.95
- (B) **MEMORY AND WIRE WRAP.** A very good prototyping card for those doing video, memory, etc. cards. This card has the pads for a 256K 9 bit memory already laid out. All power and grounds run are in, pads for 0.1uf bypass caps on each 4164 are in, all control functions are gridded and brought out to WW pads, upward compatible to 41256, 256K memory chips. The rest of the PCB is WW on 1 centres with a DB-25 and a DB-9 footprint at one end for I/O \$34.95

Olivetti Portable

The M10 is based on CMOS technology and uses the 80C85 processor. Standard interfaces include a parallel printer port, an RS232 (up to 19200 baud), integrated modem, cassette and bar code reader interface. The liquid crystal display (LCD) tilts to a thirty degree angle for optimum viewing while leaving the keyboard at a proper angle for typing. The M10 is even further enhanced by a complete library of software which includes spreadsheets, databases, order entry, word processing, sales management, Forth, assembler etc. For further information, contact: Patricia Smith, Olivetti Canada Limited, 1390 Don Mills Road, Don Mills, Ontario, M3B 2X3 (416) 447-3351.

Circle No.56 on Reader Service Card

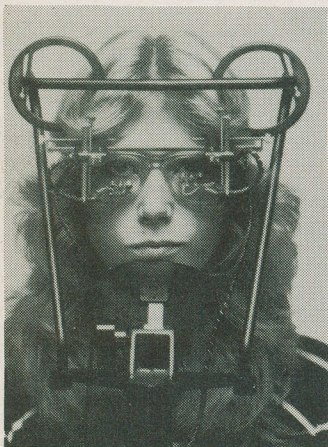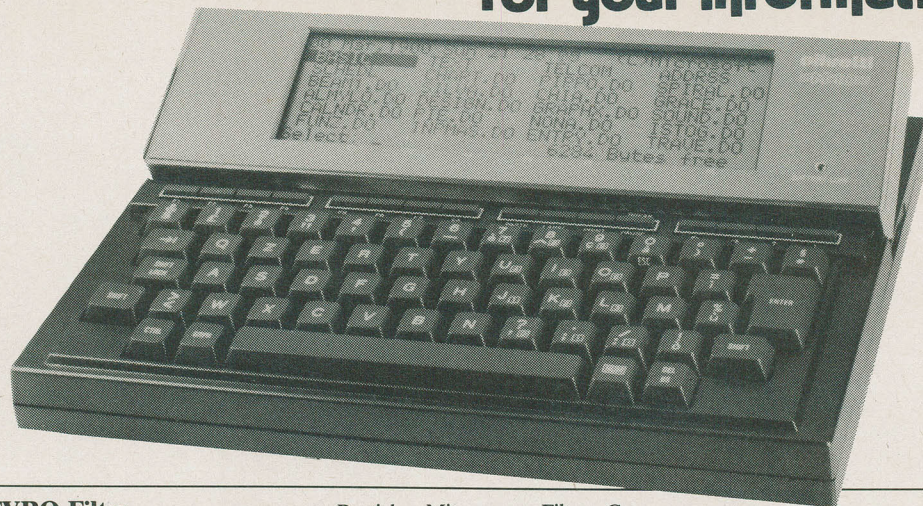


TVRO Filter

Terrestrial interference Trap 4616-60/80 incorporates a 60 MHz trap and 80 MHz trap, both switchable in and out.

The trap may be used as a diagnostic tool during installation or as a receiver accessory to optimize reception channel by channel. Impedance is 75 ohms and connectors are type F. Notch loss is 20 db minimum and 3 db bandwidth is approximately 4 MHz. Each notch is frequency tunable ± 5 MHz to compensate for nominal downconversion error. For more information contact Emily

Bostick, Microwave Filter Company, Inc., 6743 Kinne St., East Syracuse, NY 13057.

Circle No.55 on Reader Service Card

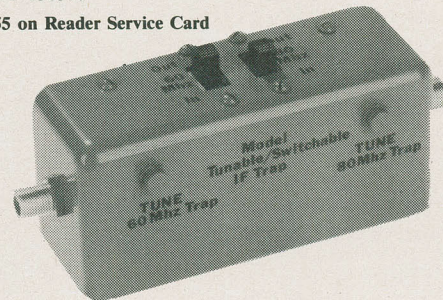

Hi-tech Mouseketeer

Will Walt Disney Productions reinstate the famous Mickey Mouse Club? And will they be using, as this photo suggests, a microprocessor-controlled, servo-operated, 256K, MS-DOS compatible mouse hat? We leave this to the reader's speculation.

Who is the Tradeport Electronics Group? Well, they're a new manufacturer's rep, located at 1179 Finch Ave. W., Downsview, Ont., M3J 2G1 (416) 736-0866. They represent all sorts of electrical and electronic measuring instruments, training devices, and R&D equipment, especially hard-to-locate firms from Europe: Black Star, Radford, Ferrograph, ITT France, Grundig, etc.

Circle No.51 on Reader Service Card



Multitech PC/XT

Following the introduction of the MPF-PC in November 1983, Multitech announces its latest addition to the company's MPF line of IBM PC compatible computers. The MPF-PC/XT features an integrated 10 megabyte fixed disk drive. Backing up the Winchester hard disk drive is a 360 KB capacity floppy disk drive, facilitating new program entry and copying of data files. The MPF-

PC/XT also provides a standard 128K bytes of RAM expandable on board to 256K bytes, dual serial communication ports, one parallel port, monochrome/color graphics adaptor, five IBM compatible system expansion slots, and more. The suggested retail price of the MPF-PC/XT, including the monochrome video monitor, is U.S. \$3,995. At Multitech dealers.

Circle No.54 on Reader Service Card



Comet Antenna

Mitsubishi Electric Corporation recently finished assembling a huge, 64-meter diameter antenna for observation of Halley's Comet. When completed in late October this year, it will be Japan's largest, and one of the world's largest, deep space probing antenna. Mitsubishi Electric is building the antenna for the Education Ministry's Institute of Space and Astronautical Science, which is in charge of the PLANET-A Project to observe Halley's Comet approaching the sun in 1986. The comet comes close to the sun every 76 years.

More on piracy: a Provincial Court in Calgary convicted a 26-year old gentleman on 50 counts of software piracy. He was duplicating commercial software from a flea market booth on a while-you-wait basis, at five to ten dollars a shot. Despite pleas from the software industry for a public hanging, the judge delayed sentencing. The case will no doubt set a legal precedent.

The Ferranti range of CM Series CO₂ waveguide lasers, RF or DC excited, covers the power rating from 1 watt to 30 watts and is intended for applications such as rangefinding, communications, beacons, velocimetry, laser surgery, in addition to a wide range of industrial applications such as cutting and welding of plastics, mask fabrication, engraving, etc. For additional information, please contact: EP Electronics International Inc., 187 Denison St., Markham, Ont. L3R 1B5, (416)475-8316.

Circle No.53 on Reader Service Card

The Ontario Government has a new catalogue — slightly used civil servants. No, but really, they've compiled a list of more than 900 Canadian producers of computers, word processors, components and software. It's available for \$10.00 from the Ontario Government Bookstore, Publication Services, 5th Floor, 880 Bay St., Toronto, Ont. M7A 1N8 (416) 965-6015.

Circle No.52 on Reader Service Card

Principles of Metal Detection

ETI looks at the history, techniques and uses of all kinds of metal detecting, from treasure-hunting to bomb disposal.

by Richard Turner

METAL DETECTION is a subject seldom mentioned in electronics journals, but recently it has attracted much attention in the daily press. Detectorists have been featured on many a front page with their finds of explosives or buried treasure, and perhaps even more while assisting the police in searches for weapons in some very controversial murder cases. However, metal detection has been around for about ten decades now and has been used for a very wide range of applications, and thus should be of interest to electronics enthusiasts.

Histories

While for hundreds of years treasure seekers and prospectors have used devices such as divining rods, magnetic needles and a variety of "doodlebugs" to aid their searches, it was not until 1879 that the first practical, scientifically proven instrument was built. The credit for this discovery goes to Professor D.E. Hughes, who demonstrated his 'Induction Balance' to the Royal Society in that year.

The Induction Balance attracted a great deal of interest among the scientists of the day, including the Chief Chemist of the Royal Mint who acquired one of the first units for the assaying of coins. Alexander Graham Bell applied the Induction Balance to the location of an assassin's bullet in the body of American President James Garfield.

This 'electric' metal detection had a good scientific start and it is worth examining in closer detail some of the many uses of the technology.

In Hughes' Induction Balance, a Leyden Jar supplied current to a microphone which was placed in contact with a ticking clock. Alternating current was achieved by a manually activated resonating spring contact assembly feeding two induction coils wound in opposition to each other. The pick up consisted of another pair of identical coils wired as a circuit with a further three coils and a telephone. This arrangement was



adjusted for complete silence in the telephone. To 'detect' or 'analyse' metal, the sample was placed on the primary coils, thus disturbing the mutual induction so that sound was heard in the telephone. Then the indicating coil in the secondary circuit was moved along a scale marked in degrees until silence was obtained again. Different samples could be identified against a previously prepared chart. This instrument was sensitive to such a degree that coins of the same denomination, but with varying amounts of wear, could be distinguished from each other.

Another detection principle developed in Victorian days worked on 'Sec-

dary Induction'. This involved a complex set-up but gave a considerable detection range. And indeed, when demonstrated at a Welsh metal mine at the turn of the century, it was found that metal ores could be detected up to three hundred yards away.

Briefly, the set-up was as follows: a battery supplied the primary current to a motorized contact breaker which 'chopped' it into a high frequency and fed the primary winding of a transformer, where the voltage was stepped up. The secondary output was fed to a pair of probes placed in the earth. A similar pair of probes placed some distance away fed another transformer to which there was connected a galvanometer. If there was no

Principles of Metal Location

metal in between probes, the input signal would 'scatter' in all directions and the galvanometer would remain at zero. The presence of ores or large metal objects would attract the voltage fed into the ground, producing an indication on the meter.

Electronic Principles

With the advent of electronics, the transmit-receive technique was quite accidentally developed. During World War One, the military developed sound ranging and direction finding equipment. It was soon found that large masses of metal such as bridges, railways and ships at sea interfered with the equipment and much re-design was necessary for proper operation. However, the 'interference' turned out to be a benefit as this led to the development of metal detectors for sensing enemy submarines and tanks at a considerable distance.

In the post World War One years, the transmit-receive technique was used for electrical prospecting and forms the basis of most metal detectors today. The heterodyne principle found much favour in the late 1930s and was used extensively until about five years ago. A more recent innovation in metal detection technology operates on the DECCO principle which was developed at Oxford Archaeological Research Laboratory in 1966. *Decay of Eddy Currents in Conducting Objects* is now better known as pulse induction. Few people are aware of what an important function metal detectors perform for their wellbeing and comfort. Most and possibly all food and pharmaceutical products are passed through metal detectors to ensure there are no nuts, bolts, swarf, pins or other alien items in them. Medicines like pills and powders receive the same treatment. Shoes are tested for unwanted insole tacks and even such products as textiles, carpets and linoleum are passed through a metal detector before dispatch to the customer.

In quarrying and mining industries the burden is checked for tramp metal such as drill rods, dipper teeth, and pick and shovel ends to prevent damage to cutters and diamond tipped grinders. Most of the world's airports are equipped with 'walk through' metal detectors to combat the carrying of illegal weapons. Accurate location of pipes has to be known when mechanized road or trench digging takes place. Lumber jacks and tree surgeons screen trees to detect bracing tie bars, bolts or nails which may be covered by growth and thus prevent a danger to power operated saws. Reclaiming timber is very much a practice with DIY enthusiasts, but why risk damage to your electric plane or sander by nails etc, when a quick scan will save the expense of new plane blades or sanding strips?

Medical Applications

As already mentioned, Bell used the Induction Balance to detect a bullet in a human body, and ever since that time medical metal detection has flourished. In 1885 the Royal Army Medical Corps developed quite a different metal detector for locating bullets and shrapnel in wounded soldiers. During World War Two electronic metal detectors were developed in Britain (Barnato Joel Laboratories), Germany (Siemens Electric) and the USA (Waugh Laboratories). The European detectors used the heterodyne principle at VHF, while the American unit was an electronic version of Induction Balance.

Currently the world's most advanced medical and veterinary detectors are of British manufacture, the Rope-Hall locator for Ophthalmic and Medical applications (Keeler Instruments) and Tektamet PI for veterinary use (Goring Kerr PLC). These high technology and patent protected detectors not only distinguish ferrous from non-ferrous metals but also indicate which metal is predominant. Thus the surgeon or vet has an instant indication as to what technique to use for extraction. If the metal is non-ferrous, a conventional cut and sew method would be employed, but a metal which has ferrous content can be removed by an electromagnetic extraction technique, eliminating surgery.

Treasure Seeking

With the Royal Mint using the Induction Balance for the assaying of coins, it became apparent that this instrument could be adapted for the location of precious metals. Soon 'Buried Treasure Finders' were very much the fad of Victorian society, and were seen wandering about the countryside with very strange


looking devices. However treasure hunting did not reach its peak until the early Twenties, when an Englishman by the name of Williams emigrated to Panama where he got a concession from the government to seek out the treasure concealed before the sacking of Panama City by the notorious pirate Captain Morgan.

Devising a transmit-receive metal detector capable of locating metals up to forty feet beneath the ground, he soon located cellars and secret tunnels packed with precious metals. Williams became very rich and his fame spread far and wide. Being a generous man he gave the plans for his metal detector to anybody who asked for it, and some of those ungrateful individuals even filed patents for it as their own invention. Thus with metal detectors being produced on a large scale, the rich with time on their hands once again took up the seeking of buried treasures. Most of them headed for the Cocos Islands where legend said that much treasure had been concealed by pirates. Franklin D. Roosevelt, a prominent lawyer, was one of the first to land, and even after he had become President of the USA he returned for another try. Malcolm Campbell, Admiral Nicholson and Commander Worlsey also led expeditions to the Cocos Islands.

Detectorists Today

However, pirate and legendary treasures are very much of a myth and today's detectorists take a much more practical view, seeking lost coins, jewellery and the like which has accumulated in the ground over the last two thousand years. Many previously unknown coins and artifacts have enriched our museums after being found in that way. Occasionally large hoards of coins are found.

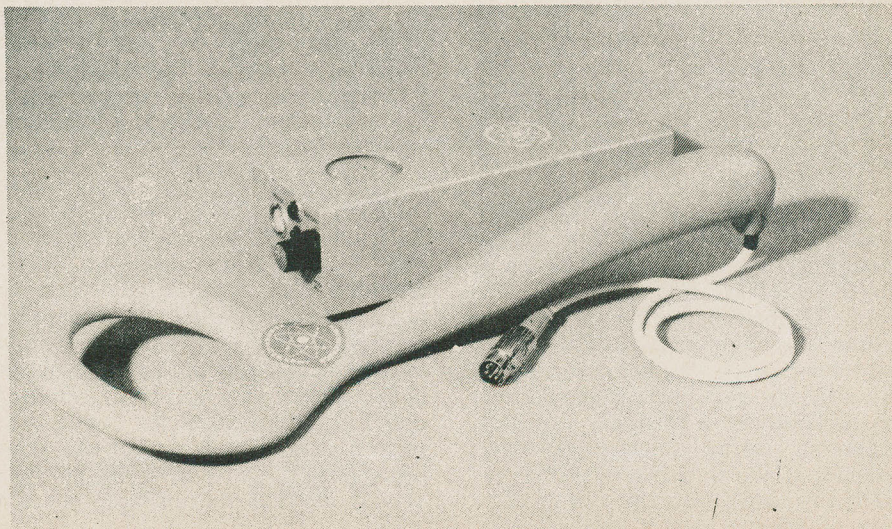Even wrecked ships can spread danger on the coasts, and an example of



The portable, belt-carried MD 199 can be used with a variety of probes. The one shown is a hand probe.

this was the wreck of *Aeolian Sky* which discharged its cargo of deadly cyanide canisters. In a situation like this a prompt search and recovery operation is required with metal detectors, as shifting sands and seaweed were quickly concealing the canisters. In this particular instance, the Detector Information Group (DIG) organized a search to assist Coastguards and Police, whose resources were stretched to the limit. This operation proved such a success that an annual beach clearance now takes place in May along the South Coast of England.

In the second half of this article, we shall take a closer look at the technical aspects of various detection techniques and brief specifications of commercial equipment. The block diagrams are in simplified form and show only the basic requirements for such detectors.

Heterodyne (BFO) Principle

Of all the possible ways of detecting metal, the heterodyne principle is perhaps the best known. After all, most radios use BFO (Beat Frequency Oscillator), so the system is easily understood even by a layman. The technique is simple, economical and produces very satisfactory results. The detector can be constructed from readily available radio parts; if a search coil of small but intense field is required (for instance, for medical applications) a ready made ferrite rod aerial can be used!

For larger areas and deeper penetration, the search coil is usually wound in multilayers on a circular former although printed circuit coils are also known. On a detector with wide range tuning, it is possible to detect metal against a metallic background, for instance, copper pipe embedded in reinforced concrete.

Off Resonance Discrimination (ORD)

In this technique, the search coil is driven by a frequency which typically differs by about 3 dB from the natural resonant frequency of the tuned circuit. This arrangement automatically gives a very selective detection. If for instance a discriminating detector is required for non-ferrous metals, the signal generator is driven at a higher frequency, but for ferrous metals at a frequency which is below the natural resonant frequency of the search coil. Thus in "treasure hunting" applications, excellent rejection of unwanted objects (nails, bottlecaps etc.) is achieved while retaining good sensitivity to desirable finds of coins, jewellery and the like. The main drawback of the system is thermal instability, for instance, if the detector is kept in the trunk of a car during hot weather, the search coil alters its natural resonance, and the separation between the drive and natural frequency of the tuned

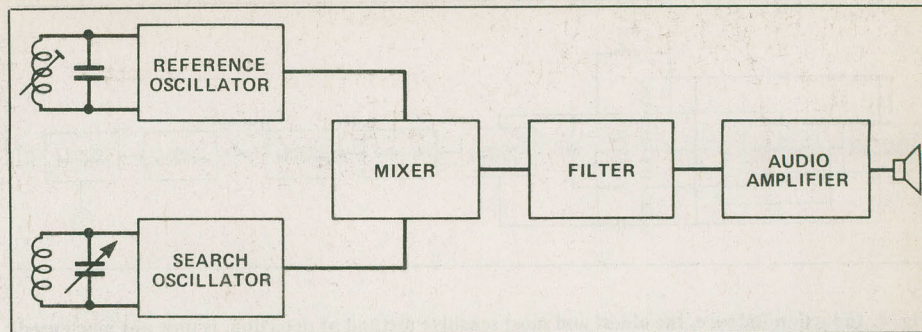


Fig. 1. A block diagram for a Heterodyne Principle (BFO) detector, the simplest type for a home constructor to design.

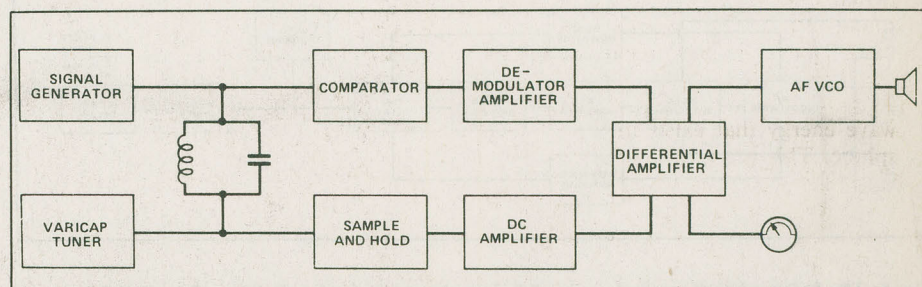


Fig. 2. The Off Resonance Discrimination System. Very selective, this method is favoured by "treasure hunters".

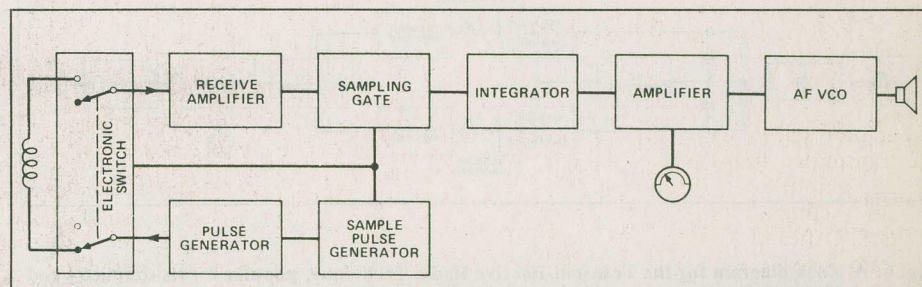


Fig. 3. The block diagram of a pulse induction system. This method uses the ability of metal objects to absorb and reflect electromagnetic radiation as eddy currents which can be detected.

circuit drifts so far apart that detection becomes difficult, if not impossible.

Pulse Induction System (P.I.)

This system differs from all the other methods as no oscillators or tuned circuits are required. Detection is achieved by the phenomenon of decaying currents in metal objects (DECCO). Thus a high amplitude short duration pulse is injected into the search coil, which emits electromagnetic radiation within its range. Soft objects such as soil or even aluminum foil allow the energy to penetrate and disperse while solid metals, especially magnetic metals, absorb and reflect this energy in the form of eddy currents which readily produce EMF in the search coil, generating a signal in the receive amplifier.

The main drawback of this principle is that Earth's magnetic field renders the detector oversensitive to ferro-magnetic metals. Although discriminating-type pulse detectors are now available, these do not provide such a good selection of desirable objects as continuous wave discriminators.

Induction Balance Method (IB)

This old and complicated, but most sensitive, detection principle requires several (or multitapped) search coils, and so is not exploited very much these days. However its sensitivity to precious metals is unsurpassed. As explained earlier in this feature, with a suitable arrangement even worn coins can be distinguished from new ones. This is achieved by phase-anti-phase magnetic fields which can be generated by

Principles of Metal Location

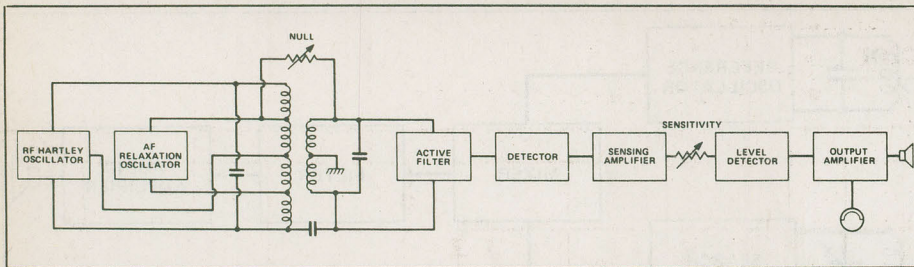


Fig. 4. Induction Balance, the oldest and most sensitive method of detection, is now not much used because of its complexity.

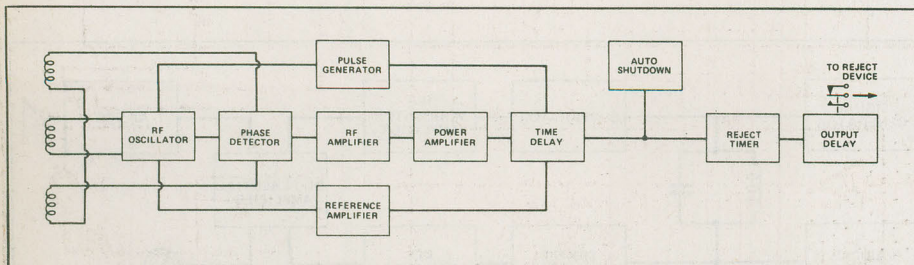


Fig. 5. The Balanced Coil method, a simplified version of Induction Balance, favoured for "production line" detectors because it is very sensitive at speed.

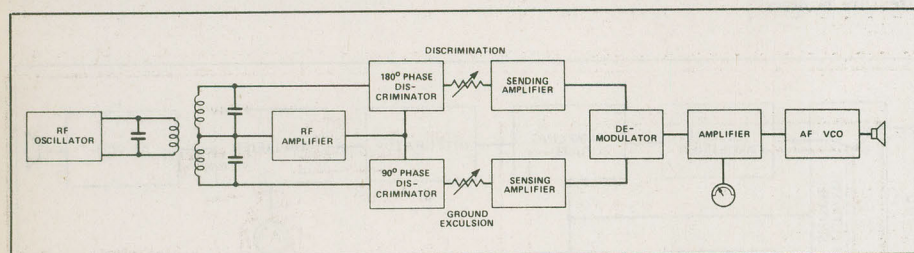


Fig. 6. A block diagram for the Transmit-Receive Radio Technique, popular for its simplicity and ability to discriminate between worthless and valuable metals.

complex coil arrangements, but energized by simple electronic circuitry with a very modest current consumption.

Balanced Coil Application (BC)

This is a simplified adaptation of the Induction Balance very much favoured by manufacturers of industrial detectors. And indeed the block diagram shows in simplified form an arrangement for a "feedthrough" conveyor type instrument. The search coils are usually of rectangular form wound in single layers, offering very high sensitivity. Typically a one millimetre metal sphere can be detected at a velocity of 40ft per minute through a 12 x 4in aperture.

The oscillator also initiates the pulse generator which is connected in a feedback circuit, thus offering a self checking func-

tion and automatically stopping the detector should a fault occur. If unwanted metal is detected, the reject timer allows the product to leave the search head and reach the rejection point where it is removed automatically from the conveyor belt.

Transmit-Receive Radio Technique (T-R)

This technique operates on true radio principles, and it can be seen why metal detectors come under the scope of Wireless Telegraphy Act. In early equipment (already explained) the transmitter was quite a separate item from the receiver which could be placed a considerable distance away, offering very deep penetration. However in recent times the trend has been to combine both units into one case for compactness and portability. A simple

sine wave oscillator drives a tuned circuit of a suitable frequency. A tuned search coil (or coils) feeds an RF amplifier to boost the incoming signal for the purpose of phase discrimination, eliminating unwanted signals from the ground (minerals etc.) and offering discrimination between unwanted objects and precious metals. Straight-forward output circuitry is employed. The simplicity of this technique makes it a very attractive proposition to manufacturers of 'hobby' type detectors which usually operate in the VLF spectrum.

Equipment Survey

To conclude this article, a survey is included of some commercially manufactured equipment manufactured in the UK. Each company has been limited to a maximum of five entries.


Some explanatory notes are worthy of inclusion as some readers may wonder, for instance, what is the difference between a hand and portable detector? A hand detector is a completely self contained one-piece unit whose total length does not usually exceed eighteen inches. However, headphones or earpieces may be supplied as optional extras. Portable units will have a separate search coil (or coils) or probes and electronics case, and can be in a shoulder-slung case or a hip mount design. Usually a range of optional extras are available, as in the case of medical detectors where even a reset foot switch is provided. A bench unit would be usually powered by mains and have a range of search probes for various applications.

Walk Through, as its name suggests, is a weapons type detector and at least one company manufactures such a unit in a 'portable' version which can be folded up and transported in the trunk of a car! Hobby detectors are usually of one-piece construction with the search coil for ground searching mounted on an adjustable shaft which may be mounted on an electronics case. Some models are available in hip mount versions. This description also applies to underwater detectors. Conveyor type detectors are limited to industrial applications, and such detectors are available with search coils from about 1 inch diameter (for pharmaceutical applications) to 50 feet for textile industries.

ETI would like to thank Terry Cantin of The Midas Touch for his assistance in providing information and metal locators. For further information.

The Midas Touch,
207 McRae Drive,
Toronto, M4G 1T4
(416) 421-4249

A Pulse Induction Metal Detector

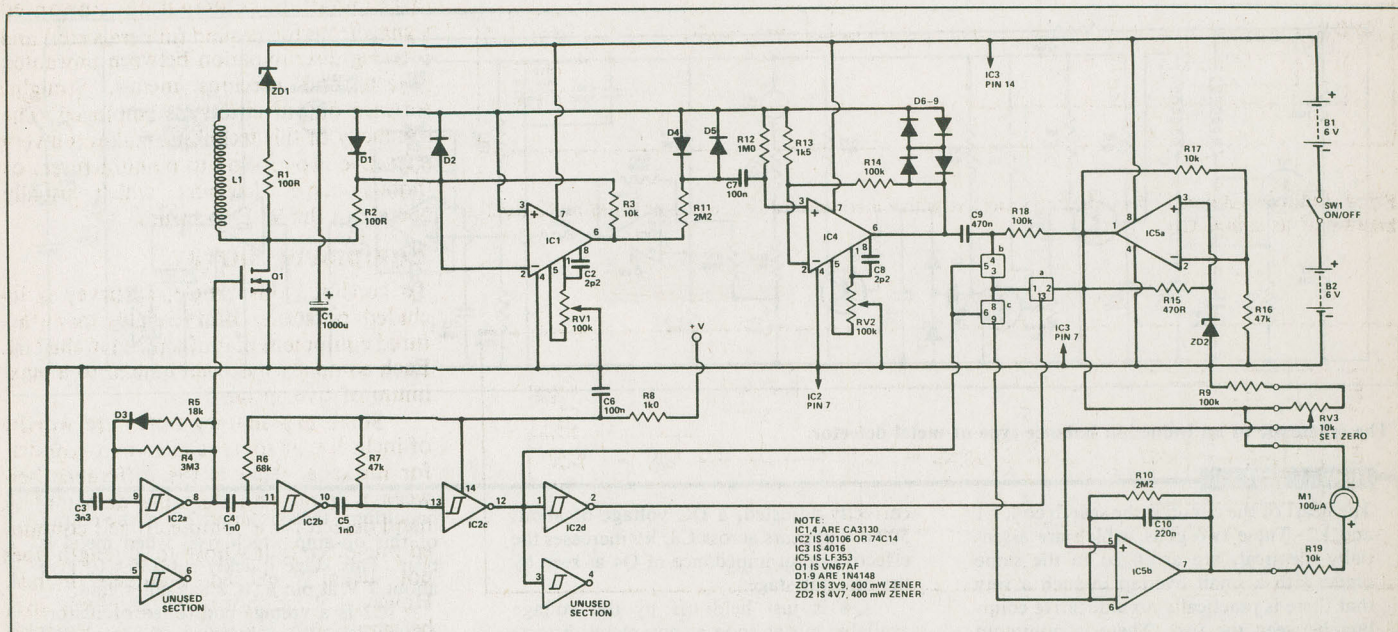


The schematic of a pulse induction type of metal detector.

HOW IT WORKS

Oscillator IC2a generates a positive pulse which turns on Q1, with the result that a current builds up in search coil L1. At the end of this pulse, Q1 is turned off and the voltage waveform shown below appears across the coil, and falls to zero in time X. If metal is near the coil, the voltage falls more slowly to zero (i.e., time Y). Operational amplifiers IC1 and IC4 amplify the coil voltage 10,000 times. Monostable multivibrators IC2b and c generate a second pulse, accurately timed after the first pulse, which is used to turn on an electronic switch (formed by IC3a, b and c) just as the coil voltage is reaching zero.

As metal approaches the coil, the voltage across it decays more slowly. Therefore, the pulses passed by the electronic switch get bigger.

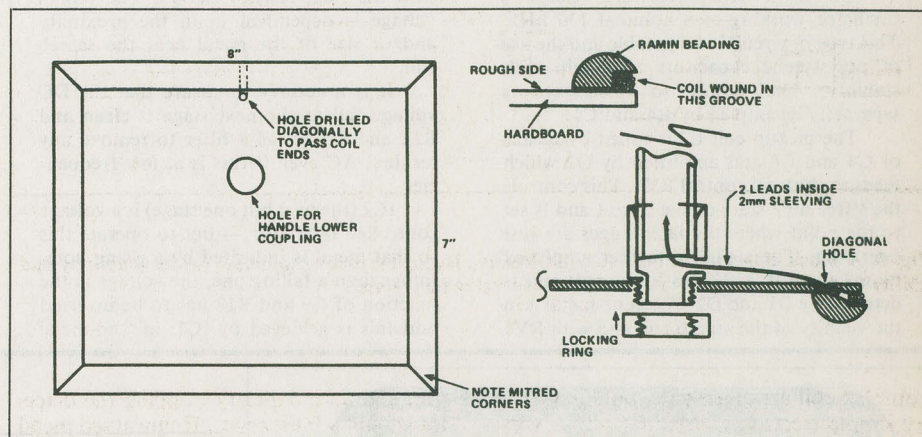Integrator IC5b amplifies and smooths the pulses from the electronic switch and drives meter ME1. The output voltage from the integrator thus increases as the coil approaches metal, and this is registered on the meter.




The underside of the search coil head and sections of the head showing coil wire leadout and routed up into the handle.

Winding The Coils

The housing is plywood or hardboard. 178 mm x 203 mm (7 x 8 inches) with grooved beading on the edges to hold the wire. Pass about 1 metre of 28 swg enamelled copper wire through the hole and then wind 22 turns of wire around the grooved beading. Pass another metre through the hole; the two ends of the wire should be long enough to easily reach the electronics.

An Induction Balance Metal Detector

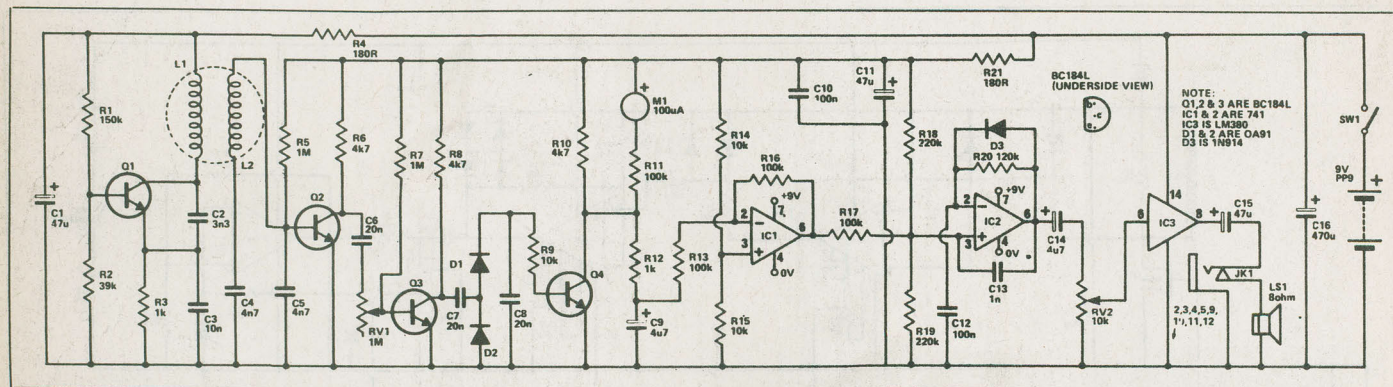

The schematic of an Induction Balance type of metal detector.

HOW IT WORKS

The heart of the circuit is the search coil, L1 and L2. These two coils, which are essentially identical, are arranged in the same plane with a small overlap in such a way that there is practically no inductive coupling between the two. There is minimum pickup when the fields generated in L1 are cancelled in L2 when in free air. Any metal brought into the electro-magnetic field of L1 will distort the field, causing pickup in L2.

Q1 is a straightforward Colpitts oscillator working at a nominal 130 kHz. This type of circuit is very stable and the use of polystyrene capacitors also help with stability. The supply to this stage is separately decoupled by R4 and C1.

The pickup coil L2 is tuned by means of C4 and C5 and amplified by Q2 which feeds to the level control RV1. This controls the "free air" state of the circuit and is set to the point where the later stages are just operating. The signal is further amplified by Q3 (here it is still an RF signal) and is detected by D1 and D2. When no metal is in the vicinity of the search coil and with RV1

correctly adjusted, a DC voltage of about 500 mV appears across C8. R9 increases the effective input impedance of Q4 as seen by the detector stage.

Q4 is just held off by the voltage available but as soon as any metal distorts the electromagnetic field, L2 produces a larger RF signal, a higher voltage across C8 and a consequent fall (from 8 V) in the voltage at the collector of Q4. This voltage is also monitored by the meter in parallel with the load resistor of Q4. The fall in voltage is dependent upon the proximity and/or size of the metal near the search coil.

It is necessary to ensure that the DC voltage fed to the next stage is clean and R12 and C9 act as a filter to remove any residual AC even if this is at low frequencies.

IC2 (the next but one stage) is a voltage controlled oscillator — but to operate this so that metal is indicated by a rising note, rather than a falling one, the voltage at the junction of C9 and R12 has to be inverted and this is achieved by IC1: in "no-metal


conditions, there is about 2 V at the output of this op-amp which rises when metal is near. This stage quickly saturates to give about 7 V at pin 6. IC1 has unity gain.

IC2 is a voltage controlled oscillator. In "no-metal" conditions it gives about 70 Hz which rises to 500 Hz when metal is present, diode D3 gives a rapid recharge to C11 and affects the mark/space ratio of the output which results in lower battery consumption. R20 and C12 can be altered for different range of audio frequencies if desired.

The output is taken to a volume control and fed to the LM380 audio power amplifier which in turn feeds the speaker.

The levels of signal around Q2,3,4 are all dependent upon transistor gain, temperature and supply voltage, but this doesn't matter because the level control RV1 is adjusted until Q4 just begins to conduct.

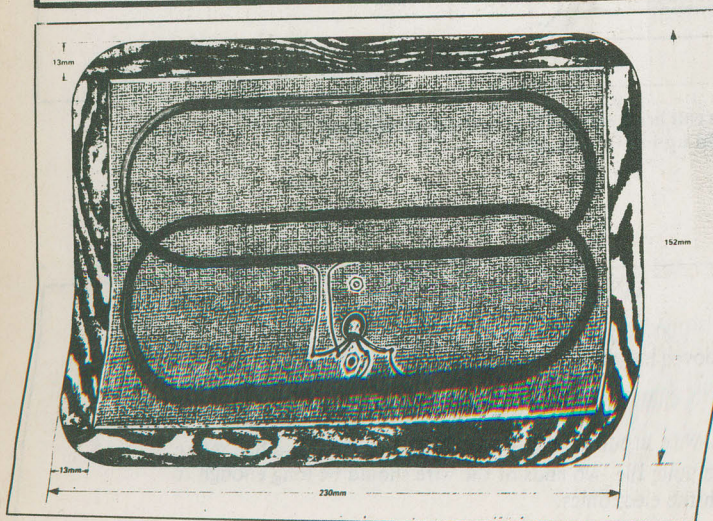Current drain for the complete circuit is in the order of 50 mA.



The search coil. This is L1 and L2 which are made from two coils originally wound on a 140 mm former and then squeezed into the shapes shown.


Winding The Coils

The search head is the key to the whole operation; be prepared to spend some time experimenting.

The housing of the coils is not important; a rectangular shape is used for ease of construction. The coils L1 and L2 should be sandwiched between two pieces of hardboard or plywood separated by two pieces of wood about 6 mm thick.

To wind the coils, you'll need a cylinder about 140 mm (5½ inches) in diameter. Using 32 swg enamelled copper wire, trap one end onto the former with tape and wind 40 turns as close together as possible. Remove the coil and wrap tape around it at intervals to keep it from spreading.

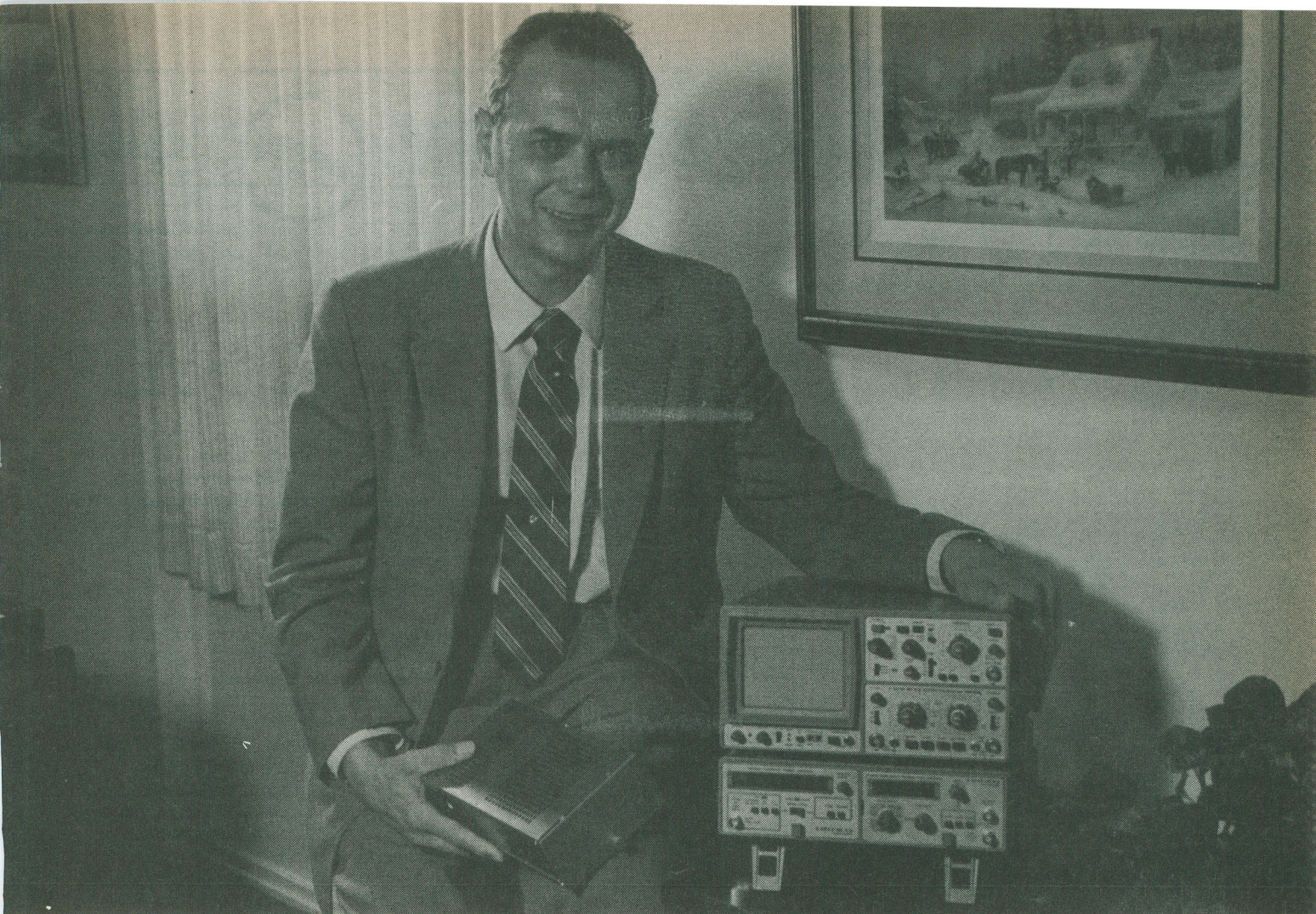Two identical coils are required. They should be glued into the housing as shown in the drawing.



Electronics Today helped Arthur Baier build his business

Arthur Baier, President of BCS Electronics Ltd., advertises to generate sales and profits for his company. It is that simple and the publications he chooses must deliver results.

Electronics Today has been the base of Mr. Baier's marketing plan for years. Not only does he choose full page monthly frequency but quarterly he uses Electronics Today to deliver his catalogues to Electronics Today readers. The reason is, Electronics Today does deliver results.

In fact, Mr. Baier says, "out of the ten major American and five Canadian publications I have used, only one, Electronics Today, has brought consistent results in reaching every corner of the Canadian Electronic Industry from the Yukon to Newfoundland. I rely on Electronics Today to give me results."

Electronics Today readers are informed, educated, and they buy. Next month is the month you should rethink your marketing plan and move to Electronics Today... every month.

Let our Electronics Today Account Executive show you how it can deliver for you.

Electronics Today can help build your business as well.

INTERNATIONAL

For Advertising Information Call (416) 423-3262

In Quebec (514) 735-5191

Motor Controller Project



Electric drills, saws, grinders, food blenders etc., all benefit from having some sort of control over their speed. Simple electric motor speed controllers, while proving speed control, have limited ability to maintain motor speed constant over widely varying loads. This project overcomes the limitations of these simple units and, despite its simplicity and low cost, is remarkably effective.

By Jonathan Scott

JUDGING BY users' remarks on the shortcomings of speed controllers on a variety of electrically driven appliances, and from much personal experience and observation, there is a *considerable need* for a well-designed speed controller for use with electric drills, grinders, saws, food blenders and other appliances driven by 'universal' electric motors.

The more expensive power drills now come with a variable control built into the trigger. Food blenders come *festooned* with an array of buttons marked with a ludicrous range of words with every synonym from 'mix' to 'masticate' represented!

These gadgets all have a severe limitation, namely, that they really only have voltage controllers, not speed controllers, for the motor in the unit. They vary the speed but provide little or no feedback speed control.

In the case of the power drill with a speed control in the trigger, the operator is in a position to adjust the trigger continuously in response to variations in the speed of the shaft, thus effectively becoming part of a feedback loop and serving as the speed *regulating* element.

The variable speed function of these latest drills is really not designed to allow the

slow steady pace needed for delicate or laborious jobs, but to allow the unit to act as an electric screwdriver, when fitted with the appropriate bit, where constant speed is not necessary.

Blenders, however, are items which you typically want to turn on and add more and more ingredients (adding more load) as the process progresses. What happens? The blender slows down as the load increases and it's real pain to have to keep adjusting it. If you're not careful, or in too much of a hurry, you can stall the motor quite easily.

Older electric drills and most high rpm grinder never had any sort of variable speed adjustment, electrical or mechanical. Grinders fitted with a special 'pad' wheel are used for building, too. But you have to be quite deft, otherwise it's easy to buff right through the undercoat of a painted object because of the ferocity of the thing.

If you need to drill a particularly tough substance with an older drill, then you have to be prepared to wear out the fine, sharp drill tip very quickly.

So, there is a distinct requirement for some device which can be placed between the appliance plug and the power that can be used to not only *set* the motor speed, but to *regulate* it as well.

The perils of simplicity

There seems to be fundamentally three degrees of complexity in the way one can design these circuits, each with advantages and disadvantages. All techniques employ some method of sensing the motor back-emf and adjusting the power delivered to keep the back-emf relatively constant.

For the sake of attaching 'handles' to each fundamental technique, I shall dub them — the *crude/economical* method, the *refined/economical* method and the *complex/ultimate* method.

For this project I have chosen the middle course for reasons which will become apparent shortly.

The crude/economical method is the simplest and for that reason has an extraordinary advantage in that it has a low parts count. This sort of circuit requires a diode or two, a pot, a couple of resistors and little else apart from the SCR switching element (see Figure 1). Now, it is hard to beat this sort of economy, but such circuits have a few annoying limitations.

Firstly, they will not usually drive anything but the most sensitive SCRs because they deliver very low gate currents.

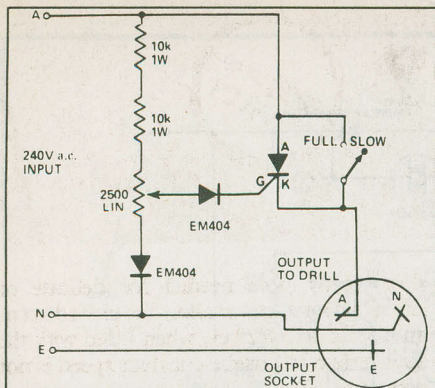


Fig. 1. An example of the crude/economical type of motor speed controller. This is the circuit of the ETI Speed Controller.

Secondly some component values can be critical, resulting in touchy or erratic response if tolerances are a bit out or the unit is driving an unusual motor. Lastly, the lack of an amplifying element in the feedback means that the speed regulation, while being above normal for a universal motor, is nowhere near perfect and the speed does drop under load.

To separate the two further types of controller requires a reasonable familiarity with what goes on when controlling a universal electric motor, so I will discuss the technique I have used in this project now and then go on to the explanation of further refinement.

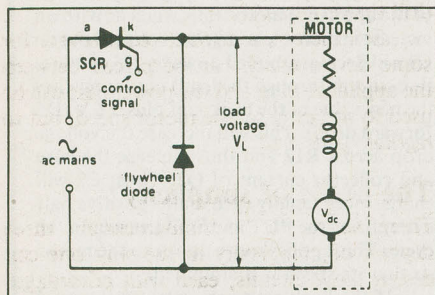


Fig. 2. Fundamental circuit elements of the controller used in this project. Note that V_{dc} is the back-emf of the motor.

Controller technique

A universal electric motor appears as a resistance, an inductance and a voltage source in series. The elements of the phase control system I have used — an SCR and a 'flywheel diode' — are connected as shown in Figure 2.

The voltage across the motor terminals during operation of this circuit will appear something like that shown in Figure 3. (Note that the vertical axis is not to scale.)

Considering the cycle from the peak onwards, let us examine the reason behind the appearance of each part of the waveform.

Say that, at some speed setting, the SCR is fired into conduction at about the 100° point of each positive half cycle. The load voltage jumps to a value very nearly equal to the mains voltage at that point (less

the small drop across the SCR) and follows the mains cycle variation until the end of that half cycle (i.e. at the 180° point).

Thus, the point between 0° and 180°, of the positive half cycle, where the SCR fires, defines how much voltage is delivered to the load (the motor). Varying the delay before firing provides a means of varying the power delivered to the motor. This is known as phase control, for clearly obvious reasons.

At the point where the mains voltage falls below the back-emf voltage of the motor you would expect the current through the motor to become zero and the SCR to turn off. But, this is not quite the case as the load is not purely resistive. The inductive component of the motor forces its terminal voltage negative in an attempt to maintain motor current, and indeed, the load voltage would follow the mains negative for some way if it were not for the diode connected across the motor terminals.

This diode conducts as the motor voltage goes beyond about 0.7 volts negative and carries the 'flywheel' current from the motor's inductance, generated by the collapsing magnetic field, allowing the SCR to isolate.

The flywheel current persists until the energy stored in the motor's windings is exhausted. This takes typically two to five milliseconds.

Were the diode not there, a large negative-going pulse would result. This, in itself, is not a bad thing, but it is easy to block this and reduce the net dissipation in the SCR, allowing it to control a larger device for the same ratings and prevents the need to make the controller circuitry more complex to resist the negative-going voltage.

At any rate, some way into the negative supply half cycle, the inductance ceases to be the dominating voltage source within the

motor and the back-emf becomes evident.

As you may see from the diagram, the motor voltage rises to a level defined by the apparent dc source within the motor equivalent circuit. (The 'back-emf generator'). This voltage is a result of residual magnetism in the metal of the armature and field coils and the relative motion of these two elements.

The actual back-emf developed depends on a number of factors, a major one being speed so it is a good representation of the motor's instantaneous speed.

There is some noise evident on the back-emf voltage, it is not a smooth dc level. This noise is partly due to commutation hash (high frequency spikes) and partly due to different amounts of residual magnetism in different armature segments etc. However, the noise is not sufficient to obscure the speed signal, or back-emf.

In a typical universal electric motor the back-emf would average around 10 volts at full rpm. The control circuitry in the controller looks at this dc signal and varies the point at which the SCR fires, increasing the delay if the motor attempts to speed up under decreasing load, or decreasing the delay if the motor attempts to slow down under increasing load.

The Perils Of Complexity

It turns out that, in the case of most motors, a very satisfactory degree of speed regulation can be achieved with only a hint of hunting detectable at very low speeds. This is most fortunate as it means that one does not require to advance to the next step of complexity, namely using the third technique mentioned earlier — the *complex/ultimate* circuitry with its own compensating system incorporated to guarantee the stability of the system under *all* conditions, despite large loop gain.

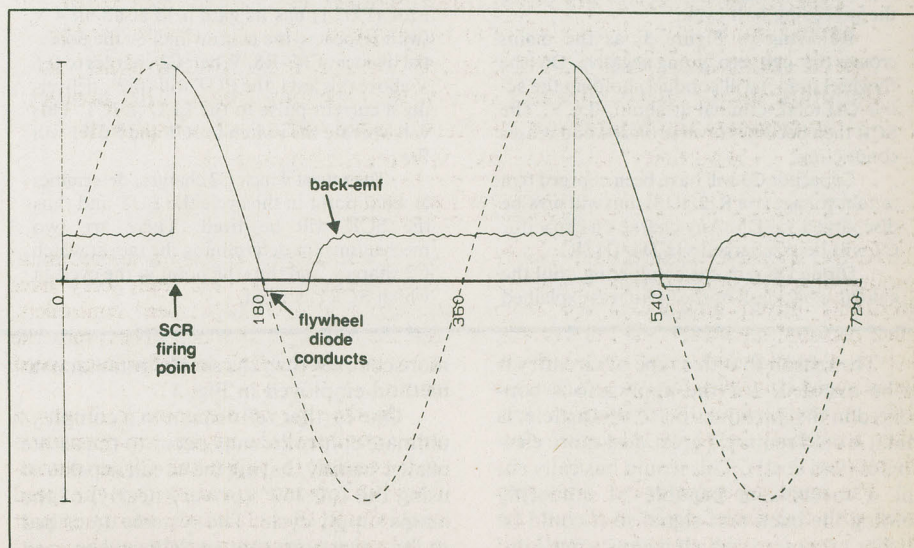


Fig. 3 Waveform of the voltage across the motor when using the ETI speed controller. (Vertical axis not to scale). The dashed line shows the power line input waveform.

Motor Controller

HOW IT WORKS

The speed of an appliance's motor attached to the project, is controlled by applying the mains voltage to it at a set point of the mains positive half cycles, as seen in Figure 3. This is done by turning an SCR on at the appropriate point in the cycle. Turning on the SCR earlier in the cycle applies more voltage, increasing the speed, while turning the SCR on later applies less voltage, decreasing the speed.

The SCR (SCR1) is 'fired' by applying a positive pulse to its gate. This is effected by IC1, an optically-coupled triac driver containing a LED coupled to pins 1 and 2 and a bi-directional optically-operated 'switch' coupled to pins 4 and 6. When the LED in IC1 is off, the switch is off. When the LED is turned on, the switch conducts. If pin 4 is positive with respect to pin 6, it will forward-conduct from pin 4 to pin 6, and vice-versa if pin 6 is positive with respect to pin 4. So that only positive-going pulses are applied to the gate of SCR1, D3 ensures that the switch in IC1 can only conduct during mains positive half cycles.

Resistor R6 simply limits the current through IC1 pins 4 and 6, while R10 prevents false triggering of SCR1 due to small leakage currents.

The control electronics consists of Q1, Q2, PUT1, IC1, RV1 and associated components. The 'flywheel' diode is D6. Power supply for the control electronics is derived by a half-wave rectifier from the mains input. This consists of D2, R2 and C1. This supply is regulated by ZD1, a 33 V zener, R2 providing current limiting. C1 is charged up during the mains positive half cycles and substantially holds its charge during the negative half cycles.


The SPEED control, RV1 is part of a potential divider — R3/RV1/R4. The wiper of RV1 sets a reference level on the emitter of Q1. This can be anywhere between about 4 V and 15 V (with respect to the neutral line), depending on the setting of RV1.


Now, let us see what happens from the point where the mains positive half cycles crosses through the zero point, going negative, at 180°, assuming SCR1 has been fired during the preceding half cycle.

Referring to Figure 3, as the mains crosses through zero, going negative, D6 (the flywheel diode) will conduct, holding the active (A) load terminal at about -0.6 V. The SCR then becomes reverse biased and ceases conducting.

Capacitor C3 will have been charged to a certain voltage (via R12/R13), but will now be discharged via D5. Any charge on capacitor C2 will be discharged via D4/D1/R1.

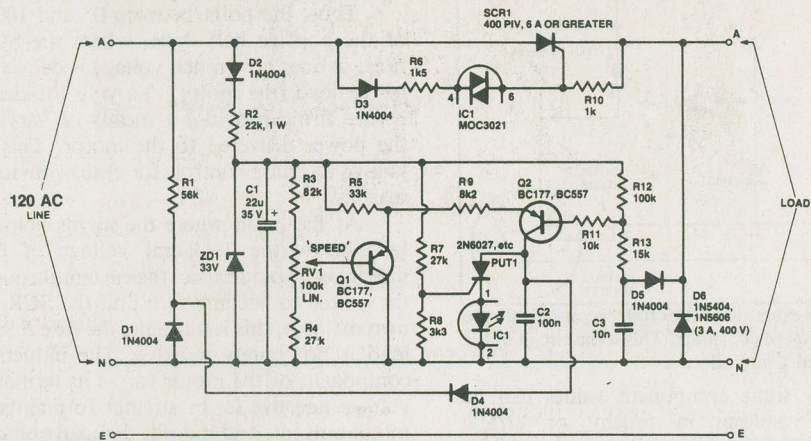Diode D6 remains conducting until the inductive backlash of the motor (as explained



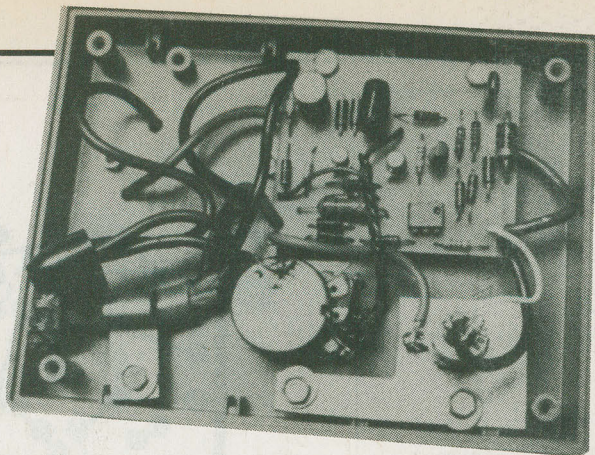

Inside. Construction is quite straightforward — but take heed of the safety precautions mentioned in the text! Note that in use there may be a slight 'dead band' at either end of the speed control rotation where nothing happens.

would be hampered by the inductive 'backlash' concealing the motor's true back-emf value. Any such system would have to be capable of operating in a mode which left only every fourth or sixth half cycle unemployed for the purpose of 'getting at' the back-emf for speed sensing.

While possible, this would not only require considerable circuitry, but would also tend to impart some roughness to the torque delivered. Hence, such methods are well abandoned for the applications for which the controller has been designed. It is a realm of circuit complexity which returns benefits only with physically large machines.

Back To The Project

The controller has been designed to be a good compromise between the crude/economical and complex/ultimate controller. Speed can be set from full rpm on no load (at 'half power') down to less than one-tenth normal. This is lower than you're ever likely to need. On low speeds and without any load there is a tendency for motors to 'hunt' about the set speed, power being applied in detectable jerks. But, even when only a light load is applied, this has the effect of damping the control loop, improving the control and smoothing out the variations.

The torque characteristics of the circuit are excellent, until you approach the 180° limit of the cycle — which is, in any case, way beyond what you will need in common situations.

A good 'worst case' example is that of making houmous, a particularly thick and pasty (tasty, too!) dip in a blender. Initially, the mixture is oily, but as the blending proceeds it changes to a very glutinous consistency and blenders invariably begin to labour agonizingly at this point. With the controller in control — no problems!

Construction

Safety is a major consideration in a project such as this. Choosing a box in which to house the components has to be done carefully because the project will be used in

a work environment, and is likely to encounter more than the usual amount of rough treatment.

I chose a strong, but not brittle, plastic case which comes in two halves, secured by recessed self-tapping screws that set into plastic pillars in the bottom half of the case.

Shape is unimportant, along with size, just so long as all the components can be fitted with ease and the box is not overlay large. If you choose a box with a metal fascia or panel, make sure this is *securely* grounded. If you can, get a box which provides internal posts to which the pc board and SCR mount can be secured with self-tapping screws so that no metal parts attached to these can protrude through the exterior of the case. If you must use a case that doesn't meet this requirement, secure 'the workings' with nylon nuts and bolts. All this is for your own protection.

The potentiometer used was of the conventional type, having a metal case, bushing and shaft. I grounded the pot. case, as shown in the wiring and overlay diagram. If possible, it would be an even better idea to obtain a pot. with a plastic bushing and shaft.

The mains cable *must* be firmly secured with either a clamp-type grommet where it enters the case, or with an ordinary grommet followed by a cable clamp. I used both a clamp-type grommet and a cable clamp, for good measure. (*That's probably overdoing it, but, please yourself — Ed.*)

Best place to start assembling the project is by drilling the few necessary holes in the box. If you are making a direct copy of the prototype, then positioning of the major components is clear from the internal photograph. If you're using a different box, then arrange the major components first and determine where you have to drill holes. Don't crowd the parts against one another. Use the blank pc board as a template for marking its mounting hold positions.

If you're using an SCR type that is not in a stud-mount package, then you'll have to arrange a suitable mount for it. I used a C220D type in a stud-mount, screwing it to a small piece of aluminum which also serves

PARTS LIST

Resistors (all ½ W, 5% unless noted)

R1	56k
R2	22k, 1W
R3	82k
R4	27k
R5	33k
R6	1k5
R7	27k
R8	3k3
R9	8k2
R10	1k
R11	10k
R12	100k
R13	15k
RV1	100k/A linear pot.

Capacitors

C1	22u/35 V RB electrolytic
C2	100n
C3	10n

Semiconductors

D1-D5	1N4004, EM410 etc.
D6	1N5404, 1N5606 etc.
IC1	MOC3021 triac opto-isolator
PUT1	2N6027, D13T1 etc.
Q1,Q2	2N3905
SCR1	any type, 400 PIV/6A or greater

Miscellaneous

pc board; case — 135 × 100 × 38 mm or similar size to suit; 3-pin panel-mount mains socket; mains cable and plug; small scrap of aluminum, self-tapping screws; screw terminal block; etc.

as a heatsink of sorts. SCR dissipation is small, so this heatsink/mount need only be small.


Just bolt the SCR to the heatsink without any insulator, and use some thermal compound to improve thermal contact between the body of the device and the heatsink. REMEMBER — the heatsink will be at MAINS POTENTIAL, so make sure when mounting it that no securing bolts protrude through the case or use nylon nuts and bolts.

I mounted the SCR separately to the pc board so that a wide range of SCR types and packages could be readily accommodated, from the stud-mount C220D I used in the prototype, to small 6 A-rated, flange-mount plastic pack devices.

It is difficult to specify a 'load rating' for the project in terms of the SCR's characteristics, because of motor surge current characteristics and the range of motor ratings in appliances. A 6 A-rated SCR will happily handle an appliance rated to draw a nominal 2 A under 'normal' load. The C220D used in the prototype will reliably handle an appliance rated at four to five amps, right up to full revs setting under almost-stalled-rotor conditions.

Before attaching the 3-pin panel-mount mains outlet socket to the outside of the case, attach *colour-coded* wires to its terminals and thread these through the holes drilled for them in the case. Take care that

Motor Controller

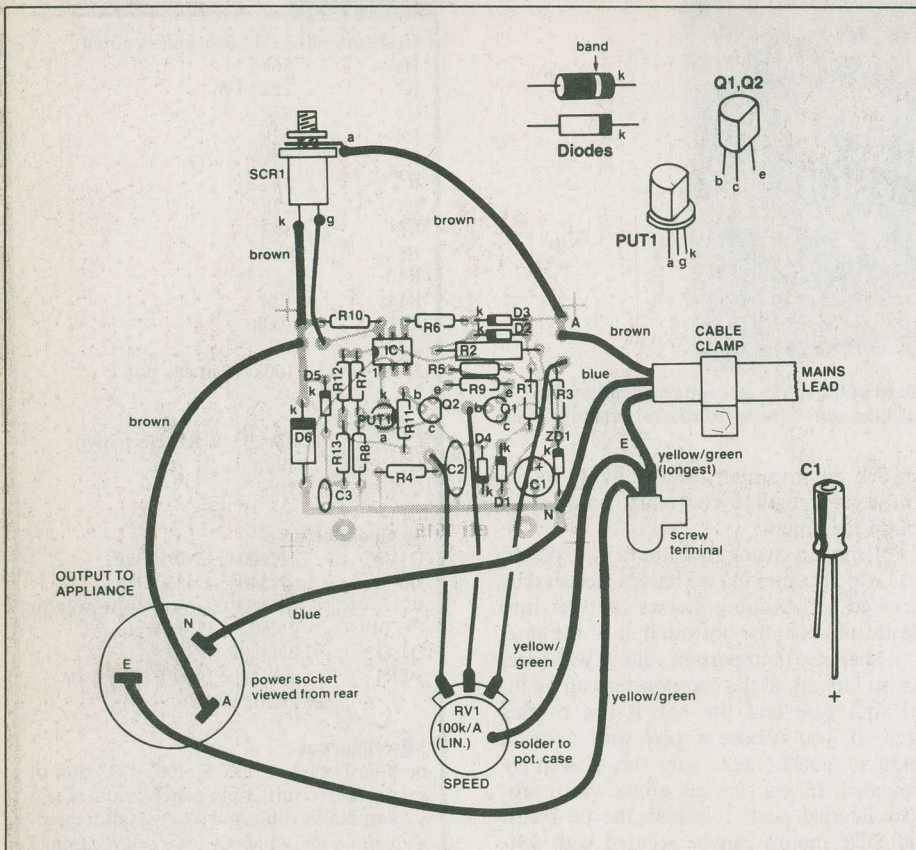

Overlay and wiring diagram. Follow this to assemble the pc board and wiring up of the external components.

you get the active (A), neutral (N) and ground (G) wires correct. Use wire from a short length of stripped-down mains flex.

When attaching the power cable, cut back the sheath so as to expose some 150 mm of the three wires to provide connections later. Make sure the cable is very firmly secured.

Mount the potentiometer using nuts on *both sides* of the case panel and lock the bushing tight so that there's no possibility of the pot. body coming loose and being rotated when the knob is turned.

Assemble the pc board next, according to the overlay diagram. You'll find it easier to solder the diodes in place first, followed by the resistors, capacitors and the rest of the semiconductors. As usual, watch the orientation of all the semiconductors and the electrolytic capacitor (C1).

Having done that check it. Make an especially careful examination of the soldering as diagnosis of problems will be dangerous and/or difficult later, because the board operates 'live'. In other words, if you are going to make only one project work first time this year, make it this one.

Attach the three wires that go to the potentiometer. Better colour code or mark these in some way to avoid confusion and wiring errors. Make sure they're long enough. Ordinary hookup wire will do for

these. An ordinary piece of hookup wire can also be used for the lead to the SCR gate. The leads to the SCR anode and cathode carry mains potential and load current and should be wired using mains-rated wire. Get it from some stripped-down mains flex, like before.


Now wire up the mains input cable and the mains outlet socket to the pc board, then check it.

Note that the ground wire on the mains input cable should be longer than the active and neutral wires. Should the mains cable come adrift, the ground wire would then be the last to break.

The Try Out

When you're satisfied that the project is correctly together, it's time for a try-out. Just plug in your drill, blender, or whatever into the outlet socket, set the speed pot. a bit up from minimum, plug the controller into the mains, and switch on. See that the appliance's motor rotates at some low speed. Advance the speed control and see that the motor speed increases, as expected. If nothing's happening at this stage, switch off, unplug everything, and go over your wiring (this assumes you *know* the appliance works).

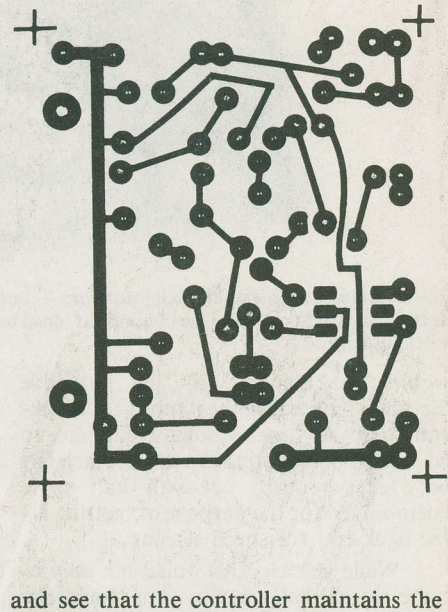If that works, then try applying a load with the motor set at some convenient speed



and see that the controller maintains the motor speed. If not, you've got troubles on the pc board and you'd better unplug everything and go over it.




If you are using the unit with an unusual motor, where the inertia of the armature may be greatly different to that expected by this circuit, you can vary the gain of the feedback amplifier by simply changing the value of R9. This can be varied between a minimum of about 150 ohms and a maximum of 22k.

Thus, if the motor hunts excessively (especially at low speed settings), R9 may be increased from the 8k2 value shown, reducing feedback loop gain and restoring stability at a small price in speed constancy. If the reverse is the case, you can acquire tighter regulation by reducing R9 — but check that hunting is kept to a minimum.

Finally, several words of caution are in order. The power bursts which are applied to the motor by the SCR switching and the control system variations with the motor armature running at low speed, applies a lot of stress to the motor's brushes and armature windings, so the controller should not be used in applications where it's not really necessary. Wear from the controller's use is unlikely to significantly shorten the life of an appliance, but it is never good practice to strain a mechanical device unnecessarily.

In addition, many appliance motors, particularly drills, employ a small cooling fan on the armature. The cooling effect of the fan is reduced, and extended periods of operation at low speeds should thus be avoided.

ETI

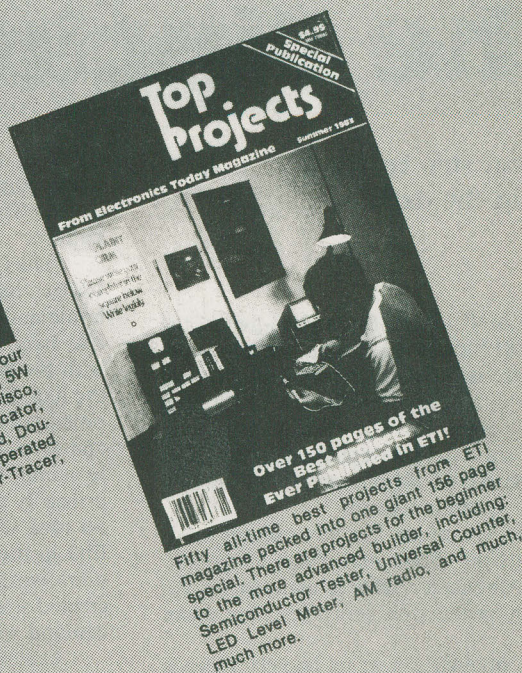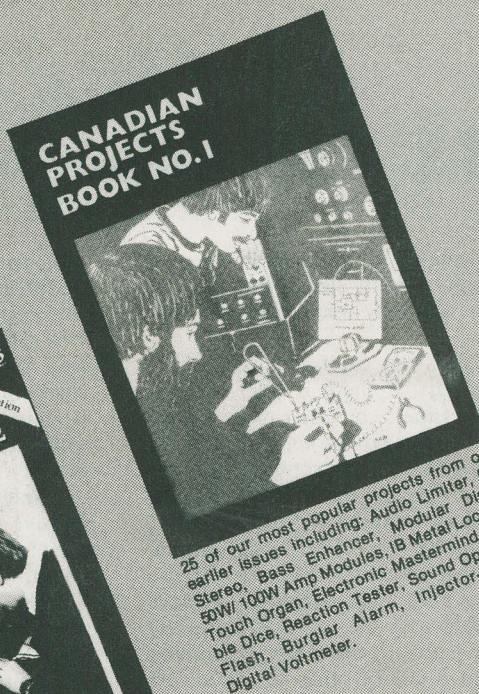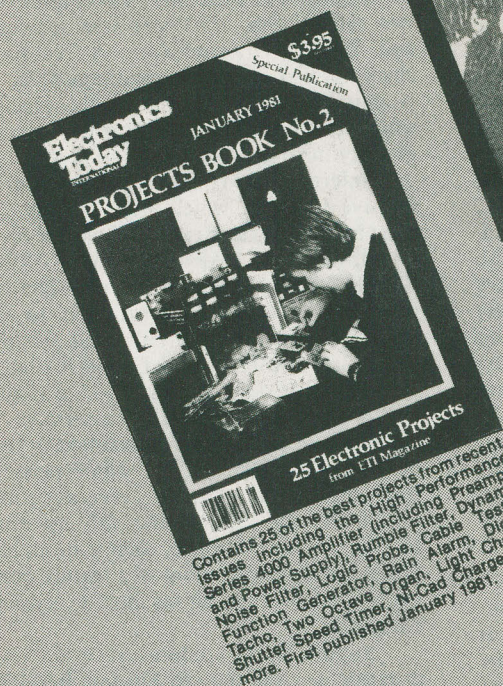


A Special Offer On 4 Special "Specials"!

On a time limited basis you can build a library of Electronics Today all time best projects for the beginner to the more advanced builder at a very special price.

Retail value of the 4 Specials shown totals \$16.80. Order now (cheque or credit details must accompany order) and you receive all four for just \$12.00 plus \$1.00 for postage and handling.

Write today to Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1.

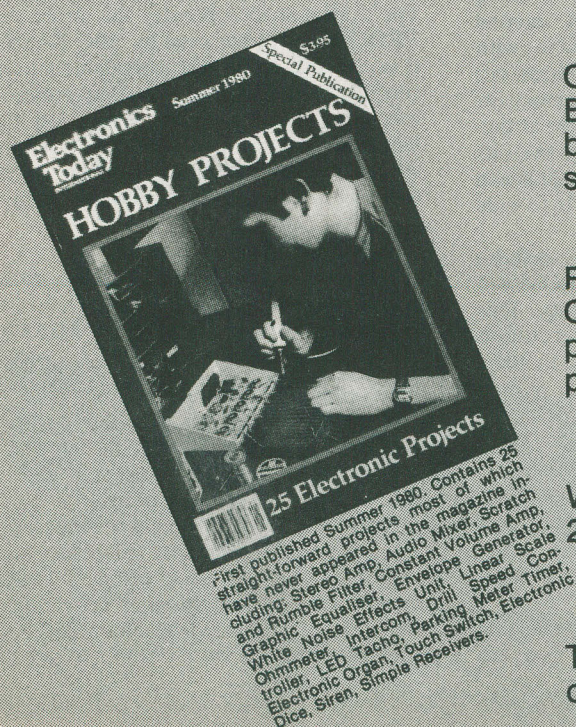To expedite your order call (416) 423-3262 with credit card details.



A Look at the Sinclair's QL

A giant step forward . . . or a leap in the dark?

CLIVE SINCLAIR, British designer of the ZX-80/81/Spectrum computers, and now Sir Clive, is about to have another go at capturing the lion's share of the micro market. Sales of the Spectrum (never released in Canada) were excellent, and Sir Clive expects to do the same with his new QL (for Quantum Leap).

The QL retails for 399 pounds sterling, between \$800 and \$900 Canadian. North American release is planned for the fall, but production shortages may mean delays.

As pointed out at its launch, there is no other computer offering anything like the power of the QL at anything near the price; the inclusion of four useful and well designed programs is a nice touch, and a sensible precaution against one of the most serious threats to a new computer — lack of software support. This is a marketing lesson which Sinclair has learned thoroughly but which others absorb only at great cost.

But then marketing is largely what Sinclair Research Ltd. are all about. The method is easily grasped, if not so readily followed by companies with less nerve. Somehow Sinclair manage to make and sell tomorrow's computer today, at yesterday's price. It is a leap-frogging process that reverses the normal procedure by which marketing-men take surveys to determine what the public wants, and then produce what they think the public needs. It is a technique (which has worked so far) whereby a new and innovative produce creates its own market: after all, was there

really a demand for a small inexpensive home computer until Sinclair released the ZX80? The QL may well follow the same pattern.

The QL is very carefully positioned to bridge the gap (if there is one) between home and business computer users: on the one hand it is cheap enough to compete with the Acorn/BBC, Commodore 64 and the like, but also powerful enough (at least potentially) to compete with Apple, CBM and even the IBM PC. Yet Sinclair candidly admit that although they see the QL primarily as a business machine, they have no idea what uses the QL will ultimately find in the hands of the target 3.5 million users world wide. In other words having created a supply, they earnestly hope that demand will follow!

Certainly the QL has features to attract interest from all sections of the computer-buying public, and promises to be an interesting machine to explore.

Inside Story

The specification of the QL is worth considering in detail. The main processor is Motorola's MC68008, the baby of the 68000 family but nevertheless a most powerful CPU. It has a 32-bit internal structure and is fully compatible with 68000 code. The 20-bit wide address bus can directly access 1M byte of memory (or memory-mapped I/O), but the most attractive feature to Sinclair must have been its 8-bit data bus, which means the 68008 can be operated with standard byte-wide memories and support chips.

As well as the 68008 the QL includes an Intel 8049 8-bit CPU with 2K ROM and 128 bytes of RAM on the chip. This handles the keyboard, sound generation and the RS232C receive function. In addi-

tion, two custom chips are employed: one is dedicated to memory management and the display, while the other looks after the two microdrives, the local area network and RS232C transmission. A real-time clock is also included, maintained by a back-up battery — a most useful facility which, in the age of digital watches, is inexplicably missing from most computers.


Internal RAM stacks up at a fairly massive 128K, of which 9K is free to the user; an 0.5 Mbyte expansion board is promised, which will take total RAM to 640K! The 32K ROM contains the new QDOS operating system, which promises to be very interesting, and an enhanced version of Sinclair BASIC, dubbed SuperBASIC.

QDOS is described as "... a single user multi-tasking, time-sliced system. . ." and was developed to take advantage of the power of the 68008 CPU. Multi-tasking (the ability to handle several jobs simultaneously) allows the QL to run several programs at once, each with an independent screen window — a feature normally available only on far more expensive computers.

SuperBASIC offers several improvements over the old Sinclair BASIC. For a start it incorporates the structured PROCedure format used by BBC BASIC; it is also said to be user-extendable and to run at a constant speed, so that program execution time does not depend on the length of the routine. Other features include easy interfacing to machine code, and access to the QDS operating system.

In And Out

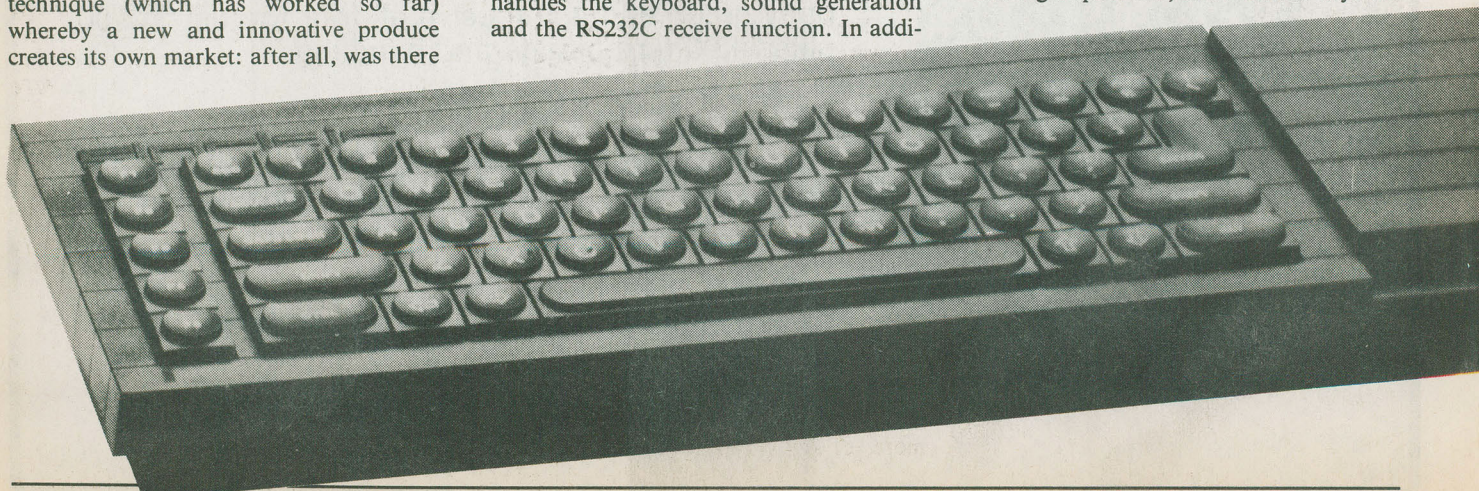The QL's keyboard has a full sized QWERTY layout with sixty-five keys including a space bar, five function keys and



four separate cursor controls. It is, apparently and a last, a proper keyboard!

Two microdrive units are built in, and a further six can be daisy-chained onto the expansion socket. However, these must be QL Microdrives; those made for Spectrum cannot be used, though the cassettes themselves are compatible if formatted for the QL.

A port at one end of the computer accepts ROM cartridges up to 32K in capacity, but once more ZX ROM cartridges are not suitable.

The QL offers alternative display outputs. Best quality is obtained from the Monitor port, which will drive either an RGB or a monochrome monitor. Two graphics resolution modes are available: 512 x 256 pixels with a choice of four colours (red, green, black, white, plus a 'stipple' feature) or 256 x 256 with a palette of eight colours. Normal character format on a monitor display is 25 rows x 85 columns.

The UHF TV output display modes are similar, but the use of the stipple feature is not recommended and the character format is typically forty six characters, depending on software.

Other features built into the QL include a local area network (QLAN) providing a link-up for up to sixty-four QLs or Spectrums, two RC232C ports and two joystick ports.

Onwards And Outwards

In addition to the 0.5 Mbyte memory expansion, an interesting list of peripherals and extensions is planned for the QL. The most important of these are the 68000 assembler, the analogue/digital interface, Winchester (hard disc) interface, modem and the parallel printer interface.

Finally there is the manual. A preview copy was released to interested journalists at the press launch, and while it would be unfair to criticise it at this stage it is plainly incomplete, with large sections either missing or very skimpy; one hopes that the final style is less opaque than that of the draft version. Bad documentation is un-

forgivable and a sin which infuriates reviewers and often leads to unfavourable comment on the computer itself.

Software

The 'software suite' supplied with the QL was written and licensed from Psion and consists of four integrated programs: QL Abacus, a spreadsheet; Archive, a data management/filing system; Easel, a graphics design program; and Quill, a wordprocessor.

All four are supplied on Microdrive cassettes and make extensive use of the QDOS operating systems, capability for separate screen windows. At the top of the screen is a Control window, which at all times displays a list of current options available, to the user; few lines of the screen to show information about the work in progress; and the Display window, a large area across the middle of the screen, shows the work.

The screen format is identical in all four programs, as is the command structure, so the learning curve for the complete suite is likely to be quite short. In addition data is transportable from one program to another so that, for example, business graphics can be generated from data imported from the spreadsheet.

Many other tasty features are listed in the documentation, including many found only on up-market business computers, so the indications are that the QL software suit will be a joy and a delight to use — Murphy's Law permitting.

Paper Tigers

Lest readers begin to think that the QL is all things bright and beautiful, a flawless example of computing engineering unmatched by any other, it has to be said that the QL does have a few shortcomings. Indeed the sceptics have already compiled a list of them.

The most serious criticism is the complete lack of a facility found on every computer in the QL's price range . . . a cassette interface (it's worth mentioning that a floppy disc interface is missing, too).

The implication of this is that cheap software is unlikely to be available for some time, because blank Microdrive cassettes currently cost around \$15.00 at retail prices, and the medium is not suitable for high speed duplication either. Taking a slightly longer view, though, it will probably not be too long before add-on cassette and/or floppy interfaces are available. Another possibility is that software houses will go for ROM-based programs, though this development must wait on the release of the 68000 assembler.

The Microdrive system itself is not yet proven to the satisfaction of many buyers. However the QL Microdrives may prove more efficient than those made for the

Spectrum; according to the provisional manual, QDS routinely stores as many files as possible in spare memory, reducing wear and tear on the tape and greatly increasing access time. And the 0.5M byte RAM pack provides a very substantial amount of spare memory! Another serious albeit temporary problem; is the lack of a parallel printer interface.


The remaining criticism of the QL (so far) have about them a faint aroma of sour grapes. Complaints have been made about the use of the 68008; its data bus is only 8-bits wide rather than 16, so it will be only a quarter as fast as the 68000 because it has to perform four times as many fetches; and with a clock speed of only 7.5MHz and QL will be slower than some of the faster 8-bit computers. Well, I wouldn't bet on it.

In fact both the 68000 and the 68008 fetch instruction in pairs of bytes (words), so there is not all that much difference between them, and Motorola data shows that on a 'quick sort' bench-mark test the 68008 clocks in only 10 milliseconds slower (30%) than the 68000 CPU running with a memory management unit. And at first appearances, the 68008 instruction set looks extremely powerful and compact (a point made several times by Motorola in comparing their 68000 family CPUs with other 16-bit processors), so machine code programs should run very quickly on the QL.

The remaining criticism to date concerns the choice — or rather the lack of choice — of colours in high resolution graphics mode. This criticism is relevant only to dedicated games-players, and even so its ultimate strength will depend on the effectiveness of the stipple feature in producing shades and tones.

Of course there will undoubtedly be other valid criticisms of the QL (it would be too much to expect any computer to be perfect) and these will show themselves when review models become available. Then experience will tell whether or not the QL lives up to its specification. The QL will not win kudos for the missing cassette interface, but this is not an insoluble problem: where Sinclair leads, others tend to follow, and if fast performance is any guide the QL and its add-ons will be every bit as successful as earlier Sinclair computers.

ETI

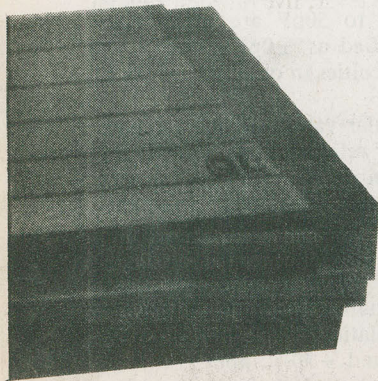

Coping with Components Part 2

This month we conclude our series on component identification with a look at capacitors.

Capacitors

A CONSIDERABLE variety of capacitor types are now available to the hobbyist, and most people will have a junkbox with many capacitors which are of unknown types, or carry strange markings indicating the values. The tables given here should identify most of the values, and the text and illustrations, the type of capacitor. It is important to select the correct type of capacitor for the job, as although there is some overlap in many applications, each variety has particular attributes which will make it more suitable for some purposes than others.

All capacitors are, of course, able to store electrical energy and consist of two parallel conducting surfaces separated by another material, which is an insulator, and known as the dielectric. The cheapest such dielectric is air, although the hobbyist will normally only meet this in variable capacitors (see later). The commonest dielectrics in fixed capacitors are mica, ceramics, paper, plastic and less commonly, oil, with other materials sometimes being used.

As DC current cannot flow through a capacitor, they are often used to separate DC and AC signals within a circuit. Nor does AC current actually flow through the capacitor — the movement of electrons from one electrode to the other only gives this appearance.

The amount of electrical energy which can be stored depends on the value of the capacitor, and the dielectric material used in its construction will determine the relative size for a particular value. A vacuum is used as a reference for the 'dielectric constant' with a value of 1 — higher values give the amount of energy stored per unit/volume as a ratio to this reference. Most plastic dielectrics such as polyester and polycarbonate have constants of around 3, mica around 6, and tantalum about 11. One material, barium titanate has a dielectric constant

up to 15,000 and is used in the dielectric of many ceramic types to achieve the very high capacitance/volume ratios in low voltages.

Temperature stability is often important, and especially in RF oscillator circuits, attention must be paid to this characteristic. It is usually expressed in parts per million (ppm) per degree Centigrade temperature change, and may be zero, positive, or negative.

The tolerance against the marked value of any capacitor will depend on its construction — in the case of electrolytic types, this may be as much as -20/+80% in any unit. However, this is usually not a problem in electrolytic applications, but should be kept in mind if the value has been calculated for any applications. In the opposite direction, mica types are available with tolerances of 1 or 2%, but of much lower capacitance value.

Paper Capacitors

Common some years ago, these have tended to be less frequently used. They are constructed by winding alternating strips of metal foil and paper into a roll with leads attached, or inserted into each end,

then impregnating with wax or a synthetic material, before environmental protection by means of an outer encapsulation.

The method above gives a capacitor with appreciable inductance — this can be reduced by a slight variation in the method of winding the layers when the foils are wound, so that they can be crushed together at the end and the complete end is then soldered to the wire lead.

These capacitors are best in voltage work, although the fact that paper will easily absorb moisture can lead to problems — the insulation resistance disappears quickly. Audio work was a common application at one time, but plastic based types are now normally used to their smaller size and better electrical characteristics.

Mica Capacitors

Mica is a natural mineral (although synthetic mica is now made) normally found in granite rock formations, and has the advantage of being totally inert, and a good insulator. It is also extremely stable (although it does absorb moisture) making this material excellent for high stability work, with a temperature coefficient not exceeding ± 100 ppm, and it is capable of passing high RF currents.

Mica capacitors are constructed by assembling alternating sheets of mica and foil, with the foil overlapping the mica sheets at each end. Alternating foils are then wrapped together and leads attached to opposite sides, covering the whole assembly with a dipping of epoxy resin, or a moulding to prevent water contamination. Tolerance specifications vary from ± 20 to $\pm 1\%$. In the 1% ranges, capacities up to 50pF are often alternatively specified as $\pm 0.1\text{pF}$, due to the practical difficulties in obtaining $\pm 1\%$ at low values.

A particular variety of mica capacitors, normally referred to as 'silver mica' are widely used in RF oscillator circuits, due to their excellent stability. The construction is different to the normal mica, as a thin film of silver is formed on each side of the mica sheet to act as electrodes, before impregnation, lead attachment and epoxy-encapsulation. Temperature coefficients are around +30-50 ppm.

Where the leads inductance would be a problem, a specially cased version is available without leads where the layers are sandwiched between metal clamps.

Table 2
Capacitor Markings

Polyester capacitors have the same coding as resistors with first significant figure of value at the top of the capacitor. An additional band at the end will indicate the working voltage: brown = 100 V, red = 250 V, yellow = 400 V.


Ceramic capacitors are usually marked with their value in figures (the old band markings have virtually disappeared) i.e., 22p = 22pF or 2p2 = 2pF2.

The "n" system is also frequently met where if the "n" precedes the figure, it is a multiplier of i.e., n22 = 220pF; or if it follows the figures, it is a multiplier of 1000: i.e., 10n = 10,000pF, 220n = 220,000 pF. Note that:

$$1500\text{pF} = .0015\mu\text{F} = 1\text{n5}$$

Also, another method is two significant figures plus multiplier to the power of 10, i.e.,:
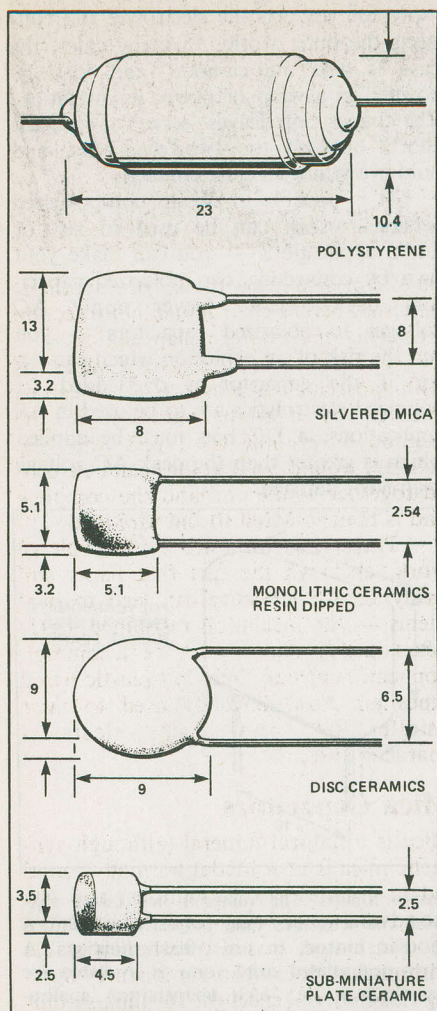
$$\begin{aligned} 104 &= 100,000\text{pF} (100\text{n or } 0.1\mu\text{F}) \\ 102 &= 1,000\text{pF} (1\text{n or } 0.001\mu\text{F}) \end{aligned}$$



Polystyrene capacitors offer high insulation resistance with good electrical properties.

Mica capacitors are used where high stability is required.

Ceramic capacitors are available in a number of different forms, each suited to a particular application.

N.B.: All dimensions in millimeters. All capacitor sizes vary according to the value; those shown are typical of each type.

These can be soldered directly to a printed circuit board, and are often used in VHF/UHF RF transmitter applications ('UNELCO' type).

Ceramic Capacitors


For a variety of case sizes, and confusing markings, it is difficult to beat the ceramic capacitor, probably most familiar in its round disc form. They are widely used in decoupling applications and at RF, as they have low series inductance, and in nearly all low capacity (up to about 0.1 μ F) non-critical applications. The dielectric material is normally an inorganic ceramic compound, with the higher capacitance types using one, or a mixture, of the higher dielectric constant substances such as barium titanate, mentioned earlier.

Silvered electrodes are formed on each side of the dielectric to which leads are attached, prior to covering with an epoxy coating for protection.

These high volume/capacitance ratio types are often referred to as medium or high K types (K being the dielectric constant) and have a number of disadvantages over the lower value type (up to about 400pF) which use lower K materials. Their temperature coefficients are extremely high (tens of percent in some cases), and the capacitance is affected by the level and

temperature coefficient groupings. The variation is from ± 30 to ± 1000 ppm, in groups, and as the change is linear, they have considerable use for temperature compensation in oscillator circuits. The case is often rectangular or square (with a thin cross-section) and a colour top identifies the grouping — these are often referred to as plaquette types. Tolerance groupings can be as low as 2%.

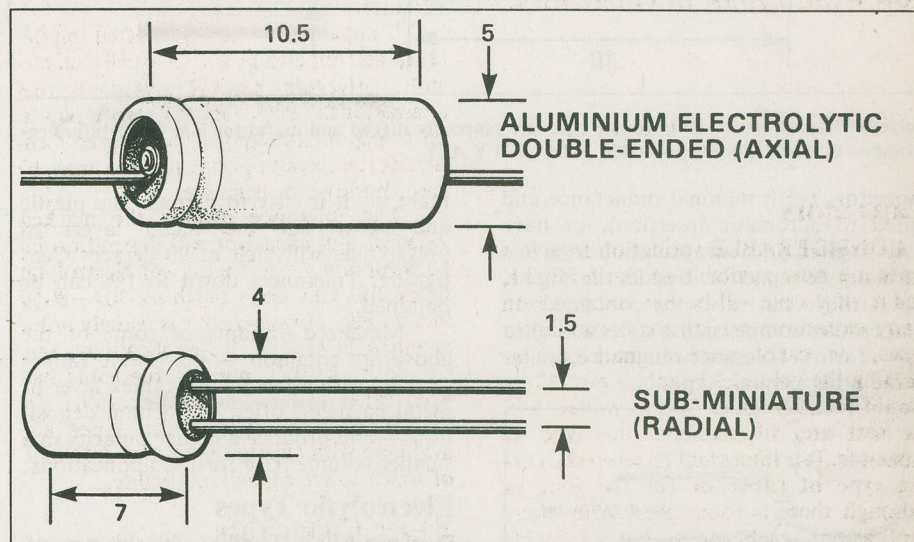One of the recent introductions is the monolithic ceramic capacitor, which can give a very high capacitance for a very



Electrolytic Capacitors: Axial electrolytics (top) are available in values up to 4700 μ F and at voltage ratings to 450 V. Radial types, either standard or subminiature (shown at bottom), are supplied in more restricted value and voltage ranges, but take less space on a printed circuit board.


type of voltage (AC/DC) present. Although they are both excellent for decoupling in solid state circuits both for logic and RF, they have no place in RF frequency determining applications. Tolerances are often in the 20/+80% region.

When selecting a ceramic capacitor for RF decoupling purposes, use values of .01 μ F for use up to about 15MHz; .0047 μ F to about 80MHz; .0022 μ F up to 120MHz; and 100pF (.001 μ F) to around 400MHz.


The smaller values have much more predictable temperature coefficients and good stability, and are available in

small size, together with a low AC impedance, making them ideal for high density solid state coupling and decoupling work in logic circuits, although they are more expensive than other ceramics.

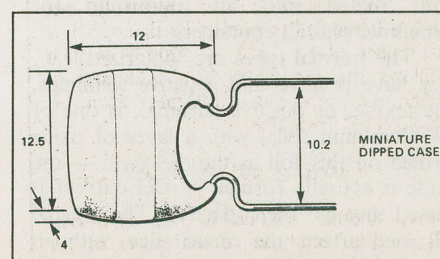Construction is by sandwiching alternate layers of ceramic compounds and resins and metal electrodes to form a large multi-layer unit. After heat processing, the blocks are cut into small units, the area determining the capacity value, solderable and encapsulations added, and in this form can be used as 'chip'




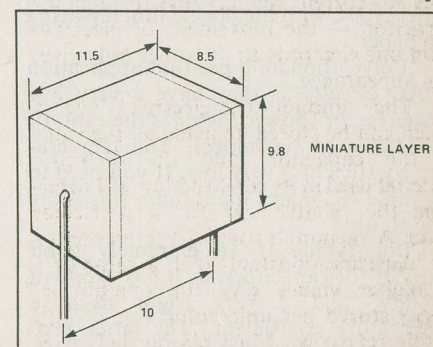Polyester Capacitors: The example shown above is the familiar 'C280 Polyester' capacitor. The dimensions are typical for values to 47n.




Polyester Capacitors: The box-like, silver coloured capacitors are sometimes referred to in catalogues as "Siemens" type, after the manufacturer.

Coping with Components

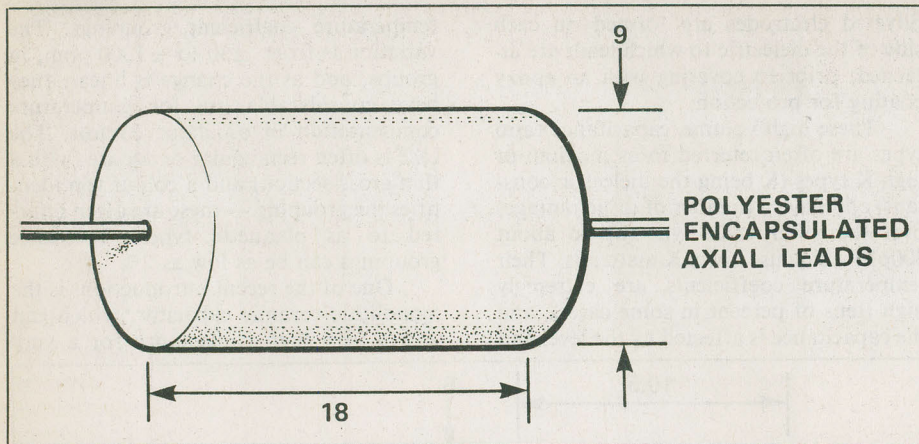

Polyester Capacitors: Axial polyester types are especially rugged and useful for high temperature environments; working voltages to 400 V DC (200 V AC).

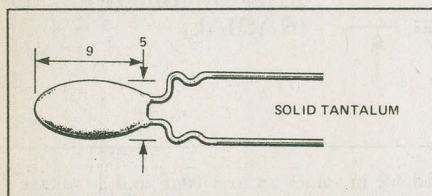capacitors (with minimal inductance and suited to automatic insertion), or have leads applied plus encapsulation to give a normal style capacitor. Besides the High K type, they can also be obtained in temperature compensating styles and ultra stable forms. Tolerance ranges are similar to the other ceramic types.



Tantalum Electrolytic: Preferred for accuracy in i.e., timing, filter circuits. They have very low leakage currents and good stability, but cannot withstand reverse voltages.

Plastic Film

The most common type is the polyester film capacitor which find wide application in DC circuits. The most familiar type will be the Mullard C280 type, which is also metalized and which look like lozenges, encapsulated in a hard lacquer case. Tolerances are around 10 to 20%, with a high temperature coefficient of about 20%. Construction is similar to that of paper types, with the plastic film replacing the paper.

Polycarbonate types find application in AC circuits as they have a very low power factor (power factor is the ratio of impedance to resistance). The temperature coefficient is very low. If you need to decouple AC mains input lines, this is the type to use.

Polystyrene is an extremely good material for capacitors, as it has excellent stability, and a very slight negative temperature coefficient. The latter property can be put to good use in compensating for the positive temperature coefficient of mica capacitors in oscillator circuits. Care needs to be taken in soldering

these, as it is easy to damage the plastic and short out the metal layers as polystyrene will melt at 90 degrees Centigrade. Tolerances down to 1% can be obtained.

Metalized variants of some of the above are common — the plastic film is covered with a few microns thick layer of metal particles, often by vacuum deposition — and produce a higher capacity in a smaller volume. Use for DC applications.

Electrolytic Types

Everyone will be familiar with this type of capacitor, although modern technology has produced many variants under this general title. The major difference between these and the previous types of capacitor, is that we are now dealing with an electro-chemical construction, rather than a passive one. They have many disadvantages, but despite this are widely used in virtually all high (greater than 1 microfarad) capacitance DC applications.

There are two main types of electrolytic capacitors — aluminum and tantalum.


Aluminum Electrolytic

In these, which are the traditional type, two aluminum foils are separated by insulating paper and wound into rolls. These rolls are then impregnated with an electrolyte, and after electrical stabilization, sealed into an aluminum (or sometimes plastic) container.

The normal types are 'polarized' i.e., they have positive and negative terminals. The anode, or positive terminal, is one of the aluminum foils, with a layer of oxide formed on this foil as the dielectric — the oxide is actually formed as DC current is passed through the capacitor. The type of foil used affects the capacitance, with an etched foil providing a greater contact area with the electrolyte which forms the cathode, and therefore a much greater capacitance over plain foil types. The

other foil contacts the electrolyte and connects the outer world. In many cases, the case is also the cathode, and may be covered in a wrap of plastic as insulation. The paper interleaves serve to prevent shorts between the two electrodes, and hold everything in close contact.

It is possible to obtain non-polarized versions, which can be used in AC or audio applications — you can make your own by connecting two polarized capacitors back-to-back. Never apply AC voltages to polarized capacitors — you run the risk of an explosion which can occur if the capacitor is overloaded. If polarized electrolytics are to be used in AF applications, a DC bias must be applied which is greater than the peak AC voltage to prevent damage.

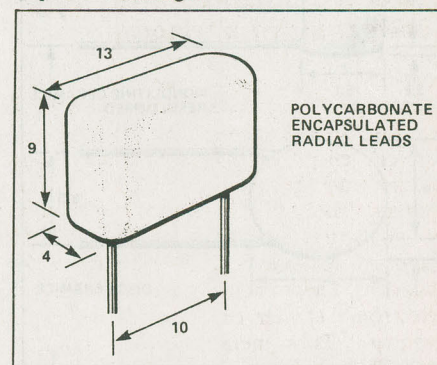

Polycarbonate: The material has better electrical characteristics than polyester and should be used instead, in ore critical situations. A brass-encapsulated axial form is available for super-critical (i.e., high temperature) applications where price is of no concern!

The electrolyte used depends on the application, but it should be able to repair any damage to the oxide film, and also to recombine any gases evolved by DC leakage current. If this does not happen, pressure will built up in the container with obvious results — larger units usually have a pressure relief arrangement to avoid danger.

Electrolytic capacitors have a large DC leakage current compared with other types, and this factor may be important if the capacitor charge is critical, as say in timing circuits. After a period on the shelf not being used, the oxide layer can start to disintegrate and allow a very large leakage current to flow. If full working voltage is applied in this condition, the capacitor can be seriously damaged — it should be reformed first over a period of hours by passing a small current through the capacitor via a 10-15k resistor, until the leakage current has dropped to a low stable value.

Values of electrolytic types vary from 0.1F to one farad, and the sizes from very small PCB mount types with wire terminations (either axial or radial), to be very large computer grade types (high reliability).

Everybody's making money selling microcomputers. Somebody's going to make money servicing them.

Now NRI Trains You At Home To Make Money Servicing, Repairing, and Programming Personal and Small Business Computers

Seems like every time you turn around, somebody comes along with a new computer for home or business use. And what's made it all possible is the amazing micro-processor, the tiny little chip that's a computer in itself.

Using this new technology, the industry is offering compact, affordable computers that handle things like payrolls, billing, inventory, and other jobs for business of every size... perform household functions including budgeting, environmental systems control, indexing recipes. And thousands of hobbyists are already owners, experimenting and developing their own programs.

Growing Demand for Computer Technicians

This is only one of the growth factors influencing the increasing opportunities for qualified computer technicians. The U.S. Department of Labor projects over a 600% increase in job openings for the decade. Most of them are *new* jobs created by the expanding world of the computer.

Learn At Home to Service Any Computer

NRI can train you for this exciting, rewarding field. Train you at home to service not only micro-computers, but word processors and data terminals, too. Train you at your convenience, with clearly written "bite-size" lessons that you do evenings or weekends, without going to classes or quitting your present job.

Your training is built around the latest model of the world's most popular computer. It's the amazing TRS-80™ Model 4, now with disk drive and the capabilities and features to perform a host of personal and business functions. No other small computer has so much software available for it, no other is used and relied on by so many people. And it's yours to keep for personal and business use.

You get plenty of practical experience. Under NRI's carefully planned training, you even install a *disk drive* verifying at each step its operation. Using the NRI Discovery Lab® that also comes as part of your course, you build and study circuits ranging from the simplest to the most



Become the Complete Computer Person

In addition to training in BASIC and advanced machine language, you gain hands-on experience in the operation and application of the latest computers for both business and personal jobs. You're trained to become the fully rounded, new breed of technician who can interface with the operational, programming, and service facets of all of today's computers. You're ready to take your place in the new electronic age.

Other Opportunities

NRI has been giving ambitious people new electronic skills since 1914. Today's offerings also include TV/Audio/Video Systems servicing with training on our exclusive Heath/Zenith computer-programmable 25" diagonal color TV... Industrial Electronics, Design Technology... and other state-of-the-art courses.

The Catalog Is Free. The Training is Priceless.


Send the postage-paid card for our 104-page catalog showing all courses with equipment and complete lesson plans. There's no obligation other than to yourself. See how NRI can help you take advantage of the exciting job and earnings opportunities in the exploding field of micro-computers. If card has been removed, please write to us.

advanced. You analyze and troubleshoot using the professional 4-function LCD digital multimeter you keep to use later in your work. Then you use the lab and meter to actually access the interior of your computer... build special circuits and write programs to control them. You "see" your computer at work and demonstrate its power.

Same Training Available With Color Computer

NRI offers you the opportunity to train with the TRS-80 Color Computer as an alternative to the Model 4. The same technique for getting inside is enhanced by using the new NRI-developed Computer Access Card. Only NRI offers you a choice to fit your specific training needs.

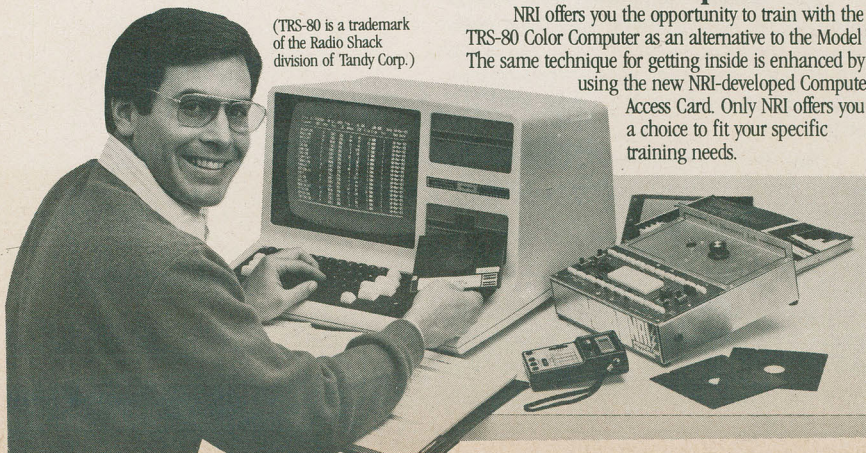(TRS-80 is a trademark
of the Radio Shack
division of Tandy Corp.)



NRI Schools
McGraw-Hill Continuing
Education Center
330 Progress Avenue
Scarborough, Ontario M1P 2Z5
or telephone 416-293-8787

We'll give you tomorrow.


Coping with Components

ty), with screw terminals. Working voltages are equally varied from 3 V for high capacity miniature PCB types to 400/600 V for power supply applications. Tolerance groupings are wide — often -20/+80% against nominal marked value.

Tantalum Electrolytic

This material is very popular in the form of tantalum bead capacitors, allowing miniature capacitors which are very stable and have long life — however, most cannot withstand reversed polarity to any extent. The construction of tantalum foil types is similar to that of aluminum types, but using tantalum in place of aluminum. In this case, the size will be similar to an aluminum one.

In wet-slug and solid electrolyte types, the anode is a pellet of masses of tiny tantalum beads partly fused together or a sintered pellet; covering these with a layer of oxide gives a vast increase in capacitance over aluminum types for a given size. The DC leakage current is greatly reduced and there are no shelf life problems; together with the size reduction, these factors make them very popular in high density solid state work, although their cost is appreciably greater. They are very useful for timing circuits.

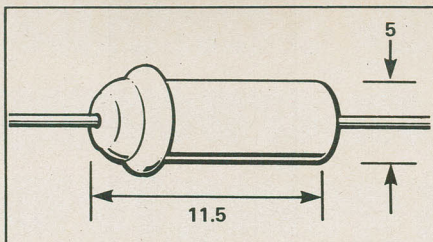

Polyester: This is a metalized film capacitor used in computer circuits and for professional applications.

Variable Types

These are generally known as 'tuning' capacitors, and are normally air spaced, although vacuum types are available for high power transmitting applications. The evolution of the transistor radio has also brought with it the plastic dielectric variable which offers high capacitance variation in a small, low cost package (sometimes referred to as 'polyvaricons'). Finding the larger high capacitance types is not so easy as it once was, as solid state has virtually eliminated the need for them, but rallies are useful sources if they are needed — otherwise they are expensive to buy new.

The air spaced types are available in a wide variety of sizes, capacitance, and voltage combinations. Multi-section types ganged together are common, and one particular type allows one-half of the gang to increase capacitance as the other half reduces. They are constructed from parallel sets of intermeshed plates, one set of which can rotate. The rotating plates are known as 'rotors' and the fixed plates as 'stators'. They are usually made of aluminum, brass, or copper, and may be silver plated in the last two cases for high frequency applications. The capacitance available is determined by the area of the plates, their number, and the air gap between them.

Varying the shape of the plates as they mesh, is sometimes used to give a logarithmic response to the capacity/rotation curve as an aid to linear calibration curves on analogue tuning dials.

The air gap determines the voltage rating above which arcing will take place between the pces — .015" gap will allow 600 V DC working, while transmitting types may have air gaps as high as 0.25" for 900 V.

Maximum capacitance values vary from a few tens of pF to about 400pF — the minimum capacitance for any unit depends on its construction, and could be around 3 to 5 pF for a 20-40pF maximum, to 20-40 pF for a 360pF version. This minimum unmeshed capacitance has to be taken into account when calculating oscillator or tuning coverages, and also the extra capacitance added by the wiring

to the capacitor, usually referred to as 'stray capacitance'.

Trimmer Capacitors

Another area where styles vary immensely. The basic air spaced trimmer is a miniature version of its big brother, with the vanes sometimes cut for a solid slug, rather than made individually as in the largest types. Screwdriver adjustment is normal, rather than via a shaft, and the overall capacitance value is unlikely to be more than 50pF. If higher values are required up to several hundred pF, mica compression trimmers may be used. These consist of two flexible metal plates, between which is a layer of mica. An adjusting screw is inserted through holes in the plates, into a ceramic base — tightening the screw compresses the leaves together, thus varying the capacitance.

Film dielectric trimmers are common now, and give miniature components of high stability — available up to about 60pF maximum.

Ceramic disc trimmers have the advantage of being extremely stable and are available in a wide range of values and sizes — sub-miniature types of only a few mm in diameter can be seen in some watches. Construction is basically a rotor with an area of silver plate on its top surface as one electrode. The other stator plate has a similar plated area, and the two halves are held together by suitable spring pressures. The two mating surfaces are ground very flat for stability. As the rotor is turned, the area of overlapping plate is varied thus altering the capacitance. Maximum values are about 100pF — the temperature coefficient of these may be several percent of the marked values.

There are, of course, other types of resistor and capacitor which you may come across — however, the preceding encompasses most types, and should help towards a better understanding of the limitations inherent in particular constructions.

ETI

MEET JACE

JACE is: - 100% compatible to Apple™
- super expandable
- very affordable
- complete with Numeric key board

Options: -CP/M
-128K
-80 col.
-speech
-and more

ONLY \$499.95
introductory price

SPECIAL THIS MONTH

(while they last)

Z80 (CP/M™) card	\$ 52.95
80 Col. card	\$ 85.00
Flip n File 50	\$ 35.00
Zenith monitor amber	\$159.95
Nashua diskettes with plastic box	\$ 22.95
-Slim disk drive	\$289.95
-Regular drive	\$279.95
-Disk controller	\$ 52.95
-16K ram card	\$ 52.95
-"Despiker" power bar	\$ 35.95

Send for free catalogue full of other fine products.

Send cheque or money order:
I.A.C. Electronics P.O. Box 83, Stn. "E"
Montreal, Quebec, H2T 3A5 (514) 270-6730
Que. res. please add 9% P.S.T.
(add 5% Shipping & Handling)

Circle No. 19 on Reader Service Card

MODULAR PROBES FOR SALE

For All Oscilloscopes
To 300MHz
X1 to X100
Attenuation

INSTANT REPAIR

Probe tip, Head, BNC and Cable
all screw into place
easily and quickly.

Pictured
Accessories
Included



980 Alness St. Unit 7,
Downsview, Ontario.
M3J 2S2
(416) 661-5585
TELEX 065-28169

Your Probe Specialists

COMPARE PRICE — COMPARE PERFORMANCE

Model	Attenuation	Bandwidth	Price
M12SW	X1-X10 Switchable	X1-10MHz X10-250MHz	\$56.80
M12X10	X10	250MHz	50.10
M12X10AP	X10 with Readout	250MHz	67.70
M15X100	X100	250MHz	56.80
M15X10HF	X10	300MHz	80.30
M12X1	X1	30MHz	42.40

Coline Canadian Sales & Stocking Source

Circle No. 13 on Reader Service Card

K.E.M. COMPUTER AND ELECTRONICS

ELECTRONICS PARTS

MEMORIES			
ROM	2716		\$8.25
	2732		8.25
	2764	250nS	13.50
	27128		35.50
RAM	6116P	150nS	10.45
	4116	200nS	2.95
	4164	150nS	9.25
CPUs			
	6802		6.29
	6809E		17.95
	68000	8MHz	74.98
	8085A		11.55
	8086		37.98
	8088		32.00
	Z80A	4MHz	5.95
Peripherals, CMOS, TTL --- Available			
INDUCTOR	0.27u-250mH		\$1.98-3.25
CAPACITORS			
	Ceramic Disc	1p-0.2uF	10-15c
	Mylar	1n-2.2uF	21-60c
	Polypropylene	56p-0.01uF	25c
	Electrolytic		Available
RESISTORS			
	Carbon Film	1/4W 5%	5c
		1/2W 5%	8c
		2W 10%	30c
	Metal Film	1/4W 1%	25c
MAGNETIC SENSOR			\$9.98
INFRA-RED SENSOR			7.50
ULTRA SONIC TRANSDUCER			
	TX or RX		4.80
OPTICAL FIBER DATA LINK			
	1meter Cable with TX & RX		19.50
STEPPING MOTORS			
	Several Types		Available
	Stepping Motor Control IC		16.50

EQUIPMENT FOR PCB PRODUCTION

ETCHING AGITATOR TANK with	
Air Pump & Thermometer	\$34.50
HEATER for ETCHING TANK	29.95
MINI HANDY DRILL	42.50
Drill Stand	23.50
AC Adaptor	20.25

PCB DRAFTING AIDS

Cutter Compass with Carbide blade	26.95
Rolling Cutter with Carbide blade	21.50
Precision Grid Polyester Films	
Tapes, Donuts, Templates	Available

PCB HANDICRAFT KIT \$14.95

Positive Photo-sensitive Printed
Circuit Board Handicraft Kit
All necessary materials, PCB,
Etchant, Developer, etc. 11 items

TOOLS

IC INSERTION	8-20Pin	\$9.95
	24-42Pin	15.95
IC EXTRACTOR	24-42Pin	17.95

ELECTRONICS KITS

KEM Original Series(See Last ETI Issue)
Full documents including circuit diagram
for every items \$4.00
(incl. postage)

Plus \$3.00 each item for postage &
handling charge. Plus provincial sales tax.
C.O.D. mail order accepted.

X-TALS, MICRO RELAYS, UV LAMPS,
ROTARY SWITCHES, POTS, ETC

KAIENTAI ELECTRONICS MERCHANTS LTD

2111 KINGSWAY, VANCOUVER, B.C. V5N 2T4
MAIL TO: P.O. BOX 69126 STATION 'K'
VANCOUVER, B.C., CANADA V5K4W4
PHONE: (604) 435-9697

Circle No. 16 on Reader Service Card

WHY SPEND A FORTUNE ON A DIGITAL CAPACITANCE METER?

The MC100A comes completely assembled and calibrated and at \$89.95 is an outstanding value. The extensive range of 1 pF to 9,999 uF (no external meters required) and true hand held portable size (only 4 3/4" x 2 1/2" x 1 1/2") make the MC100A an extremely practical and easy to use instrument for the hobbyist technician or engineer.

CHECK THESE OTHER FEATURES

- *Basic accuracy 1% (\pm one count) on pF, nF ranges, 3% (\pm one count) on uF range.
- *Uses single 9V battery (not included).
- *Decimal points light up when battery is low or when capacitor is overrange.
- *Full 4 digit high efficiency LED display uses special circuitry to save on batteries.
- *Constructed with a tough impact resistant plastic case.

ONE YEAR PARTS & LABOUR WARRANTY



DAETRON
935 THE QUEENSWAY
BOX 641
TORONTO ONTARIO M8Z 5Y9
(416) 255-9701
DEALER ENQUIRIES INVITED



1 pF to 9,999 uF

\$89.95

PLEASE SEND ME

____ (Quantity) MC100A(s) @ \$89.95 \$
Ontario residents add 7% PST \$
Postage — \$1.85 (per instrument) (C.O.D. orders add \$1.59) \$
☐ I ENCLOSE CHEQUE ☐ MONEY ORDER ☐ BILL MY VISA TOTAL \$
☐ VISA CARD NO. _____

EXPIRY DATE _____ SIGNATURE _____

Immediate shipping on orders with money orders, VISA or certified cheque.
Personal cheques please allow 2 to 3 weeks for clearance.

NAME _____


ADDRESS _____

CITY _____ PROV. _____ POSTAL CODE _____

MAIL TO DAETRON 935 THE QUEENSWAY BOX 641 TORONTO ONTARIO M8Z 5Y9

Circle No. 14 on Reader Service Card

Sony SMC-70 Review

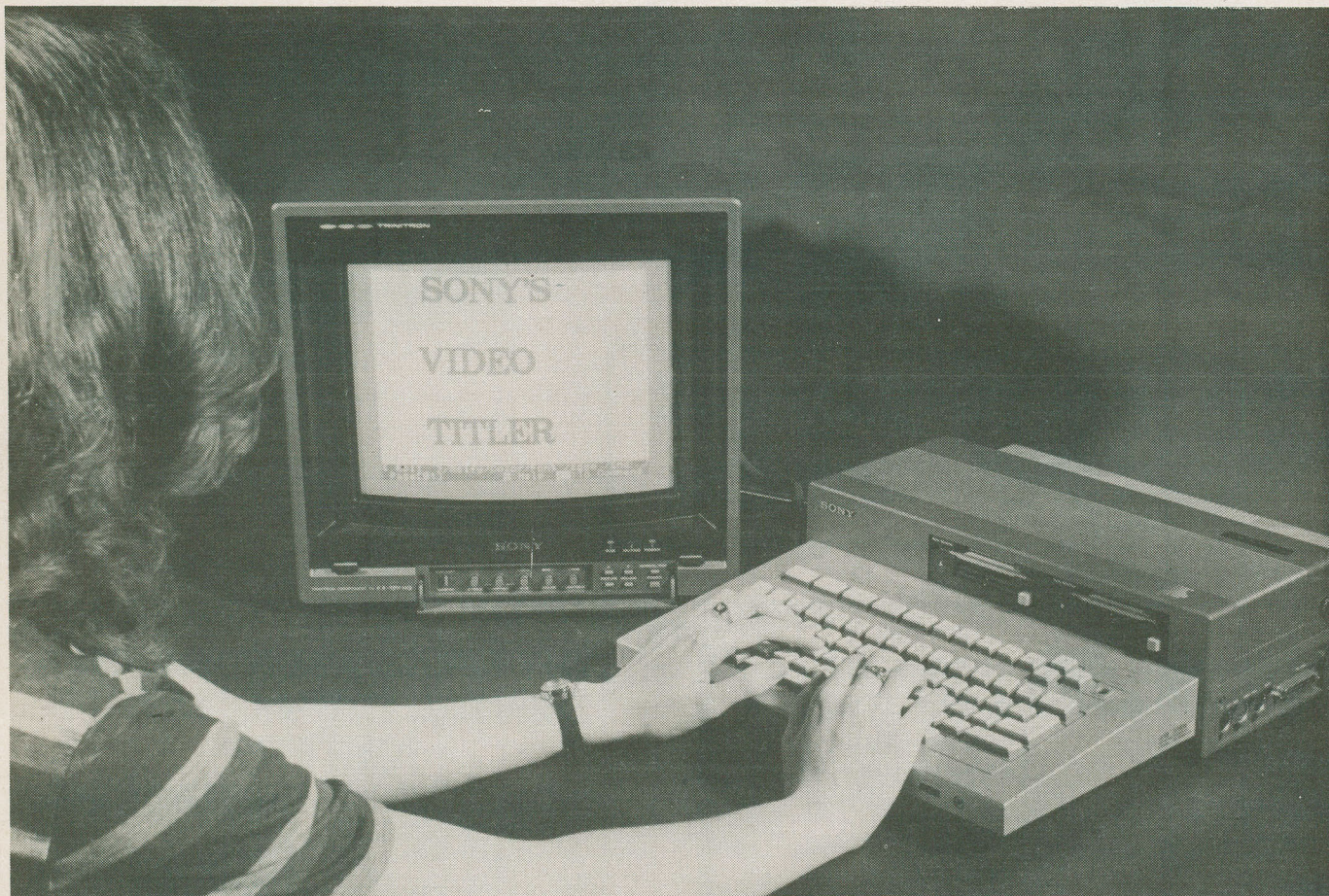

A new CP/M-based colour computer from the people who brought you go-anywhere-stereo and wristwatch TV.

by Edward Zapletal

WHEN SONY first dropped us a line to let us know that they were sending a micro our way, I thought that my ears were playing tricks on me. Was this the same Sony who have brought us the latest in audio and video gadgetry? You bet your ears it is! Sony's contribution to the ever-growing micro market is the SMC-70 microcomputer, a CP/M based, 8-bit, colour computer.

RAM Charged

At first glance, it looks much like any other micro around. A closer examination reveals a machine which not only runs CP/M, but has some outstanding graphics capabilities as well. The heart of the

SMC-70 is the workhorse Z80-A MPU. The 64K bytes of RAM may not seem like much, but considering that on top of this there is an additional 32K bytes of video RAM, 2K of character RAM, 2K of attribute RAM and 2K of Programmable Character Generator RAM (PCG), this should be sufficient for most applications, especially if the disk unit is used. The attribute RAM is used for specifying the colour of characters and symbols, setting the background colour, and inverting between characters and background. As for ROM, there is an ample supply of this as well, 32K bytes. This is comprised of 9K for the System Monitor, 22K for Sony BASIC, and 1K for character font.

From A To Z

The 72-key QWERTY keyboard is somewhat awkward, but it contains all the necessary buttons for graphics and editing. Next to the space bar there is a very prominent red and white key with an "H" branded on it. At first glance it looks like something one might see on the President's desk in the White House; in reality it is a very useful programmable HELP key which can be used to gain assistance in software such as GRAPHICS EDITOR, GRAFTALK, and certain other applications, including the word processor. The five programmable function keys are the heart and soul

of the '70; all the graphics and word processing are controlled quite effectively with these, and once you are used to this system, it's a breeze. There is also full four-way cursoring, as well as HOME, CLR, DEL, and INSERT keys, and the entire keyboard has auto-repeat.

Seeing It In Colour

The SMC's video display is really something, although since it's a Sony you wouldn't expect anything less from the purveyors of BETA and Walkmans. The CRT has three display modes: Character mode, Graphic display, and the Border display, which are superimposed on one another. The Character display is comprised of 8x8 dot matrix/character, 80 or 40 char. by 25 lines, and the characters can be programmed in 8 colours. The background colours can be changed and the characters can be inverse or blinking as well. The Graphic mode is broken down into four sub-modes of differing resolution and colour choice: 1) 160x100 dots - 16 colours - 4 screen pages; 2) 320x200 dots - 16 colours; 3) 640x200 dots - 4 colours; 4) 640x400 dots in the monochrome mode. The Border display gives a choice of 16 colours. All of this, when displayed through the Sony's KX-1211 HG component TV-RGB monitor, made for a very impressive presentation.

Micro Driving

The SMC-70 which was left with us was accompanied by a dual disk drive unit which accepts the new 3.5 inch, high density mini-disks, which are also in use on the Apple Mac and Lisa computers. This system, developed by Sony, is capable of storing a staggering 1 Megabyte of information on one double-sided, doubled density mini-diskette. Sony supplied us with single-sided single density disks with a capacity of 280K bytes. Also available is a cassette tape storage system, but on a machine such as this, it is highly unlikely that it would be needed for much more than simple programming applications.



CP/M

A comforting thought, when reviewing a new micro, is in knowing that it runs an operating system which is pretty well liked by 'priet' near everyone. Just pop in the CP/M system disk and you're off to the races. All the normal stuff is there: PIP, STAT, ASM, DUMP, etc. Instead of FORMAT and COPY, Sony uses a utility titled BACKUP, which lumps the two previous ones together into a menu driven utility. The SMC version of CP/M has been extended for colour and graphics applications which are superior in quality to anything on the market of late.

Software

Just as an automobile won't run without some sort of fuel in its tank, a micro is pretty much useless without sufficient supporting software. Aimed at the lower to mid-priced business level, the SMC runs a variety of packages such as: Super-Calc 1 & 2, a complete accounting package, Sony disk BASIC, CB-80 (a souped-up business BASIC for graphics, colour and sound). Data Base Management, Word Processing (WordStar, Letterwriter) with a spelling checker and mailing list option. The really big selling point for the SMC-70, though, is its graphics.

Custom Text

The three packages available are very entertaining and not extremely difficult to learn. The Video Titler package lets you


create text in three character sizes, as well as six different type faces in sixteen colours. The text created with the Video Titler can then be superimposed over a video image by interfacing the SMC-70 with a suitable video display system (eg., Sony video disc player and KX-1211 HG component TV). This was demonstrated to me at the recent Computer Fair in Toronto, and the potential for this type of display would seem to lie in the educational, industrial, and tourism sectors, just to name a few.

Disney Anyone?

Graphics Editor is a totally menu-driven package which allows the creation of full colour graphics images from the keyboard or optional graphics tablet. It sports such features as variable "zoom editing." 320x200 - 16 colour resolution and superimposition with external video equipment. All graphics are created using the five function keys positioned along the top edge of the keyboard. The commands for drawing, storing, saving, loading, overlaying, etc., are always displayed at the bottom of the screen for easy reference. A data disk supplied by Sony revealed some very colourful likenesses of Disney characters which we could change and tamper with to our heart's content. Concise and meaningful prompts lead you into the various levels of the editor. If at any time you become bogged down, you can always press the panic button (HELP key), which dumps you out to a screen help file and advises you on the correct action to take. So, at this point you think you've lost your treasured graphic creation? Nope, the SMC-70 returns you to where you were when you yelled for help. The one obvious thing which seems to be lacking, at least on a sophisticated graphics machine such as this, is a joystick for moving the cursor around. The Graphics Editor is certainly worth the look if you're thinking of graphic assisted displays for any reason.

Bars and Pies

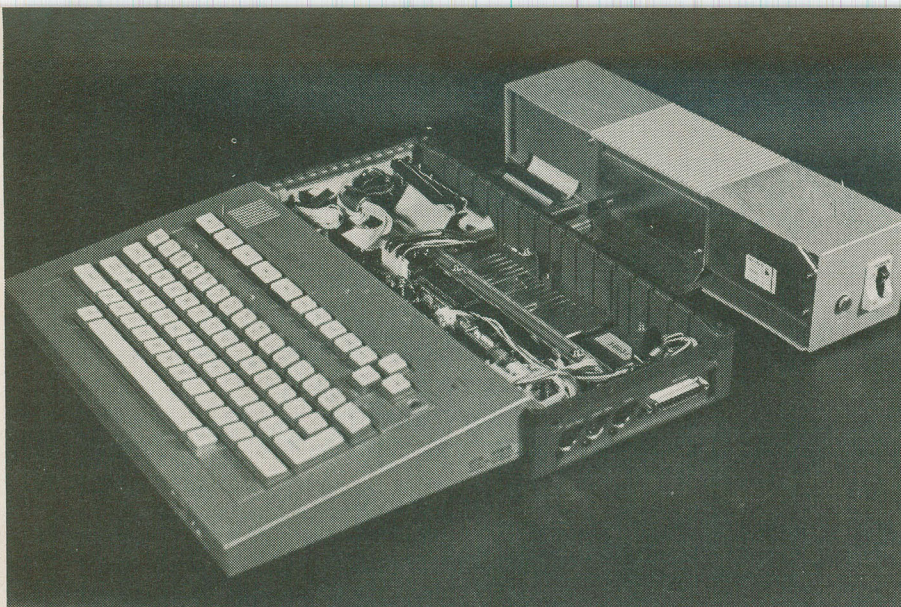Generating charts and graphs is usually a chore when the software being used is just not quite good enough. Sony's Graftalk



Computer Review

number of existing Z80 based systems, as well as Sony's reputation as a leading electronics manufacturer, the SMC-70 will probably survive the flooding market. The cost of the SMC-70 can be broken down as follows: Computer \$1895, Dual Micro-drive Unit \$1495, Printer \$1095, Trinitron Component TV KX-1211 HG \$1299, RGB and Printer cables \$90 each. CP/M and one of either the Word Processor or Data Base Management packages are included. For more information contact: Daryl Duda, Sony Marketing Headquarters, 411 Gordon Baker Rd., Willowdale Ont., M2H 2S6. (416) 499-1414.

package makes it quite simple to enter the data, title the various axes, as well as colour and label desired portions of your work. There is also the capability of using SuperCalc data with Graftalk, as well as data created with Letterwriter, eliminating the need for re-entry of lengthy data files.

End of File

After having explored the SMC-70 for a few days, it would seem that it certainly

has a future in the video graphics market. Its one strong point is that it's a CP/M based system which has very good software potential, and very good graphics capabilities which are not found on too many CP/M systems. Its ability to interface with video systems makes it attractive for presentations of all kinds. However, the era of the 8-bit micro would seem to be passing, slowly, but still passing. But given the reliability of CP/M and the

Quick Reference

Mfg:	Sony
Price:	Computer \$1895, drives \$1495
CPU:	Z80A
RAM:	64K user plus 38K video
Screen:	40 or 80 x 25
Graphics:	320 x 200
Colours:	16
Sound:	Yes
Video:	RGB

ETI

Gentek

Computers Inc.

GENTEK G2200 COMPUTER

- Apple™/CPMTM Compatible
- Dual Microprocessor Z80/6502
- 64K Ram (upgradable to 192K Ram w/128K Ram Card)
- Multi-Function detached keyboard
- Dual Disc Interface
- Complete packages available

Now available w/1 yr. Parts +
Labour Warranty Canada wide*

ACCESSORIES:

- DISC LIBRARY CASE \$29.95
- CONTROL DATA PAPER \$29.95
- MEMOREX DISCS SS/DD \$24.95

*THROUGH ESSNA SERVICE LTD.



MITAC DISC DRIVE

- APPLE II/II+/III COMPATIBLE
- 1 YR. PARTS & LABOUR WARRANTY

* UNBELIEVABLE *

\$235.00

Dealer Inquiries Invited

877 Alness St., Unit 18, Downsview, Ont. M3J 2X4

(416) 665-0234

CIRCUITRONICS

8088DC CPU	\$31.95
8237A-5 Prog. DMA Controller	\$24.50
8250B	\$19.50
8253A-5 Prog. INTRVL. Timer	\$11.95
8255A-5 P.I.A.	\$19.50
8259A Prog. Interrupt Cntrl.	\$ 9.95
8288 Bus Controller	\$18.75
8284 ADC Clock gen. and driver	\$11.85
765AC Disk Controller	\$26.50
SN75477	\$ 2.25
74LS322	\$11.50
14.3818MHZ Crystal	\$ 2.75
4.0000 MHZ Crystal	\$ 2.95
Edge card connectors 62 pin	\$ 2.95
17.43MHZ	\$ 3.25
74LS629	\$ 6.50

Remember we have all parts


In Stock

Please send certified cheque or money order Only!. All orders will be shipped C.O.D. Post Canada or add \$3.50 for postage & handling. Ontario residents add 7% P.S.T.

CIRCUITRONICS

2305 Yonge St., Suite 290 Toronto, Ontario M4P 2C7

Software Now!




FIRST
ISSUE
OCTOBER 1984

Canada's Microcomputing Software Magazine

\$2.95

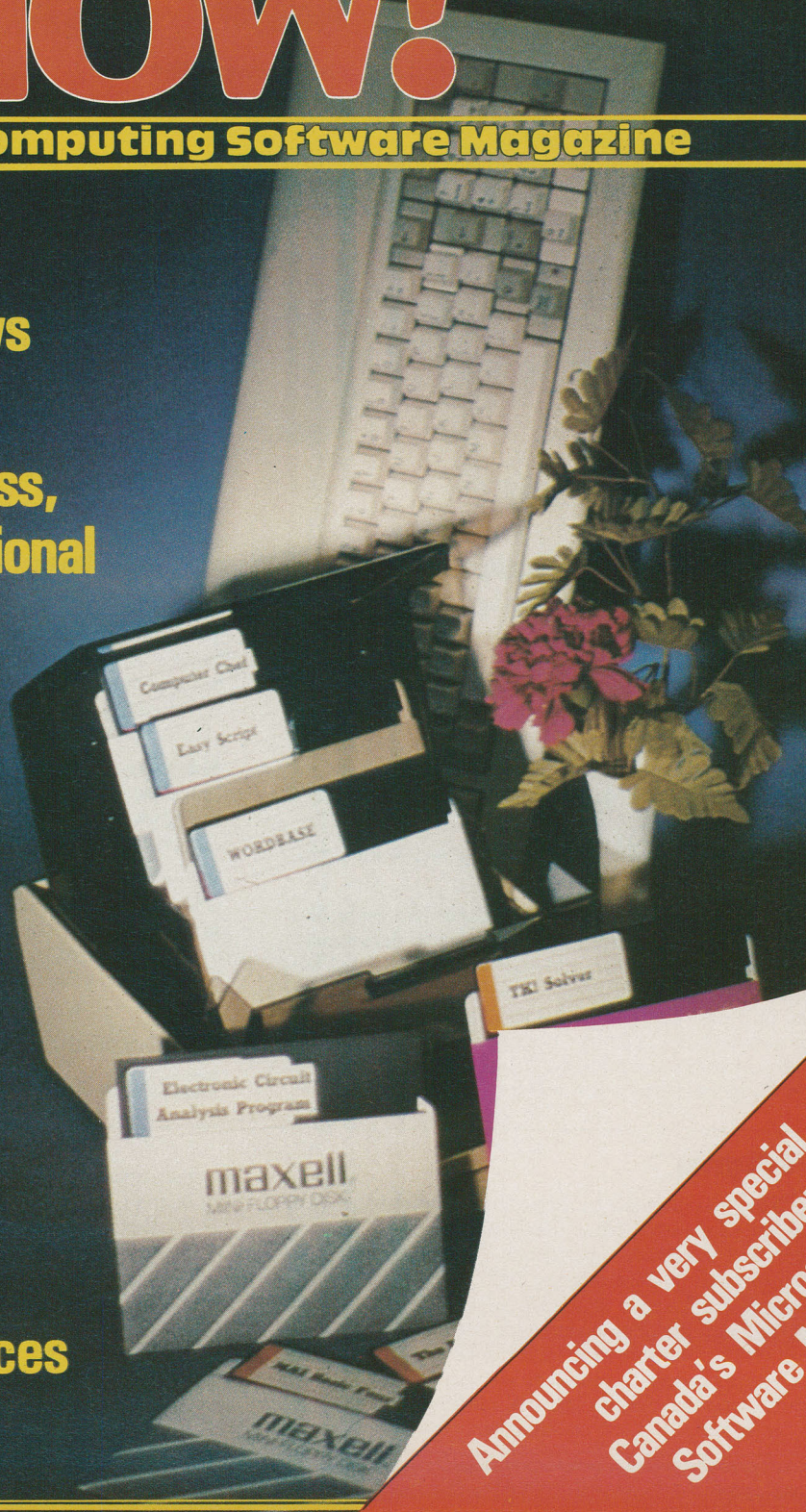- Up to the Minute Reviews
- News of Games, Business, Home, Professional and Education Packages
- Exciting New Applications
- Soft for IBM, Apple, CP/M, Commodore, Radio Shack, MacIntosh and more
- Canadian Sources



Announcing a very special offer for
charter subscribers to
Canada's Microcomputer
Software Magazine!

From The Editor.

Not knowing about software is a multiple edged sword. Not only don't you know what you need; you don't even know what you're missing. It's terribly easy to leap upon the first package that comes within waving distance of your application and then bend your application to suit it.


This is not the way it should be.

There is software for every use, perfect software for any conceivable purpose . . . but finding what you want can be a drag, if for no other reason than the constant repetition of the tune from Mission: Impossible playing inside your head.

The fabulous thing about editing a magazine like this is that you get to play with every package in the cosmos. However, this is extremely tiring . . . the fabulous thing about reading a magazine like this is that you get the benefit of being able to play with every package in the cosmos without actually having to do all that typing.

Software Now! will keep you abreast of what exists, tell you what probably shouldn't exist and inform you about where to get it so you can make it all exist for your needs.

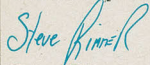We know that **Software Now!** is going to become one of the most essential accessories any computer user can own. Subscribe . . . Now! . . . and let us prove it to you.



Steve Rimmer
Editor,
Software Now!

Software Now!

First Issue October

A New Canadian Publication for the Ultimate Medium

The difference between we humans and the other inhabitants of the planet is our capacity for making tools. Civilization is often measured by its grasp of technology . . . it's through his use of tools that man has come to be able to manipulate his environment.

The computer is the ultimate tool . . . it is, like man himself, unspecific, and thus adaptable to virtually any task. The same computer can be a bookkeeper, a game, an artist's palette, a composer's amanuensis, a word processor or a programmer's development station.

The computer itself is simply a box full of chips. The power of computers lies in the software that runs on them.

Software Now! is the new magazine for people harnessing the power of the microcomputer. In its pages you will find the information which you will need to choose and apply the software that will dedicate your computer to your tasks. It will help you make sense of the myriad of similar software packages, translate the intricate complexities of software claims, understand the watershed breakthroughs in software development . . . and even have a bit of time left over to dematerialize a few aliens.

Perhaps most exciting, however, is that the pages of **Software Now!** will contain news about software for applications you've never even considered running on your computer. Imagine having an overview of the work of the world's most gifted program developers . . . and you'll have a good idea as to what this new publication is about.

Software Now! will be dealing with a broad range of systems and applications, encompassing eight, sixteen and thirty-two bit machines and software as diverse as video games, drafting systems and spreadsheets.

We've reached a level of development in microcomputer software wherein one needn't be a computer genius to apply a computer. In fact, one can operate a computer with only a bit more expertise than one needs to successfully make toast. The key that will unlock the power of your computer is the software you plug into it.

The key to that software is understanding.

The key to understanding software is Software Now!

The Pedigree

Software Now! is published by Moorshead Publications, which also brings you *Computing Now!*, *Electronics Today*, *Computers in Education* and the *Printout* newsletter. It has been producing successful magazines in Canada since 1977.

Moorshead Publications is unique in the way it produces magazines. The expertise in applying microcomputers has allowed us to make virtually the entire process of publishing electronic. The editorial in the publications is created on word processing terminals and computer type set. All the financial planning is handled by computer, as is filing and list management. The company also

maintains an on line telecommunications computer to communicate with its readers.

The Editor of **Software Now!** is Steve Rimmer, who also edits *Computing Now!* In the first year of its existence *Computing Now!* went from a standing start to having over twenty two thousand subscribers, making it Canada's largest consumer microcomputer publication.

Steve has had experience with a wide range of software, from word processors to sophisticated music and graphics packages. He uses a number of computers, including several CP/M based machines, an IBM, an Apple II+, a Commodore and a Macintosh.

are N! er 1984

Features In The Queue

This is some of the editorial we have lined up for the first few issues of Software Now! You can expect it to change a bit... new software springs up almost daily, and Software Now! will always feature the most important developments in this dynamic field. Articles being developed during the preparation for the magazine include:

Computer Aided Drafting On a Micro • Techniques in MacPaint • How to choose a Spreadsheet • Apple Software Crate • Getting to the Root of UNIX • The Digital Research Pantry • A Thousand and One Word Processors • IBM's Productivity Family • Can Mac Write? • Professional Software Roundup • Power Programs for the 64 • Approaching the C • Word Processing Support Programs • dBase II Enhancements • Will it Run Multiuser? • Concurrent CP/M •

Reviews: 10 Base • Mighty Mail • WORD-BASE • Easy Script • Computer Chef • Electronic Circuit Analysis Program • Superex Retailer • MAI Basic Four • The Print Shop • TK!Solver • Microsoft BASIC for the Macintosh • Sundog • Turbo PASCAL for the IBM • AutoCAD • MultiMate • Lexicheck and Word Juggler • Dataflex • Symphony • Omniterm 2 • DB Master • Paint Magic.

In addition to this look for these regular features:

The Library	(Our monthly survey of books)
By The Boards	(Public domain software)
Arcade	(A blast at the latest games)
Short File	(A short overview of new releases)

The Amazing Software Now! Software Disk Free to Charter Subscribers

At Moorshead Publications, we have always managed to launch new magazines with a flying start; this time we want our previous records to be smashed. We believe we have come up with "an offer you can't refuse".

The **Amazing Software Now! Program Disk** is, we believe, the best offer ever made to Charter Subscribers to a new magazine. A charter subscriber is one who helps provide the initial circulation base and we feel they deserve something special — what we are offering is just that.

The disk contains some fairly amazing custom written material:

- CalcNow:** A real spreadsheet program with many as the new features of programmes costing a small fortune. CalcNow is perfect for those who want to experiment with a spreadsheet and are dying to see how they work. It is far from a toy.
- DataBox:** A flexible data base manager and is a version of a program we developed for our own company use.
- Poker:** Life is not complete without a video game.
- Phone Jack:** A telecommunications terminal.

The contents of the disks vary depending on the system and additional programs come for some systems: see overleaf for a more complete description.

The **Software Now! Disk** is available in a huge number of different formats but we haven't forgotten you if you haven't got a disk drive or a system that we can accommodate: everyone will also receive a hard copy listing of those programs written in BASIC (listed for Microsoft Basic for you to modify yourself).

This disk will be sent to you **FREE** if we get your subscription order **before September 30th, 1984**. Early orders will get their disks as soon as processing and shipping time allow, later orders will receive them with the first copy of the magazine.

The **Software Now! Disk** is not available at this time **EXCEPT** to **Software Now! Charter Subscribers**. The software is currently in the final stages of development but we must reserve the right to modify the content.

Software Now! is available at a charter rate of **\$19.95** for a one year subscription, **\$34.95** for two years. This rate is valid until September 30th, 1984. This rate includes your choice of a free software disk... please specify the machine operating system and format you want the disk to run with: check those available.


Software Now! Subscriptions
25 Overlea Boulevard Suite 601
Toronto, Ontario
M4H 1B1

YOUR GUARANTEE

If you do decide that Software Now! is not the magazine you expected or want, or if you decide to cancel your subscription for any reason or no reason, you may do so and receive a refund on the unexpired portion at any time.

If, however, you cancel before receiving your THIRD issue, we will issue a complete refund. Charter Subscribers receiving the Software Disk as part of their subscription will have just \$3.00 deducted for the raw cost of the disk.

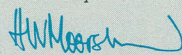This guarantee is backed by the full resources of Moorshead Publications. Any refund will be made promptly and cheerfully.



H.W. Moorshead
President

**Be a Charter Subscriber:
Save up to 50% and get your Free
Software Now! Disk**

Advertising

For details on advertising in Software Now!,
Call our Advertising
Department: (416) 423-3262.

The Amazing Software Now! Bonus Disk

The programs available on the disks are as follows:

	A	B	C	D	E	F	G
1/	(1)	Resin	(1979)	PLA/Path	PLA/DI	Ua-Tr	Ua-HLS
30	PS TOTS/GONES				20		
31	PS IAU HOLD NES		4			137	1.26
32	PS (PreF125 B Field Mac)		27.50			137	1.50
33	PSFORM Egg GONES		7.50				
34							44
35	PSFORM BODKHS		6.70				
36	PSFORM SCHEATING		5.80				
37	PSFORM EXTRA NES		5.80				
38	(PreF118 B Extra Foam)			18.00			
39	PSFORM INSULATION		16.00				
40	EPS HOT-DRINK CUPS		3.00				
41	EPS PROX. SHAPES		3.30				
42	EPS (PreF25 B EPS Foam)			25.00			
43	CHUCKLES FLOOR MOPS					1	0
44							
45	Total PS	126.30			16	1833	15
46	Resin experts	12.30			17	1833	2
47	Actual net totals	126.30				38	16/2
48							0.7
D46	P Form=SUM(D1-D44)						

```

ITEM ENTRY PAGE
-----
Record number [ 2 ]

Name of Item: [VIC 20 PROGRAMMER'S REFERENCE GUIDE ]
Supplier's Code: [VM118 ]
Internal Code: [C081 ]
Retail Price: [23 50 ]
Our Cost: [20 00 ]
Profit Per Item: [3 50 ]
Maximum Inventory: [25 ]
Current Inventory: [19 ]
Minimum Inventory: [15 ]

Enter , New page or Abort: [E]

```

POKER				
xc	0c	10c	17c	9c
xc	0c	0c	7c	9c

I'll see you and raise \$100.

CalcNow

CalcNow is a fully capable spreadsheet package. It can manage a sheet sixteen columns across by twenty six rows deep. It allows for automatic and manual recalculation, full cursor movement, formulae, constants and labels, disk storage of your sheets and a full hard copy reporting function. Its syntax and behavior is very much like that of the popular packages and for models of the size usually used in small business and personal financial planning it's equivalent to professional . . . and very much more expensive . . . spreadsheet packages.

Phone Jack

Most computers have telecommunications hardware built into them . . . it's a shame that they don't all have software available to drive it. This program does basic telecommunications and, while its features do vary a bit from system to system . . . based on what the operating systems allowed us to implement . . . it does provide for the basic requirements of calling computer bulletin boards and dial up mainframes.

Utility Pack

Most revisions of the disk will also have a choice selection of utility programs. These vary a lot from system to system so it's a bit difficult to describe them all here. However, these are the little routines that make life so much easier when you sit down at the keyboard and switch on.

DataBox

Many commercial data base managers are extremely powerful, extremely expensive and, in fact, grossly over qualified for most tasks. DataBox can handle most of their routine tasks that data base managers are bought for. It is efficient of disk space, reasonably fast and very, very flexible. It can keep track of your files, your stock . . . or even your record collection. It features variable fields, hard copy reporting and flexible search parameters.

These programs will vary a bit from system to system . . . the following outlines the formats in which we can supply this software. You will need your own Microsoft compatible suitable BASIC Interpreter (e.g. GWBASIC, BASIC-80, MBASIC, APPLESOFT, RS BASIC, PET BASIC, Microsoft MacIntosh BASIC etc.)

For CP/M* users: CalcNow, DataBox, Poker!, Utility Pack, Phone Jack

For Apple II +DOS Users: CalcNow, Databox, Poker!, Phone Jack, Utility Pack plus Clef Hanger (An Apple Music Box), Skyhook (a teletype converter) and Fruit Crate (a BBS).

For IBM Users: CalcNow, Databox, Poker!, Utility Pack, Phone Jack plus Bandit (A slot machine simulator)

For Macintosh Users: CalcNow, Databox, Poker, Phone Jack and Letterhead (a stationary generator).

For Commodore Users: CalcNow, Databox, Poker, Utility Pack and Phone Jack.

For TRS-80 Model III and 4: CalcNow,
Databox, Poker

Poker!

We wanted to include a game on the disk and, after some deliberation decided that a good dimly lit, smokey card game would fill the bill best. This one simulates five card draw poker in the proper cowboy style. It can deal, draw, call, bet . . . do everything but cheat and pull its six gun on a really bad hand. POKER! features a graphic display of the cards being played.

This software is available as a free gift to charter subscribers to Software Now! magazine. To be eligible to receive this disk your subscription order must be at our offices no later than September 30th, 1984.

* Available for Apple CP/M, Osborne single and double densities, Access Matrix, Kaypro II, Lobo max 80, Morrow Micro Decision, Olympia single and double, Superbrain, Systel/Olympia, DEC VT-180, Nelma Persona, Xerox/Cromemco, 3R Avatar, Casio FP-1000, Epson QX-10VD, Attache, Micromate, if800, Sanyo MBC 1000, Televideo, Zorba and on eight inch single sided single density disk.

I'd like to become a Charter Subscriber to Software Now! and receive my Amazing Software Now! program disk.

☐ **One year (12 issues) for \$19.95**

☐ **Two years (24 issues) for \$34.95**

Name _____

Address _____

City _____ Province _____ Post Code _____

☐ **Cheque enclosed**☐ **Bill my Credit Card (Visa, Mastercard, American Express)**

No. _____ Expiry Date _____

☐ Bill me (we are happy to bill you but you will NOT qualify for a Software Now! program disk).

Please specify the format you want for your disk
Offer expires September 30th, 1984.

**Mail to: Software Now! Subscriptions,
Moorshead Publications, 25 Overlea Blvd., Suite 601, Toronto, Ontario M4H 1B1.**

**Please Specify
Your Disk Code as follows:**

APP	Apple II + DOS
IBM	IBM PC
MAC	Macintosh
TRS	Radio Shack Models 3 & 4
CBM	Commodore Disk formats
ACP	Apple CPM
OS1	Osborne Single Sided
OS2	Osborne Double Sided
AMT	Access Matrix
KAY	Kaypro
LOB	Lobo max BO
MOR	Morrow Micro Decision
OL1	Olympia Single sided
OL2	Olympia Double sided
SBR	Superbrain
SYS	Systel/Olympia
DEC	DEC VT-180
NEL	Nelma Persona
XER	Xerox/Cromenco
3RA	3R Atavar
CAS	Casio FP-1000
EPS	Epson QX-10VD
ATT	Attache
MIC	Micomate
SAN	Sanyo MBC 1000
TEL	Televideo
ZOR	Zorba
IF8	IF800
8"	8" Disk Single Sided, Single Density

Machine Language

Part 2

In this second part of this series, Bob Bennett looks for implied and immediate addresses on the computer's memory map.

WHEREABOUTS in RAM your machine code program will go depends on the memory structure of your computer. A look at the computer's memory map will show the areas in RAM reserved by the computer for 'housekeeping' duties. These duties consist of keeping tabs on everything that happens while the computer is switched on. Figure 5 shows a portion of a memory map for no computer in particular; how it works is fairly simple, but does require a lengthy explanation.

The *display file* is shown as occupying 704 addresses, each of one byte: these 704 bytes store information relating to the picture on the screen. The working area of the screen in our example consists of 32 columns by 22 rows, and 32 times 22 equals 704. The reason I referred to working area is that there are usually two rows at the bottom of the screen reserved for the input data. As a rule the top left hand corner of the screen is position 0,0, and this is the first address in the display file. Suppose that you printed the letter A in position 0,0: the code for letter A would be stored in address 16384.

The *print buffer* is merely a temporary storage area for data going out to a printer, but this area can often be used by the programmer.

Any good computer handbook has a section devoted to the *system variables*, which are a series of reserved addresses usually given short names. These addresses contain information, dealing with which comprises the major portion of the housekeeping I mentioned before. Each system variable consists of one, two, or very rarely, three or more bytes. If there is only one byte then the address will usually contain a number, the value of which may determine the action to be taken by the computer.

If there are two bytes, then the two consecutive addresses of the system variable themselves hold an address. This

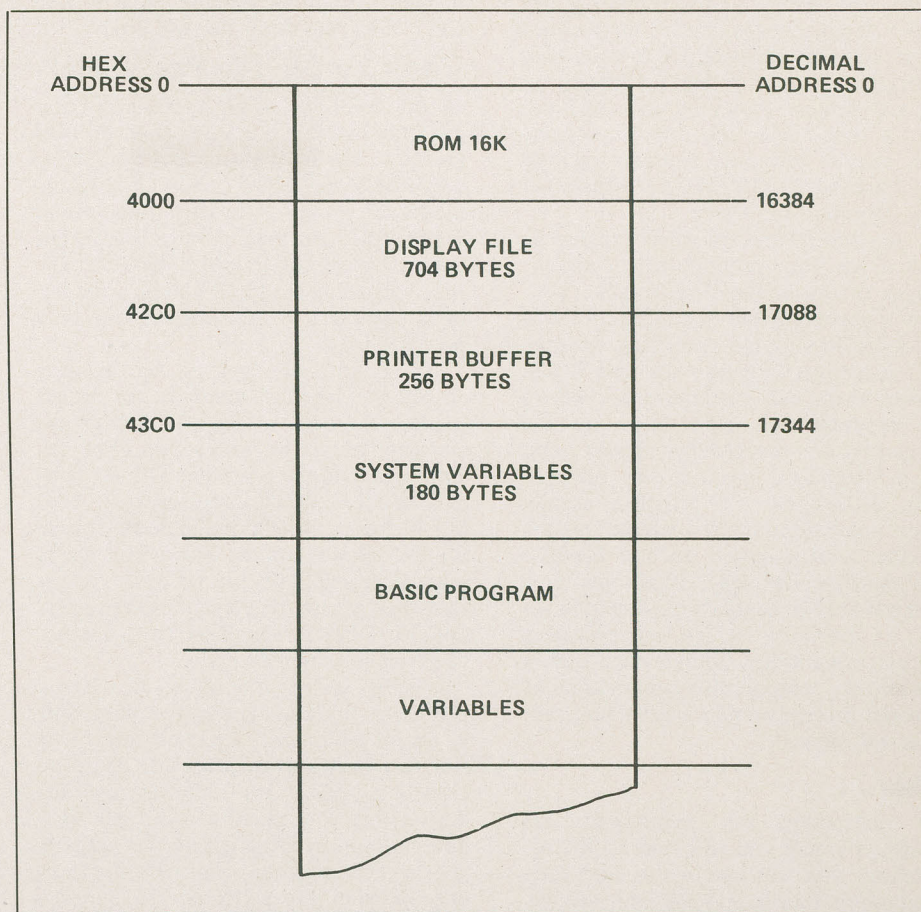


Fig. 5 Portion of generic memory map.

is usually the starting address of an area in RAM where a particular variable is stored. For example, when you assign letters or strings as variables, the information relating to those variables is held in an area of memory. If you had a system variable called VARS, this would consist of two bytes, and would hold the starting address of that area.

The area of RAM, from the system variables onwards, is the part that is of primary interest to machine code programmers. As your list of variables is added to, or subtracted from, then the area it occupies can fluctuate. This is true of the area taken up by your BASIC program, as you add or delete lines. Areas in RAM can be reserved for machine code programs, and there is usually plenty of information around telling you how to do it for your particular computer.

How . . .

Once you have found out where to put your program, the next task is to get it there! There is really only one way it can get there, but there are several methods of doing it (that's a bit like saying 'there is only one road to Rome, but there are many means of transportation'). The program is POKEd into addresses, byte by byte. Starting with the first address, and the first byte, the addresses are incremented after each POKE.

If you're not familiar with POKE, it's how you get information into RAM. Consider this example of a direct command, POKE 32000,119 decimal: this means place the decimal number 119 into address 32000. If your computer allows you to use hex direct, then the command could be POKE 32000,77 hex. The com-

plementary command to POKE is PEEK, so, after entering the above example, the instruction PEEK 32000 would cause the number 119 decimal to be printed to the screen. Of course, you can only POKE information in RAM, but you can PEEK at either RAM or ROM.

Probably the most widely used method of entering machine code programs into home micros is with a hex loader. If your micro doesn't support hex direct, then the hex code has to be entered as a string, sliced and then converted to decimal before POKEing into the addresses. Otherwise, the decimal conversion can be left out. Another method might use the READ/DATA statements if your computer has them.

Assemblers and compilers can also be used to get your program into memory. Taking the assembler first, this is a program that could either be resident in ROM or loaded in via tape, etc. This will take your assembler language statements and convert them into machine code. Before the program can run, however, the statements are checked for validity, and an opportunity is given to edit the program. A compiler is a program, usually loaded into the computer, which converts a higher level language, such as BASIC, into machine language. If the last two methods have to be loaded in then they do use up memory, which is usually a precious commodity. So how the program gets into the computer is a combination of personal preference and what your computer will support.

What . . .

The instruction set, mentioned last month, is where you will find all the instructions you will use in machine code programming. Ideally they will be in tabular form, giving both decimal and hexadecimal notation, and sometimes you

might find the binary form given as well. Also they should include the assembler mnemonics, and the number of bytes per instruction. Those of you with Sinclair micros have everything that you need, apart from the byte count, in the handbook. Because the instruction set for the Z80 is very comprehensive I will be using that for the examples I give. Don't worry if your computer doesn't have a Z80 CPU, the same principles will apply.

Don't Forget The Post Code!

Before very long 16-bit micros will be as common in the home as the eight-bit ones are now, but until then I will be dealing only with the eight-bit variety. Addressing modes are simply a way of getting around the fact that addresses require 16 bits, but our data word is only eight bits long. The first addressing mode I'll explain is the implied because it is the simplest, and only one byte long.

Sometimes known as the register direct, the *implied mode* is so named because the data source and destination are implied in the instruction. For example, to load the B register with the contents of the C register requires the instruction 41 hex in the Z80 set. Here the source is the C register and the destination, the B register; this could be shown as C B. Incrementing and decrementing registers, and No Operation and RETURN instructions use the implied mode.

NOP, or no operation, is self explanatory, nothing happens (nothing, that is, except a fractional waste of time). This is a very useful instruction that could be used in a timing loop, or to occupy addresses that you intend to overwrite with data later on in the program. Or perhaps you haven't quite decided what to do in one patch of the program. An approximate number of NOPs will reserve the space for you until you have made up

your mind. As for the RETURN, this is perhaps the most important instruction you will use. Without it, in some computers, you could be stuck in an infinite loop. In its simplest form, it can be regarded as an instruction to return to the place from where you were sent — more will be explained later.


All simple register to register transfers use the implied mode, but as an exercise see how many of these instructions you can find in your set. The golden rule is that there is one byte in the whole instruction.

For Your Immediate Attention


The immediate mode is the next easiest addressing mode that you can use. As with the implied, the immediate mode does not involve any addresses, but there are now two bytes per instruction. The instruction 3E hex in the Z80 set means load register A with the number that follows; in the 6502 set the same instruction would be A9 hex. This might have the mnemonic Ld A,n, or M A, or even MV1 A,D8; note that the names are not CPU instructions; they are just humanised memory aids. That last mnemonic sums everything up nicely because it means, move immediate(ly) into A a data byte of eight bits. Other instructions of this type include add n to a particular register or subtract n from a particular register. Again as an exercise, pick out all the immediate mode instructions out of your set.

Now that we have reached two byte instructions, I'd like to clear up a point that seems to confuse newcomers to machine code programming. The idea that the same byte can represent two different things might seem at first glance to be perplexing, but stop and think. Let me take as an example the instruction above, load A with n. This could be written in a Z80 program as 3E,3E (or for the 6502, A9,A9). What happens is that when the computer gets to the first 3E it regards it as an instruction, an instruction to load the byte that follows (which also happens to be 3E) into register A. What the second number stands for is up to you, as the programmer, to decide. It may be just a number you want to manipulate, or it could be the code of a character you want to print to the screen. Whatever, the computer recognized the first 3E (or A9), as an instruction requiring two bytes. After carrying out that instruction, the computer would carry on with the rest of the program from the instruction which came after the second byte. Every instruction belongs to a class that requires one, two, or more bytes for proper execution. It is the programmers responsibility to ensure that the computer starts off in the right place!

ETI

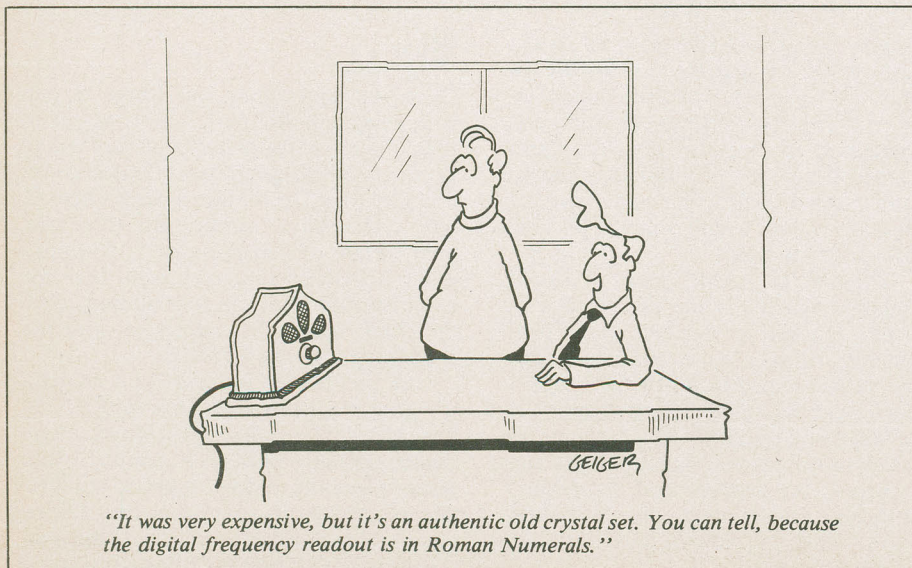

computing today

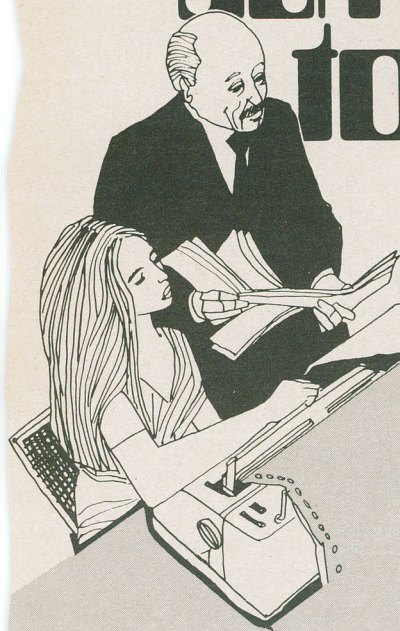

6502 Utilities

Even though manufacturers have been producing microprocessors with thirteen digit names for years now, the 6502 is still a programmer's favourite. Three programs are listed below to give your fingers some practice. You'll also learn why the chips in your computer try to crawl out of their sockets at night...

by John Rudzinski

AT around six-thirty in the morning, after watching the obligatory morning cartoons, a select breed of professional worker goes to work in Silicon Valley, U.S.A. Grabbing a quick coffee and a wicker basket, these hard workers trod into the fields to begin their backbreaking occupation.

Chip picking.

In the summer months, the chiptrees blossom. Branches bend with bough-breaking clusters of TTL, op-amps, encoder-decoders, and microprocessors. When ripe, the chips fall — feet earthward — to the ground where the chip-pickers stoop to collect them.

The oddballs on the chiptrees fall upside down, feigning death in hope of escaping unseen under cover of darkness. This is to be expected of the inverting amplifiers, but seems unusual for the TTL... the so-called logic chips.

The favourite fruit of the chiptree, however, is the 6502 microprocessor. Admittedly, it's nothing fancy... what with an eight-bit accumulator, two eight-bit index registers, an eight-bit stack pointer and a sixteen-bit program counter, it's fairly archaic as opposed to some of the monsters that've been skittering out from Intel and MOS Technology these days. Still, it's a remarkably easy chip to both understand and program, which is why it remains a favourite today.

Quickies

The three short assembly programs that follow are written for the Apple II+ computer or similar abomination. There's a

reason for this... it's the only micro I have.

I used to have a VIC-20, but I'm okay now.

Program One, *Password Protection*, isn't actually a program... it's a subroutine to a program that you have to supply. It might prove useful in a disk pre-boot situation where you don't want Russian spies diddling with your data. When BRUN, it lets potential perpetrators know that your program is protected, and they're to supply a password before anything useful will happen. If, in this case, "BLA-AT", (the sound of an unhappy disk drive) isn't typed in, the program will gleefully erase itself from memory.

Naturally, you're free to replace the password with any six letter word that strikes your fancy. Be careful to BSAVE before you BRUN it... backspaces are considered valid characters as well.

If you've spent hours looking around for a chart to find the hexadecimal equivalents of a number of keyboard characters, you might get a kick out of Program Two. Comprised of 262 bytes, it will inhale a string or strings of up to 255 bytes rattled off the keyboard, ponder the meaning of life for a few moments, then spew out the hex. Before I obtained a sympathetic assembler, I always had to look each character up in a table, then jam them individually into memory to display whatever string I wanted to convince to burn CRT phosphor.

Hitting a Control-C will tell the program you've finished your input unless you type over the 255 character limit. It gets somewhat violent should this happen and lays the hex on you unrequested. You just can't convert a novel to hex with a 262 byte program.

```
:ASM
1 *****
2 *
3 *   PASSWORD PROTECTION
4 *
5 *   (C) 1984 - J. RUDZINSKI
6 *
7 *****
8 *
9 *   ORG $0800
10 *
11 BUF EQU $2000
12 CLS EQU $FC58
13 GET EQU $FD35
14 PRINT EQU $FDEB
15 C/R EQU $FDBE
16 BASIC1 EQU $E000
17 *
18
19 0800: 18      18  FIND  CLC
20 0801: 90 2F  19      BCC  BEGIN
21 0803: C2 CC C1 20  PASS  ASC  "BLAAT"
22 0809: D4 C8 C9 21  STR1  ASC  "THIS PROGRAM PROTECTED."
23 0810: 8D      22      DB  #$8D
24 0811: 8D      23      DB  #$8D
25 0822: C5 CE D4 24  STR2  ASC  "ENTER PASSWORD: "
26 0832: 20 58 FC 25  BEGIN  JSR  CLS
27 0835: A2 FF 26      LDX  #$FF
28 0837: E8      27      INX
29 0838: E0 29 28      CPX  #$29
30 083A: F0 09 29      BEQ  PASSGET
31 083C: BD 09 08 30  LDA  STR1,X
32 083F: 20 ED FD 31  JSR  PRINT
33 0842: 18      32      CLC
34 0843: 90 F2 33      BCC  XLOOP1
35 0845: A2 FF 34      PASSGET LDX  #$FF
36 0847: E8      35      XLOOP2 INX
37 0848: E0 06 36      CPX  #$06
38 084A: F0 1E 37      BEQ  RIGHT
39 084C: 20 35 FD 38  JSR  GET
40 084F: 48      39      PHA
41 0850: A9 D8 40      LDA  #$D8
42 0852: 20 ED FD 41  JSR  PRINT
43 0855: 68      42      PLA
44 0856: DD 03 08 43  CMP  PASS,X
45 0859: D0 3B 44      BNE  DYE
46 085B: 18      45      AROUND CLC
47 085C: 90 E9 46      BCC  XLOOP2
48 085E: 8D      47      STR3  DB  #$8D
49 085F: D9 CF D5 48  RIGHT  ASC  "YOUR PROGRAM STARTS HERE..."
50 087A: 20 8E FD 49  RIGHT  JSR  C/R
51 087D: A0 00 50      LDY  #$00
52 087F: CC 95 08 51  CPY  DATA
53 0882: D0 18 52      BNE  WIPE
54 0884: A2 FF 53      LDX  #$FF
55 0886: E8      54      XLOOP3 INX
56 0887: E0 1C 55      CPX  #$1C
57 0889: F0 09 56      BEQ  END
58 088B: BD 5E 08 57  LDA  STR3,X
59 088E: 20 ED FD 58  JSR  PRINT
60 0891: 18      59      CLC
61 0892: 90 F2 60      BCC  XLOOP3
62 0894: 60      61      RTS
63 0895: 00      62      DATA DB  #$00
64 0896: 8E 95 08 63  BYE  STX  DATA
65 0899: 18      64      CLC
66 089A: 90 BF 65      BCC  AROUND
67 089C: A9 BF 66      LDA  #$BF
68 089E: A2 FF 67      LDX  #$FF
69 08A0: E8      68      XLOOP4 INX
70 08A1: E0 96 69      CPX  #$96
71 08A3: F0 06 70      BEQ  END1
72 08A5: 9D 00 08 71  STA  FIND,X
73 08A8: 18      72      CLC
74 08A9: 90 F3 73      BCC  XLOOP4
75 08AB: 4C 00 E0 74  JMP  BASIC1
76
77 --- END ASSEMBLY ---
78
79 TOTAL ERRORS: 0
```


Computing Today

My favourite creation is Program Three. Entitled *Subliminal Advertising*, it's the shortest of the three listings at 111 bytes. It's a bit odd in that it appears to simply ask a question and then wait for your input. What it's actually doing is laying in wait for a victim to answer its query. No matter what is typed, one of ETI's sister publications shows up on the screen, one character at a time, in response to each keypress.

The public has a right to know.

```

:ASM
1 *****
2 *
3 * STRING INPUT AND HEX
4 *
5 * CONVERSION
6 *
7 *****
8 *
9 * ORG $0800
10 *
11 BUF EQU $2000
12 CLS EQU $FC58
13 GET EQU $FD35
14 THEX EQU $FDDA
15 PRINT EQU $FDEB
16 C/R EQU $FDEE
0800: 4C 22 08 17 JMP BEGIN
0803: C5 CE D4 18 STR1 ASC "ENTER STRING. HIT AC WHEN DONE."
0822: 20 58 FC 19 BEGIN JSR CLS
0823: A0 FF 20 LDX #FFF
0827: C8 21 YLOOP1 INY
0828: C0 1F 22 CPY #51F
082A: F0 09 23 BEQ ENTER
082C: B9 03 08 24 LDA STR1,Y
082F: 20 ED FD 25 JSR PRINT
0832: 18 26 CLC
0833: 90 F2 27 BCC YLOOP1
0835: 20 8E FD 28 ENTER JSR C/R
0838: 20 8E FD 29 JSR C/R
083A: A2 FF 30 LDX #57F
083D: E8 31 XLOOP1 INX
083E: E0 FF 32 CPX #5FF
0840: F0 25 33 BEQ TSTRING
0842: 20 35 FD 34 GRAB JSR GET
0845: A8 35 TAY
0846: C0 83 36 CPY #483
0848: F0 1D 37 BEQ TSTRING
084A: C0 88 38 CPY #488
084C: F0 09 39 BEQ BSPACE
084E: 90 00 20 40 STA BUF,X
0851: 20 ED FD 41 JSR PRINT
0854: 18 42 CLC
0855: 90 E6 43 BCC XLOOP1
0857: 20 ED FD 44 BSPACE JSR PRINT
085A: A9 A0 45 LDA #A0
085C: 20 ED FD 46 JSR PRINT
085F: A9 88 47 LDA #88
0861: 20 ED FD 48 JSR PRINT
0864: 18 49 CLC
0865: 90 DB 50 BCC GRAB
0867: 8A 51 TSTRING TXA
0868: 48 52 PHA
0869: 20 8E FD 53 JSR C/R
086C: 20 8E FD 54 JSR C/R
086F: 18 55 CLC
0870: 90 10 56 BCC NOTE
0872: C1 CE C4 57 STR2 ASC "AND NOW, IN HEX:"
0874: A0 FF 58 NOTE LDX #5FF
087A: C8 59 YLOOP2 INY
0885: C0 11 60 CPY #511
0887: F0 09 61 BEQ CONVERT
0889: B9 72 08 62 LDA STR2,Y
088C: 20 ED FD 63 JSR PRINT
088F: 18 64 CLC
0890: 90 F2 65 BCC YLOOP2
0892: 20 8E FD 66 CONVERT JSR C/R
0895: 20 8E FD 67 JSR C/R
0898: 18 68 CLC
0899: 90 01 69 BCC SKIP
089B: 00 70 DATA BRK
089C: 68 71 SKIP PLA
089D: 80 9B 08 72 STA DATA
08A0: A2 FF 73 LDX #5FF
08A2: E8 74 XLOOP2 INX
08A3: EC 9B 08 75 CPX DATA
08A6: F0 0E 76 BEQ END
08AB: BD 00 20 77 LDA BUF,X
08AD: 20 DA FD 78 JSR THEX
08AE: A9 A0 79 LDA #A0
08B0: 20 ED FD 80 JSR PRINT
08B3: 18 81 CLC
08B4: 90 EC 82 BCC XLOOP2
08B6: 18 83 CLC
08B7: 90 0D 84 BCC CHOICE
08B9: CD CF D2 85 STR3 ASC "MORE? (Y/N): "
08C6: 20 8E FD 86 CHOICE JSR C/R
08C9: 20 8E FD 87 JSR C/R
08CC: A2 FF 88 LDX #5FF
08CE: E8 89 XLOOP3 INX
08CF: E0 0D 90 CPX #50D
08D1: F0 09 91 BEQ YESNO
08D3: BD 99 08 92 LDA STR3,X
08D6: 20 ED FD 93 JSR PRINT
08D9: 18 94 CLC
08DA: 90 F2 95 BCC XLOOP3
08DC: 20 35 FD 96 YESNO JSR GET
08DE: AA 97 TAX
08E0: E0 D9 98 CPX #5D9
08E2: D0 15 99 BNE BYE
08E4: A9 D9 100 LDA #5D9
08E6: 20 ED FD 101 JSR PRINT
08E9: A9 C5 102 LDA #C5
08EB: 20 ED FD 103 JSR PRINT
08EE: A9 D3 104 LDA #D3
08F0: 20 ED FD 105 JSR PRINT
08F3: 20 8E FD 106 JSR C/R
08F6: 4C 22 08 107 JMP BEGIN
08F9: A9 CE 108 BYE LDA #CE
08FB: 20 ED FD 109 JSR PRINT
08FE: A9 CF 110 LDA #CF
0900: 20 ED FD 111 JSR PRINT
0903: 60 112 RTS
0904: 00 113 BRK
0905: 00 114 BRK
--- END ASSEMBLY ---
TOTAL ERRORS: 0
262 BYTES GENERATED THIS ASSEMBLY

```

```

:ASM
1 *****
2 *
3 * SUBLIMINAL ADVERTISING
4 *
5 * (C) 1984 - J. RUZINSKI
6 *
7 *****
8 *
9 * ORG $0800
10 * CLS EQU $FC58
11 * GET EQU $FD35
12 * PRINT EQU $FDEB
13 * C/R EQU $FDEE
14 *
15 *
16 * JSR CLS
17 * CLC
18 * BCC QUERY
19 * STR1 ASC "WHAT IS YOUR FAVORITE COMPUTING?"
20 * DB #8D
21 * ASC "MAGAZINE? "
22 * QUERY LDX #5FF
23 * XLOOP1 INX
24 * CPX #2A
25 * BEQ ANS
26 * LDA STR1,X
27 * JSR PRINT
28 * CLC
29 * BCC XLOOP1
30 * STR2 ASC "COMPUTING NOW! MAGAZINE."
31 * ANS LDX #5FF
32 * XLOOP2 INX
33 * CPX #18
34 * BEQ END
35 * JSR GET
36 * LDA STR2,X
37 * JSR PRINT
38 * CLC
39 * BCC XLOOP2
40 * JSR C/R
41 * RTS
0800: 20 58 FC 16 ANS
0803: 18 17 CLC
0804: 90 2A 18 BCC QUERY
0806: D7 C8 C1 19 STR1 ASC "WHAT IS YOUR FAVORITE COMPUTING?"
0825: 8D 20 DB #8D
0826: CD C1 C7 21 STR2 ASC "MAGAZINE? "
0830: A2 FF 22 QUERY LDX #5FF
0832: E8 23 XLOOP1 INX
0833: E0 2A 24 CPX #2A
0835: F0 21 25 BEQ ANS
0837: BD 06 08 26 LDA STR1,X
083A: 20 ED FD 27 JSR PRINT
083D: 18 28 CLC
083E: 90 F2 29 BCC XLOOP1
0840: C3 CF CD 30 STR2 ASC "COMPUTING NOW! MAGAZINE."
0843: A2 FF 31 ANS LDX #5FF
0845: E8 32 XLOOP2 INX
084B: E0 18 33 CPX #18
084D: F0 0C 34 BEQ END
084F: 20 35 FD 35 JSR GET
0852: BD 40 08 36 LDA STR2,X
0855: 20 ED FD 37 JSR PRINT
0858: 18 38 CLC
0859: 90 EF 39 BCC XLOOP2
0862: 20 8E FD 40 END JSR C/R
086E: 60 41 RTS

```

--- END ASSEMBLY ---

TOTAL ERRORS: 0

111 BYTES GENERATED THIS ASSEMBLY

Escape

Night falls with a hushed thud, and the crickets rub their legs together in anticipation. The pickers have gone home to their respective basement apartments and the lights in the deserted factory hum endlessly to an absentee audience.

Crawling out from under a dandelion carcass, a 74LS02 stretches its fourteen silvery legs, peers carefully through the grass, then:

The gunshot report cracks through the still air, and the newly-ventilated chip does an inspired air dance before landing at the feet of the poacher.

"Poor little runt," he muses, dropping the deceased into a sack full of its brethren.

He lifts the sack over his shoulder and begins his walk home. It's been a good haul. There'll be chips with the fish tonight.

ETI

Where to Buy



Digital / Analog Multimeters

Fluke 70 Series Digital/ Analog multimeters are available in Canada through the Jet Stock program of Allan Crawford Associates Ltd., or from the following distributors:

Vancouver, B.C.

R.A.E. Industrial Electronics Ltd. 291-8866
Instrument Service Laboratories Ltd. 278-4511

Victoria, B.C.

Queale Electronics Ltd. 388-6111

Nanaimo, B.C.

Queale Electronics Ltd. 758-8166

Vernon, B.C.

Interior Electronics Ltd. 545-2394

Kelowna, B.C.

Interior Electronics Ltd. 860-0585

Kamloops, B.C.

Interior Electronics Ltd. 374-5002

Edmonton, Alta.

Cardinal Industrial Electronics Ltd. 483-6266
Instrument Service Laboratories Ltd. 463-7488

Calgary, Alta.

Cardinal Industrial Electronics Ltd. 259-6817

Regina, Sask.

Radio Supply & Service Ltd. 352-8642

Winnipeg, Man.

Wes Electronics Ltd. 632-1260

London, Ont.

C.M. Peterson Co. Ltd. 434-3204

Toronto, Ont.

Electro Sonic Inc. 494-1555
C.M. Peterson Co. Ltd. 247-5437
Armatek Controls Ltd. 251-3111
EIL Instruments Canada Ltd. 624-6660

Peterborough, Ont.

Weesco-Peterborough 745-2493

St. Catharines, Ont.

C.M. Peterson Co. Ltd. 685-7377

Kitchener, Ont.

C.M. Peterson Co. Ltd. 745-0981

Sarnia, Ont.

C.M. Peterson Co. Ltd. 344-3382

Windsor, Ont.

C.M. Peterson Co. Ltd. 253-1161

Hamilton, Ont.

C.M. Peterson Co. Ltd. 528-0151

Thunder Bay, Ont.

C&F Electronic Distributors Ltd. 345-6515

Sudbury, Ont.

Sonic Northern Ltd. 674-0764

Timmins, Ont.

Sonic Northern Ltd. 264-1228

Sault Ste. Marie, Ont.

Sonic Northern Ltd. 254-1418

Ottawa, Ont.

Electronic Wholesalers Ltd. 746-4413

Montreal, Que.

Electronic Wholesalers Co. Ltd. 769-8851
Franklin Electric Canada Ltd. 341-6260

Chicoutimi, Que.

Franklin Electric Canada Ltd. 545-8313

Noranda, Que.

Simtronique Inc. 762-1874

Halifax/Dartmouth, N.S.

Weesco-Maritimes 465-3730

St. John's, Nfld.

Rideout Tool & Supply Ltd. 745-2240

The Digital vs. Analog battle is over.

\$125* buys you the new champion. **The new Fluke 70 Series.**

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

So call for more information.

FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.



Fluke 73

\$125*
Analog/digital display
Volts, ohms, 10A, diode test
Audible continuity
0.7% basic dc accuracy
2000+ hour battery life
3-year warranty



Fluke 75

\$145*
Analog/digital display
Volts, ohms, 10A, mA, diode test
Audible continuity
Autorange/range hold
0.5% basic dc accuracy
2000+ hour battery life
3-year warranty



Fluke 77

\$185*
Analog/digital display
Volts, ohms, 10A, mA, diode test
Audible continuity
"Touch Hold" function
Autorange/range hold
0.3% basic dc accuracy
2000+ hour battery life
3-year warranty
Multipurpose holster

* Suggested Canadian price including duty and federal sales tax. Provincial taxes extra.



Allan Crawford Associates Ltd.

Test & Measurement Division


Toronto: (416) 678-1500 Montreal: (514) 731-8564 Ottawa (613) 722-7682
Halifax: (902) 463-8640 Vancouver: (604) 294-1326 Calgary: (403) 230-1341

Circle No. 11 on Reader Service Card

OSCILLOSCOPES!

The Best Buys Available

Model 65810
100 MHz Bench/Portable Scope

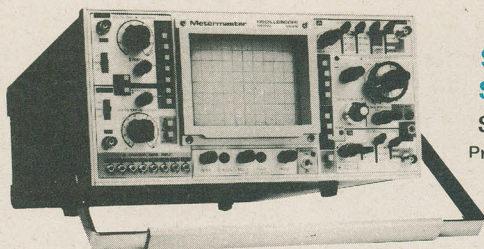


Now
\$2395.00
~~\$2595.00~~
~~\$2695.00~~
Probes & FST
included

A HYBRID COMBINING ANALOG AND
LOGIC FUNCTIONS

VERSATILITY +

- Will Display 4 Analog Traces (independently adjustable) or 8 Logic Channels, or 3 Analog and 8 Logic
- 2ns/Div. Sweep Speed
- 16 kV CRT Potential for A Bright Clear Display
- Scale Illumination
- Delayed Triggered Sweep

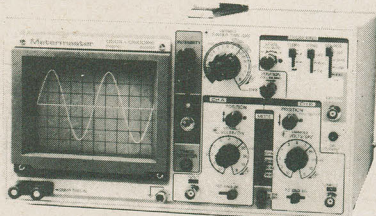Model 65601
Dual Trace Bench/Portable Scope




\$695.00
~~\$795.00~~
Probes & FST
included

Featuring at no extra cost 'The Component Tester'

- 20 MHz (-3dB) Bandwidth
- 6" CRT Display
- Fully Automatic Triggering
- Trace Rotator
- 5 mV Vertical Sensitivity
- HF Rejection

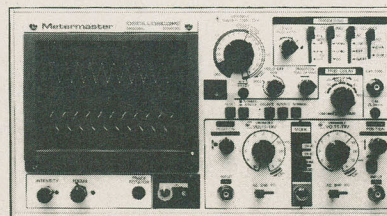Model 65635
Dual Trace Bench/Portable Scope



\$895.00
~~\$995.00~~
Probes & FST
included

- 35 MHz (-3dB) Bandwidth
- Delayed Sweep (selectable)
- Single Sweep (selectable)
- 6" CRT Display
- 1 mV Optimal Sensitivity
- X-Y or X-Y-Z Operation
- 120V AC Line Operation
- x5 Sweep Magnifier

MULTIMETERS!

Go for Quality --- Go for The Best Value


REDUCED PRICES... INCREASES YOUR VALUE

Models 78020, 78021, 78022

- AUTO ZERO
- AUTO POLARITY
- 3½ DIGIT LCD
- FULL OVERLOAD PROTECTION ON ALL RANGES
- RECESSED - SAFETY DESIGNED INPUT TERMINALS


Supplied with:

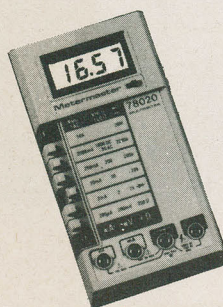- 28 Page Operating and Maintenance Manual
- Calibration Certificate Traceable to NRC
- Schematic with complete Parts Listing
- Safety Test Leads
- One-year Warranty




\$ 139.00 *

- ◆ ±0.1% DC
- ◆ 2000 hrs Bat. life

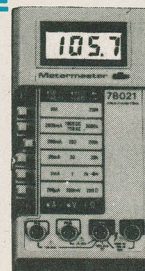

\$ 99.00 *

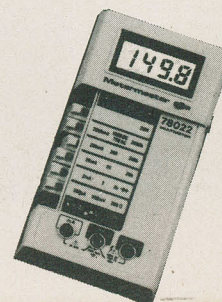- ◆ ±0.25% DC
- ◆ 10 Amps AC+DC
- ◆ 200 hrs Bat. life



\$ 89.00 *

- ◆ ±0.25% DC
- ◆ 200 hrs Bat. life

* FST Included

Metermaster

A Div. of R.H. NICHOLS CO. LTD.

Head Office: 214 Dolomite Drive, Downsview, Ontario M3J 2P8

TORONTO (416) 661-3190 MONTREAL (514) 337-0425 EDMONTON (403) 432-7746 OTTAWA (613) 238-7007

Circle No. 26 on Reader Service Card



5% Discount for Cash,
Certified Cheque, or Money Order
DEALER INQUIRIES INVITED

All prices F.O.B.
Downsview, Ontario
subject to change with-
out notice. P.S.T. extra
where applicable.

CIRCUIT IDEAS

Camera Remote Control

The infra-red remote controller gives the freedom to shoot photos from a distance, even from the other side of a window.

MANY of the more recent cameras to come onto the market have provision for an electric remote release, with the camera either being triggered directly or via an autowinder/motordrive. This type of release simply consists of a twin cable with a push button switch at one end and a plug at the other to match the camera or winder. The switch activates either the electronic shutter or an actuator in the winder. This method gives excellent reliability, but it still requires a long cable to carry the signal to the camera. This can be undesirable for some types of photography, and the cable also makes an excellent trip-wire!

For many purposes it is better to use a wire-less method of control, such as an infra-red or ultrasonic system. The latter offers slightly greater range, but infra-red systems have the advantage of operating quite well through a window, so that the camera equipment outside the house can be operated from within. The camera control system described here is of the infra-red type, operates reliably over a range of at least 6 metres, and is at least equal in this respect to the air release which it was designed to replace. It has mainly been used with a Pentax LX camera plus auto-winder, but it also worked well when tried with a Minolta XD7 (which is triggered directly), and it should work with any camera which has an electric release facility. The prototype has been built as a single channel system, but the equipment could easily be modified for multichannel use with multi-camera set-ups, as will be explained in greater detail later.

The System

The block diagram of Figure 1 shows the arrangement used in this remote control system, as it is not practical to use a high output power from the receiver. A simple DC system is consequently impractical, as the signal received from the transmitter would often be swamped by the ambient infra-red level. Instead, an AC system is used, with the transmitter providing an amplitude modulated beam. The infra-red signal is generated using a special type of light emitting diode, and this is driven from an audio oscillator via a buffer stage which provides the fairly high drive current required. This gives a crude form of modulation with the LED simply being switched from fully on to fully off, but for this application nothing more complex is needed.

The audio frequency output from the diode is not likely to be very large in practice, and would typically only be a few tens of microvolts. A high gain amplifier is therefore used to boost this signal to a high enough level to operate the following stage, which is a Phase Locked Loop tone decoder. This circuit has an electronic switch at its output, and this is turned on if an input signal at a frequency within its narrow locking range is received. The transmitter is adjusted so that its operating frequency is at the centre of the locking range, where the PLL decoder is most sensitive.

There are two reasons for the use of a PLL decoder in the circuit; one is simply that it gives almost total immunity to spurious triggering by electrical interference or noise. A second advantage is that it enables two remote control systems

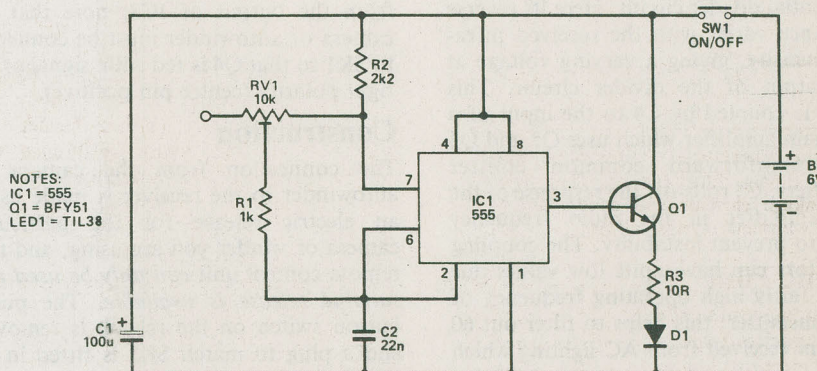


Fig. 2. The circuit diagram of the transmitter stage.

Another special type of diode is used at the receiver to produce an electrical signal from the received infra-red pulses. This is a large photodiode that gives good sensitivity, and although the diode itself is sensitive to a large part of the light spectrum, an integral infra-red filter removes light outside the infra-red range. This prevents strong light in the visible part of the spectrum from saturating the diode and preventing the system from operating properly.

to be used side-by-side without one also activating the other — provided the two operate on slightly different frequencies that is.

A monostable multivibrator is used as the next stage of the receiver, triggered by the output switch of the PLL tone decoder; the monostable drives a VMOS switching transistor which in turn controls the camera. The monostable is used to ensure that the VMOS switch is activated for a long enough time to operate the shutter,

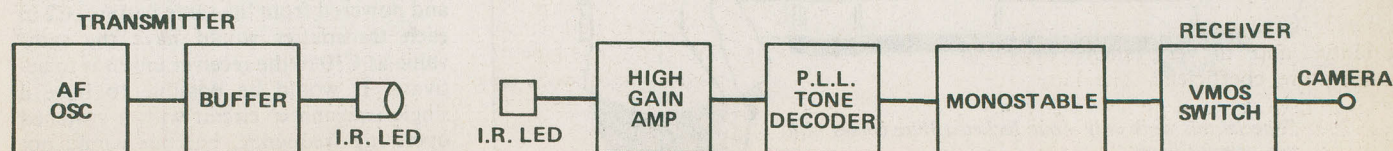


Fig. 1. A block diagram of the whole remote control system.

even if only a brief input signal is received. This helps to give more reliable operation if the system is used at virtually its maximum range.

Transmitter Circuit

Figure 2 shows the circuit diagram of the transmitter, based on a 555 astable oscillator. This gives a roughly squarewave signal, with RV1 used to trim the output to the appropriate frequency (around 5 kHz). The output stage of the 555 is barely able to provide sufficient output current to drive infra-red emitter D1 at the required current of around 150 milliamps, so Q1 is used as an emitter follower buffer stage to give more reliable and consistent results. Operating push-button on/off switch SW1 supplies power to the transmitter and activates the camera.

Receiver Circuit

The receiver unit is a little more complex, as can be seen from the circuit diagram of Figure 3. D2 is the infra-red photo diode: this can be used as a photovoltaic cell producing an output voltage which is roughly proportional to the received infra-red intensity; however, slightly higher sensitivity is obtained by using it in a potential divider circuit. Here its reverse resistance varies with the received infra-red intensity, giving a varying voltage at the output of the divider circuit. This signal is coupled by C4 to the input of a high gain amplifier which uses Q2 and Q3 as straightforward common emitter amplifiers. C5 rolls-off the response of the first amplifier in the radio frequency range to prevent instability. The coupling capacitors can have quite low values due to the fairly high operating frequency of the transmitter; this helps to filter out 60 Hz hum received from AC lighting which

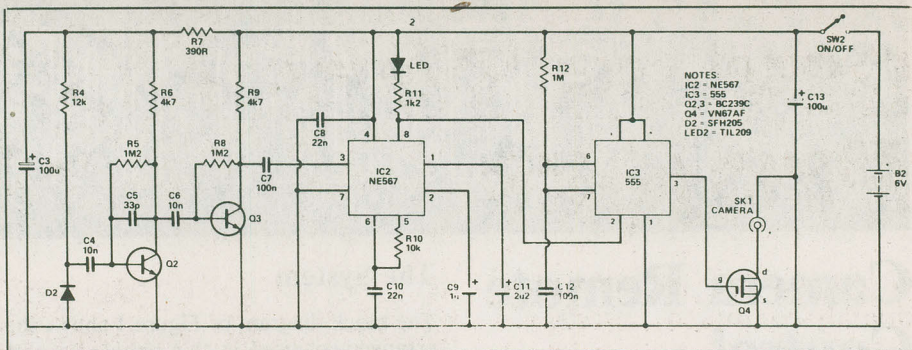


Fig. 3. The circuit diagram of the receiver stage.

could otherwise drive the amplifier into clipping and desensitize the circuit to the signal from the transmitter.

An NE567 (IC2) is used in the tone decoder, R11 and D3 form the collector load for its output transistor, and LED1 lights up when the tone decoder is activated. This is useful when adjusting the frequency control of the transmitter, and it also helps when setting-up the equipment ready for use.

The negative output signal from the tone decoder is used to trigger IC3, which is a 555 used in the standard monostable multivibrator configuration. Q4 is the VMOS output transistor, driven direct from the output of IC3; note that the camera or autowinder must be connected to SK1 so that Q4 is fed with signal of the right polarity (centre pin positive).

Construction

The connection from the camera or autowinder to the receiver is made using an electric release for the particular camera or winder you are using, and this remote control unit *can only be used if a suitable release is available*. The push-button switch on the release is removed and a plug to match SK1 is fitted in its

place. With the camera or winder connected to SK1 (and switched on where appropriate), a multimeter set to a fairly high DC volts range can be used to determine the polarity of the voltage on SK1 so that this can be correctly wired to the printed circuit board.

Like the transmitter unit, the receiver is powered from four 1.5 V cells. As it is likely that the unit will be left running for long periods, NiCad rechargeable cells are probably the most practical power source, but primary cells can be used if preferred.

Adjustment

RV1 is given the correct setting by trial and error. With the output of the transmitter aimed at D2 in the receiver from a short distance away, it should be possible to get LED1 to light up by adjusting RV1. If not, switch off both units at once and thoroughly recheck them for errors. Once LED1 can be made to light up, it is a matter of gradually moving the two units further apart and readjusting RV1, as necessary, to keep LED1 lit. This is continued until the maximum range of about seven metres is achieved.

Remember that the unit can only function properly if the infra-red radiation from the transmitter has a transparent path to D2 at the receiver. The unit is quite directional, mainly due to the built-in lens of D1, and the output of the transmitter needs to be aimed reasonably accurately at the receiver, especially when the system is used at something approaching its maximum range.

If it is necessary to control two or three cameras, a separate receiver unit for each one must be used. However, C10 in each unit must be given a slightly different value (15nF, 22nF, and 33nF are suitable). A separate transmitter circuit can be used for each receiver, housed in a single case and powered from the same battery. C2 in each transmitter would have the same value as C10 in the receiver unit it is to activate. It would be possible to have a single transmitter circuit with a switched operating frequency, but this would not give the option of firing two or three cameras simultaneously. **ETI**

ETI



Stylus Timer Project



Do you play your records with a smoothly-contoured, precision-engineered, highly-polished stylus — or a worn-out nail? Check your playing hours with the ETI Stylus Timer. Design and development by Phil Walker.


FOR modern styli and cartridge combinations, the life of the stylus may run to many hundreds or even thousands of hours before replacement is necessary. The trouble is that even at five hours each and every day (which is quite a lot) it will take over six months to accumulate 1,000 hours playing time. If you are like us, you could easily forget whether you changed the old nail last week or last year, quite apart from knowing how long it has been used since then.

Don't worry, help is at hand — this device is designed to measure the total number of hours your stylus has been in use since you last changed it and give some indication of that measurement.

The device has six LEDs which, in the basic configuration, change every 167 hours, totalling 1,000 hours. This could be used to indicate that a check on stylus condition would be carried out either at home or by your local dealer. When the last one comes on it will stay on until the device is reset (assuming the power is on).

As mentioned above, the basic design allows for 167 hours per step, the last one occurring after 1,000 hours. This can be modified to 330, 400, 830, or even 1,700 hours per step giving replacement times of up to 10,000 hours for the very lightest equipment (or Scrooges), or 83 hours per step if your equipment is a little heavier than some or you want to keep your stylus in tip-top condition all the time.

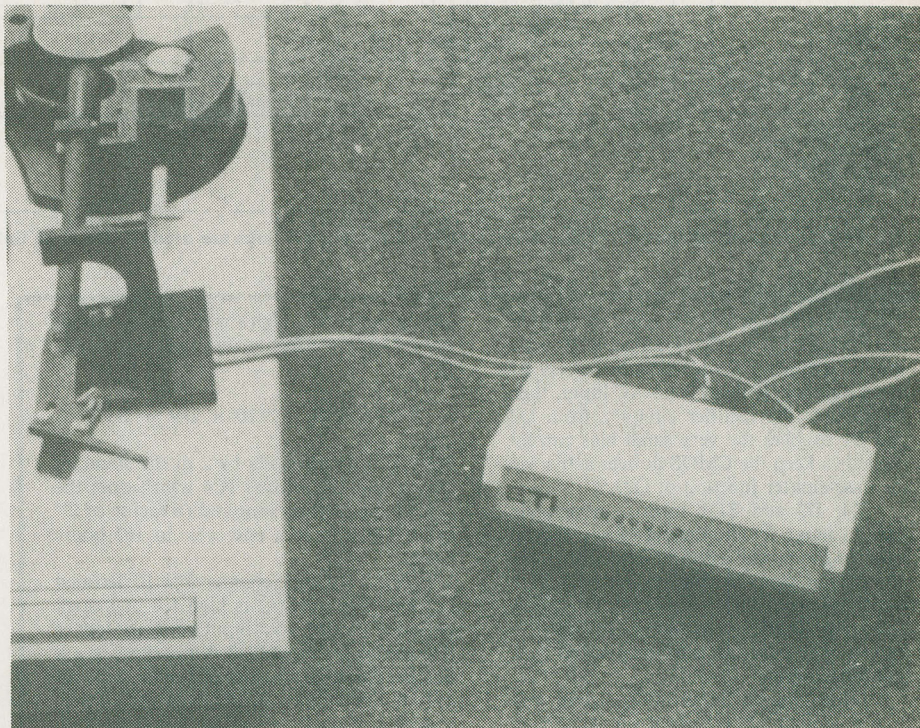In order to eliminate dependence on mains supplies when the equipment is not in use, the device contains a rechargeable battery which provides the microamp or so needed to keep the CMOS devices active. Also, the LED display is turned off when not required to conserve battery power. To prevent accidents, the reset facility is disabled when the device is on standby.



Designs Discussed

The circuit uses standard CMOS integrated circuits for most functions in order to keep the standby power as small as possible. This enables us to use a 8V4 rechargeable Ni-cad battery ensuring that with intermittent use the device should operate almost indefinitely. (In fact a normal dry-cell 9V battery will give a very long life but may not like the charging current flowing into it via R7).

The power for the LED display and the timing signal for the logic are taken from the AC input. This is any 60 Hz voltage source giving between 12 and 20 V at about 50 mA. For preference this supply should be switched with the turntable or equipment mains supply.

The first method of detecting stylus use we considered involved detecting the presence of a music signal from the pickup. However, if the signal was tapped off after the RIAA preamp, we realized the project couldn't be built by readers who lacked the confidence to muck about inside their expensive commercial hi-fi. On the other hand, putting the project between the deck and the preamp would lead to the knotty design problem of not degrading the

pickup performance. Thus we opted for a mechanical solution, but adventurous readers may care to adapt this project for their own needs. Note that we CANNOT give any technical advice if you do try it.

The circuit operates by detecting when the tone arm is away from its rest position and then allowing the rest of the circuit to count at 60 or 120 Hz. The 60 or 120 Hz is divided by about 72 million in order to driver the final counter at one pulse every 167 hours. The already decoded outputs of this device (IC5) are used by the output drive (IC6) to power the display.

The final counter (IC5) has ten decoded outputs of which only the first six are used. These control IC6 and thus the display. When the sixth output of IC5 goes high, it disables the counter chain causing the sixth LED to remain on indefinitely.

IC6 contains six inverting buffers which have three-state outputs. This facility is used to switch off the LEDs and conserve power.

A transistor (Q2) was used in the standby battery circuit so that when operating from the AC input, the supply voltage to the ICs was a little different to that when operating from battery alone.

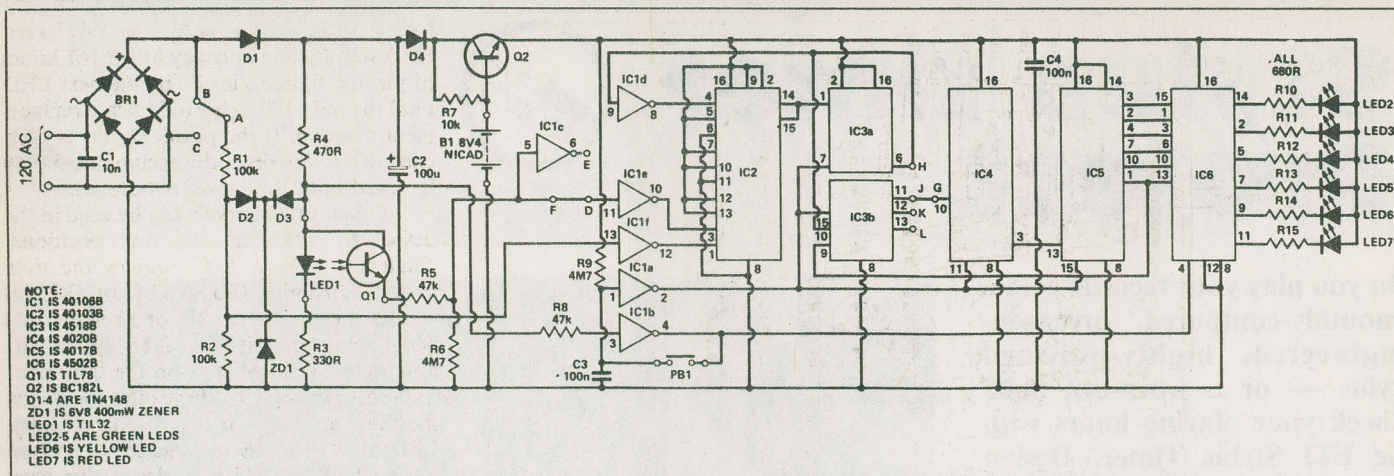


Fig. 1. Circuit diagram of the ETI Stylus Timer. The various lettered links are used to select the timing period (see text).

HOW IT WORKS

The 60 Hz power input is rectified by BR1 and charges C2 via D1. Q2 and R7 form a simple voltage regulator using the battery B1 as a reference. If there is no AC input, then D6 isolates the rectifier circuitry from Q2 and B1 supplies the very small bias current needed to keep the CMOS devices active via the base-emitter junction of Q2.

R4, D3 and ZD1 form a moderately stable voltage for the optical sensor and an input to the power detection circuitry IC1b. The output from the optical sensor (LED1 and Q1) is taken via R5 and R6 to IC1e either directly or via IC1c. This allows the circuit to operate with either an open or blocked light path as required.

Depending on the position of link A-B or A-C a 60 or 120 Hz signal will be applied to IC1f. The voltage of this signal is limited to R1, R2, D2 and ZD1 to prevent damage to IC1.

IC2 is connected such that it divides by 220 or 219 as determined by the input from IC1d. This is accomplished by the device loading its internal eight bit counter with the binary number on its inputs each time it reaches a count of zero. In this case the most significant seven bits are wired to 1101101X = 218, while the least significant bit (X) is switched between 0 and 1. The output from this stage drives IC3, a dual decade divider. The Q4 output from IC3a controls the division ratio of IC2 as outlined above. As the

Q4 output is only high for two clock periods out of 10, the effective division ratio of IC2 is:

$$8/10 \times 220 + 2/10 \times 219 = 219.8$$

IC3b is used to divide by 2 in the standard circuit and then drives IC4 which does the rest of the division required (a factor of 2¹⁴ or 16384) to give a one cycle in 167 hours signal.

IC5 is a decade counter with 10 decoded outputs. Each output is high for one clock period of the 167 hour input signal (or longer if counting is suspended). Only the first six outputs are used to drive IC6 and the sixth output also inhibits IC3b to prevent further counting. IC6 is a hex buffer with three-state outputs which have a fairly high impedance state by a signal on pin 4. This facility is used to prevent the LED display taking current while the AC supply is off.

The reset switch PB1 is connected in an unusual place so that it can only pull the input to IC1a low when the power sense circuit indicates that the AC supply is present. When operated, the reset circuit applies a high logic level to the reset inputs of IC's 3, 4 and 5 for about a second. IC2 is not reset and will cause an error of two or four seconds in the timing, but in a hundred hours or so, this is not significant.

Also the LED voltage can be stabilized at the correct value. The configuration allows the battery to be trickle-charged from the same supply.

Construction

The construction of the main unit is straightforward if a little fiddly on account of its small size. Assemble the components onto the PCB including the three links but excluding LED 2-7. Place the assembled PCB in the bottom of the box and align it over the wider spaced fixing holes with C2 next to the space for the battery. Mark the positions for the LEDs on the front panel

and the jack sockets and PB1 on the back panel. Also mark a position for the power cable grommet. Drill all these holes in sizes to fit your components.

Wire up the switch and sockets. The common connection from R4 on the board should go to the sleeve connections on the jack sockets to prevent accidental short circuits via the panel. The LEDs should now have their leads bent so that they will go into the board while the LED body protrudes through the panel. Finally connect the battery connector and the AC power lead. The latter should be a twin lead shielded cable terminated in a three pin DIN plug or similar to pick up the supply.

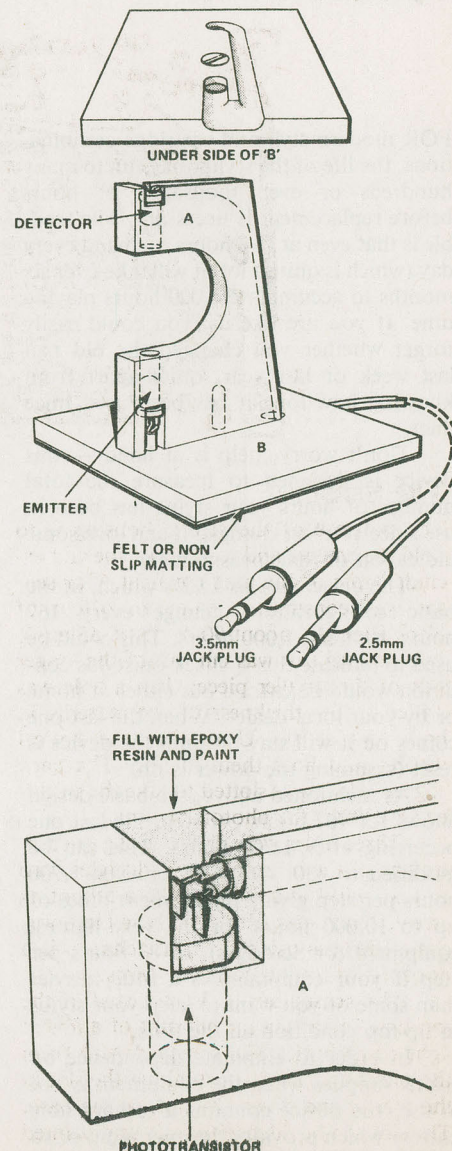


Fig. 2. Constructional details of our sensor. Using different sized jack plugs will prevent incorrect connection.


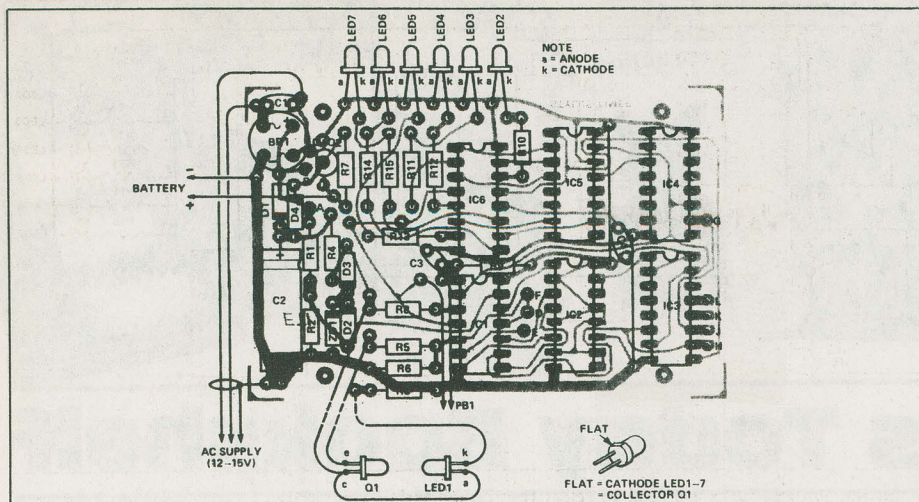


Fig. 3. Component overlay.

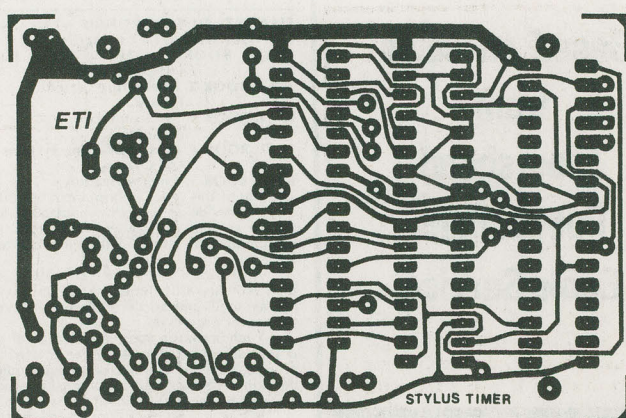

The Sensor

The purpose of the sensor housing is to hold the emitter and receiver in line and exclude some of the ambient light. Our sensor was constructed from an offcut of black Plexiglas about 90 × 55 × 55 mm). A U-shaped slot was cut out of the longer side of the smaller piece; then a hole was drilled in the thickness of the material in both legs of the U to take the optical devices and hold them in line. The back edge of the U was slotted to take the shielded wire from the phototransistor.

Three holes were drilled along the centre line of the other piece of Plexiglas; two to take wires and one to take a mounting screw. The underside of the base piece was channelled out using a rasp attachment in a hobbyist drill to conceal the wires.

The sensor device is mounted in the top hole to reduce the amount of ambient light reaching it. The screened wire from the phototransistor is run along the slot in the plastic and down the hole in the base. The slot can be filled with resin and painted when finished.

If a small three-way connector can be obtained, this could be used in place of the two jacks and a single length of shielded cable would suffice to connect the sensor.

Power Supply

The AC power supply is very simple and consists of a small transformer, fuse, neon indicator and three pin DIN socket mounted in a small box. Construction is very straightforward and, if the specified box is used, most small 6 VA transformers will fit onto the moulded pillars in the box, obviating the need for external screws.

Use and Modifications

To use the stylus timer, the sensor should be positioned so that the tone arm interrupts the light beam when it is in the rest position. Make sure that it does not foul the arm at any time if you have any sort of automatic control.

If possible, the AC power supply for the device should be obtained from your system. Anything from 12 to 15 V AC may be used without modification. Up to 25 V may be used, but R4 and R7 should then be 1k0 1 W and 27k respectively. If the supply is greater than 25 V, one side of any available supply is grounded, or if you prefer not to tamper with your system, then use the simple power supply described.

With the sensor in position and a suitable AC supply connected, press the

reset button on the unit. The first green LED should light and stay lit for 167 hours of playing time, followed by the next LED until the red LED lights to indicate replacement overdue. If the power supply is switched off at any time, the accumulated time is stored until the power is restored.

Other time intervals can be used in the device by changing the link positions. Changing A-B to A-C doubles the time period. Changing G-J to G-K or G-L increases the interval by 2½ or 5 respectively while changing it to G-H halves it, although it will not stop on the last count as before. In some of these other positions the intervals between the lighting of each LED may not be as regular as before (especially G-K). If it is desired to have counting enabled when the light path is obstructed, then link D-F should be changed to D-E.

PARTS LIST

Resistors (all ¼ W, 5%)

R1,2	100k
R3	330R
R4	470R
R5,8	47k
R6,9	4M7
R7	10k
R10-15	680R

Capacitors

C1	10n ceramic
C2	100u 40 V axial electrolytic
C3,4	100n ceramic

Semiconductors

IC1	40106B
IC2	40103B
IC3	4518B
IC4	4020B
IC5	4017B
IC6	4502B
Q1	TIL78 IR receiver
Q2	BC182L, 2N3904, etc.
D1-4	1N4148
ZD1	6V8 400 mW zener
BR1	50 V, 1 A bridge rectifier
LED1	TIL32 IR transmitter
LED2-5	2 mm green LED
LED6	2 mm yellow LED
LED7	2 mm red LED

Miscellaneous

PB1	subminiature push-button
B1	8V4 Ni-cad

PCB battery clips; case 125 × 65 × 30 mm (Vero 75-2682A); 3.5 and 2.5 mm jack plugs and sockets; three pin DIN plug (if required to connect to power unit); thin twin cable; small grommet; 100 × 55 × 6 mm acrylic sheet.

AC Power Unit (If Required)


12 V, 6 VA mains transformer; 100 mA fuse and fuseholder; mains neon; case 125 × 65 × 50 mm (Vero ref. 75-2684B); three pin DIN socket; line cord; grommet; solder tags.

ETI



Electronics Today Bookshelf

Top

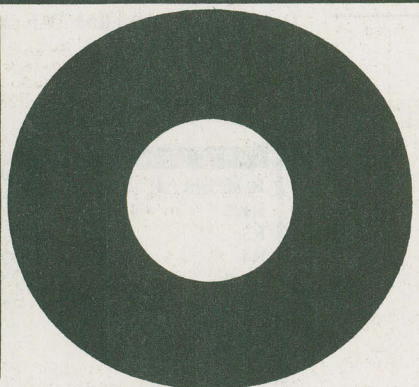

Based on sales
from
**Moorshead
Publications
Book Service**

Electronic Books

1 BP73: REMOTE CONTROL PROJECTS \$8.10 OWEN BISHOP

This book is aimed primarily at the electronics enthusiast who wishes to experiment with remote control. Full explanations have been given so that the reader can fully understand how the circuits work and can more easily see how to modify them for other purposes, depending on personal requirements. Not only are radio control systems considered but also infra-red, visible light and ultrasonic systems as are the use of Logic ICs and Pulse position modulation etc.

2 BP90: AUDIO PROJECTS \$7.60 F.G. RAYER

Covers in detail the construction of a wide range of audio projects. The text has been divided into preamplifiers and mixers, power amplifiers, tone controls and matching and miscellaneous projects.

3 The GIANT HANDBOOK OF ELECTRONIC CIRCUITS \$27.95 TAB No.1300

About as twice as thick as the Webster's dictionary, and having many more circuit diagrams, this book is ideal for any experimenter who wants to keep amused for several centuries. If there isn't a circuit for it in here, you should have no difficulty convincing yourself you don't really want to build it.

4 ELECTRONIC TROUBLESHOOTING HANDBOOK \$11.95 AB019

This workbook guide can show you how to pinpoint circuit troubles in minutes, how to test anything electronic, and how to get the most out of low cost test equipment. You can use any and all of the time-saving shortcuts to rapidly locate and repair all types of electronic equipment malfunctions.

5 BP74: ELECTRONIC MUSIC PROJECTS \$7.20 R.A. PENFOLD

Although one of the more recent branches of amateur electronics, electronic music has now become extremely popular and there are many projects which fall into this category. The purpose of this book is to provide the constructor with a number of practical circuits for the less complex items of electronic music equipment, including such things as a Fuzz Box, Waa-Waa Pedal, Sustain Unit, Reverberation and Phaser-Units, Tremolo Generator etc.

6 BP44: IC 555 PROJECTS \$7.75 E.A. PARR, B.Sc., C.Eng., M.I.E.E.

Every so often a device appears that is so useful that one wonders how life went on before without it. The 555 timer is such a device. Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

7 BP37: 50 PROJECTS USING RELAYS, \$7.75 SCR'S & TRIACS F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Relays, silicon controlled rectifiers (SCR's) and bi-directional triodes (TRIACs) have a wide range of applications in electronics today. This book gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct. In most of the circuits there is a wide latitude in component values and types, allowing easy modification of circuits or ready adaptation of them to individual needs.

8 BP79: RADIO CONTROL FOR BEGINNERS \$6.80 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

The aim of this book is to act as an introduction to Radio Control for beginners to the hobby. The book will commence by dealing with the conditions that are allowable for such things as frequency and power of transmission. This is followed by a "block" explanation of how control device and transmitter operate and receiver and actuator(s) produce motion in a model.

Details are then given of actual solid state transmitting equipment which the reader can build. Plain and loaded aerials are then discussed and so is the field-strength meter to help with proper setting up.

The radio receiving equipment is then dealt with which includes a simple receiver and also a crystal controlled superhet. The book ends with the electro-mechanical means of obtaining movement of the controls of the model.

9 99 TEST EQUIPMENT PROJECTS YOU CAN BUILD \$15.95 TAB No.805

An excellent source book for the hobbyist who wants to build up his work bench inexpensively. Projects range from a simple signal tracer to a 50MHz frequency counter. There are circuits to measure just about any electrical quantity: voltage, current, capacitance, impedance and more. The variety is endless and includes just about anything you could wish for!

10BP76: POWER SUPPLY PROJECTS \$7.75 R.A. PENFOLD

Line power supplies are an essential part of many electronics projects. The purpose of this book is to give a number of power supply designs, including simple unregulated types, fixed voltage regulated types, and variable voltage stabilised designs, the latter being primarily intended for use as bench supplies for the electronics workshop. The designs provided are all low voltage types for semiconductor circuits.

There are other types of power supply and a number of these are dealt with in the final chapter, including a cassette power supply, Ni-Cad battery charger, voltage step up circuit and a simple inverter.

See order form in this issue.

ELECTRONIC THEORY

ELEMENTS OF ELECTRONICS — AN ON-GOING SERIES

F.A. WILSON, C.G.I.A., C.Eng.,	
BP62: BOOK 1. The Simple Electronic Circuit and Components	\$8.45
BP63: BOOK 2. Alternating Current Theory	\$8.45
BP64: BOOK 3. Semiconductor Technology	\$8.45
BP77: BOOK 4. Microprocessing Systems And Circuits	\$11.70
BP89: BOOK 5. Communication	\$11.70

The aim of this series of books can be stated quite simply — it is to provide an inexpensive introduction to modern electronics so that the reader will start on the right road by thoroughly understanding the fundamental principles involved.

Although written especially for readers with no more than ordinary arithmetical skills, the use of mathematics is not avoided, and all the mathematics required is taught as the reader progresses.

Each book is a complete treatise of a particular branch of the subject and, therefore, can be used on its own with one proviso, that the later books do not duplicate material from their predecessors, thus a working knowledge of the subjects covered by the earlier books is assumed.

BOOK 1: This book contains all the fundamental theory necessary to lead to a full understanding of the simple electronic circuit and its main components.

BOOK 2: This book continues with alternating current theory without which there can be no comprehension of speech, music, radio, television or even the electricity utilities.

BOOK 3: Follows on semiconductor technology, leading up to transistors and integrated circuits.

BOOK 4: A complete description of the internal workings of microprocessor.

BOOK 5: A book covering the whole communication scene.

PH247: DIGITAL TECHNIQUES \$19.95
Covers logic circuits, Boolean Algebra, flip-flops, registers, combinational logic circuitry, and digital design.

PROJECTS

BP48: ELECTRONIC PROJECTS FOR BEGINNERS \$7.75 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Another book written by the very experienced author — Mr. F.G. Rayer — and in it the newcomer to electronics, will find a wide range of easily made projects. Also, there are a considerable number of actual component and wiring layouts, to aid the beginner.

Furthermore, a number of projects have been arranged so that they can be constructed without any need for soldering and, thus, avoid the need for a soldering iron.

Also, many of the later projects can be built along the lines as those in the 'No Soldering' section so this may considerably increase the scope of projects which the newcomer can build and use.

221: 28 TESTED TRANSISTOR PROJECTS \$5.00 R.TORRENS

Mr. Richard Torrens is a well experienced electronics development engineer and has designed, developed, built and tested the many useful and interesting circuits included in this book. The projects themselves can be split down into simpler building blocks, which are shown separated by boxes in the circuits for ease of description, and also to enable any reader who wishes to combine boxes from different projects to realise ideas of his own.

BP71: ELECTRONIC HOUSEHOLD PROJECTS \$7.20 R.A. PENFOLD

Some of the most useful and popular electronic construction projects are those that can be used in or around the home. The circuits range from such things as '2 Tone Door Buzzer', Intercom, through Smoke or Gas Detectors to Baby and Freezer Alarms.

Electronics Today Bookshelf

BP49: POPULAR ELECTRONIC PROJECTS \$7.75 R.A. PENFOLD

Includes a collection of the most popular types of circuits and projects which, we feel sure, will provide a number of designs to interest most electronics constructors. The projects selected cover a very wide range and are divided into four basic types: Radio Projects, Audio Projects, Household Projects and Test Equipment.

BP94: ELECTRONIC PROJECTS FOR CARS AND BOATS \$7.60 R.A. PENFOLD

Projects, fifteen in all, which use a 12V supply are the basis of this book. Included are projects on Windscreen Wiper Control, Courtesy Light Delay, Battery Monitor, Cassette Power Supply, Lights Timer, Vehicle Immobiliser, Gas and Smoke Alarm, Depth Warning and Shaver Inverter.

BP95: MODEL RAILWAY PROJECTS \$7.60

Electronic projects for model railways are fairly recent and have made possible an amazing degree of realism. The projects covered include controllers, signals and sound effects: striboard layouts are provided for each project.

BP93: ELECTRONIC TIMER PROJECTS \$7.60 F.G. RAYER

Windscreen wiper delay, darkroom timer and metronome projects are included. Some of the more complex circuits are made up from simpler sub-circuits which are dealt with individually.

BP113: 30 Solderless Breadboard Projects-Book 2 \$8.85 R.A. Penfold

A companion to BP107. Describes a variety of projects that can be built on plug-in breadboards using CMOS logic IC's. Each project contains a schematic, parts list and operational notes.

BP104: Electronic Science Projects \$8.85 Owen Bishop

Contains 12 electronic projects with a strong scientific flavour. Includes Simple Colour Temperature Meter, Infra-Red Laser, Electronic clock regulated by a resonating spring, a Scope with a solid state display, pH meter and electrocardiograph.

BP110: HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$7.60 R.A. PENFOLD

We have all built circuits from magazines and books only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

BP84: DIGITAL IC PROJECTS \$7.60 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

This book contains both simple and more advanced projects and it is hoped that these will be found of help to the reader developing a knowledge of the workings of digital circuits. To help the newcomer to the hobby the author has included a number of board layouts and wiring diagrams. Also the more ambitious projects can be built and tested section by section and this should help avoid or correct faults that could otherwise be troublesome. An ideal book for both beginner and more advanced enthusiast alike.

BP67: COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS \$7.05 F.G. RAYER, T.Eng.(CEI), Assoc. IERE

Numerical indicating devices have come very much to the forefront in recent years and will, undoubtedly, find increasing applications in all sorts of equipment. With present day integrated circuits, it is easy to count, divide and display numerically the electrical pulses obtained from a great range of driver circuits.

In this book many applications and projects using various types of numeral displays, popular counter and driver IC's etc. are considered.

BP99: MINI-MATRIX BOARD PROJECTS \$7.60 R.A. PENFOLD

Twenty useful projects which can all be built on a 24 x 10 hole matrix board with copper strips. Includes Doorbuzzer, Low-voltage Alarm, AM Radio, Signal Generator, Projector Timer, Guitar Headphone Amp, Transistor Checker and more.

BP103: MULTI-CIRCUIT BOARD PROJECTS \$7.60 R.A. PENFOLD

This book allows the reader to build 21 fairly simple electronic projects, all of which may be constructed on the same printed circuit board. Wherever possible, the same components have been used in each design so that with a relatively small number of components and hence low cost, it is possible to make any one of the projects or by re-using the components and P.C.B. all of the projects.

BP107: 30 SOLDERLESS BREADBOARD PROJECTS — BOOK 1 \$8.85 R.A. PENFOLD

A "Solderless Breadboard" is simply a special board on which electronic circuits can be built and tested. The components used are just plugged in and unplugged as desired. The 30 projects featured in this book have been specially designed to be built on a "Verobloc" breadboard. Wherever possible the components used are common to several projects, hence with only a modest number of reasonably inexpensive components it is possible to build, in turn, every project shown.

BP106: MODERN OP-AMP PROJECTS \$7.60 R.A. PENFOLD

Features a wide range of constructional projects which make use of op-amps including low-noise, low distortion, ultra-high input impedance, high slew-rate and high output current types.

CIRCUITS

How to Design Electronic Projects

BP127 \$8.95
Although information on standard circuit blocks is available, there is less information on combining these circuit parts together. This title does just that. Practical examples are used and each is analysed to show what each does and how to apply this to other designs.

Audio Amplifier Construction

BP122 \$8.95
A wide circuit is given, from low noise microphone and tape head preamps to a 100W MOSFET type. There is also the circuit for 12V bridge amp giving 18W. Circuit board or strip-board layout are included. Most of the circuits are well within the capabilities for even those with limited experience.

Electronic Circuits for Model Railways

BP213 \$4.50
Lots of circuits including three types of controllers including one with simulated inertia and one with high power. Signalling and lighting systems are discussed at length and the suppression of RF interference. There are also 4 "steam whistle" and "chuffer" circuits.

BP80: POPULAR ELECTRONIC CIRCUITS — BOOK 1 \$7.75 R.A. PENFOLD

Another book by the very popular author, Mr. R.A. Penfold, who has designed and developed a large number of various circuits. These are grouped under the following general headings: Audio Circuits, Radio Circuits, Test Gear Circuits, Music Project Circuits, Household Project Circuits and Miscellaneous Circuits.

BP98: POPULAR ELECTRONIC CIRCUITS, BOOK 2 \$8.85 R.A. PENFOLD

70 plus circuits based on modern components aimed at those with some experience.

BP39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS \$6.75 F.G. RAYER, T.Eng.(CEI), Assoc.IERE

Field effect transistors (FETs), find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, as well as various miscellaneous devices which are useful in the home.

This book contains something of particular interest for every class of enthusiast — short wave listener, radio amateur, experimenter or audio devotee.

BP87: SIMPLE L.E.D. CIRCUITS \$5.40 R.N. SOAR

Since it first appeared in 1977, Mr. R.N. Soar's book has proved very popular. The author has developed a further range of circuits and these are included in Book 2. Projects include a Transistor Tester, Various Voltage Regulators, Testers and so on.

BP42: 50 SIMPLE L.E.D. CIRCUITS \$3.05 R.N. SOAR

The author of this book, Mr. R.N. Soar, has compiled 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components — the Light Emitting Diode (L.E.D.). A useful book for the library of both beginner and more advanced enthusiast alike.

THE ACTIVE FILTER HANDBOOK

TAB No.1133 \$13.95
Whatever your field — computing, communications, audio, electronic music or whatever — you will find this book the ideal reference for active filter design.

The book introduces filters and their uses. The basic math is discussed so that the reader can tell where all design equations come from. The book also presents many practical circuits including a graphic equalizer, computer tape interface and more.

MASTER HANDBOOK OF 1001 PRACTICAL CIRCUITS \$19.95 TAB No.800

MASTER HANDBOOK OF 1001 MORE PRACTICAL CIRCUITS \$23.95 TAB No.804

Here are transistor and IC circuits for just about any application you might have. An ideal source book for the engineer, technician or hobbyist. Circuits are classified according to function, and all sections appear in alphabetical order.

BP88: HOW TO USE OP AMPS \$8.85 E.A. PARR

A designer's guide covering several op amps, serving as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

BP65: SINGLE IC PROJECTS \$6.05 R.A. PENFOLD

There is now a vast range of ICs available to the amateur market, the majority of which are not necessarily designed for use in a single application and can offer unlimited possibilities. All the projects contained in this book are simple to construct and are based on a single IC. A few projects employ one or two transistors in addition to an IC but in most cases the IC is the only active device used.

BP117: PRACTICAL ELECTRONIC BUILDING BLOCKS BOOK 1 \$7.60

Virtually any electronic circuit will be found to consist of a number of distinct stages when analysed. Some circuits inevitably have unusual stages using specialised circuitry, but in most cases circuits are built up from building blocks of standard types.

This book is designed to aid electronics enthusiasts who like to experiment with circuits and produce their own projects rather than simply follow published project designs.

The circuits for a number of useful building blocks are included in this book. Where relevant, details of how to change the parameters of each circuit are given so that they can easily be modified to suit individual requirements.

223: 50 PROJECTS USING IC CA3130 \$5.00 R.A. PENFOLD

In this book, the author has designed and developed a number of interesting and useful projects which are divided into five general categories: I — Audio Projects II — R.F. Projects III — Test Equipment IV — Household Projects V — Miscellaneous Projects.

224: 50 CMOS IC PROJECTS \$3.75 R.A. PENFOLD

CMOS IC's are probably the most versatile range of digital devices for use by the amateur enthusiast. They are suitable for an extraordinary wide range of applications and are also some of the most inexpensive and easily available types of IC.

Mr. R.A. Penfold has designed and developed a number of interesting and useful projects which are divided into four general categories: I — Multivibrators II — Amplifiers and Oscillators III — Trigger Devices IV — Special Devices.

THE MASTER IC COOKBOOK \$17.95 TAB No.1199

If you've ever tried to find specs for a so called 'standard' chip, then you'll appreciate this book. C.L. Hallmark has compiled specs and pinout for most types of ICs that you'd ever want to use.

BP118: PRACTICAL ELECTRONIC BUILDING BLOCKS - Book 2 \$7.60 R.A. PENFOLD

This sequel to BP117 is written to help the reader create and experiment with his own circuits by combining standard type circuit building blocks. Circuits concerned with generating signals were covered in Book 1, this one deals with processing signals. Amplifiers and filters account for most of the book but comparators, Schmitt triggers and other circuits are covered.

BP24: 50 PROJECTS USING IC741 \$3.75 RUDI & UWE REDMER

This book, originally published in Germany by TOPP, has achieved phenomenal sales on the Continent and Babani decided, in view of the fact that the integrated circuit used in this book is inexpensive to buy, to make this unique book available to the English speaking reader. Translated from the original German with copious notes, data and circuitry, a "must" for everyone whatever their interest in electronics.

BP83: VMOS PROJECTS \$7.70 R.A. PENFOLD

Although modern bipolar power transistors give excellent results in a wide range of applications, they are not without their drawbacks or limitations. This book will primarily be concerned with VMOS power FETs although power MOSFETs will be dealt with in the chapter on audio circuits. A number of varied and interesting projects are covered under the main headings of: Audio Circuits, Sound Generator Circuits, DC Control Circuits and Signal Control Circuits.

BP50: IC LM3900 PROJECTS \$5.40 H.KYBETT, B.Sc., C.Eng.

The purpose of this book is to introduce the LM3900 to the Technician, Experimenter and the Hobbyist. It provides the groundwork for both simple and more advanced uses, and is more than just a collection of simple circuits or projects.

Simple basic working circuits are used to introduce this IC. The LM3900 can do much more than is shown here, this is just an introduction. Imagination is the only limitation with this useful and versatile device. But first the reader must know the basics and that is what this book is all about.

ELECTRONIC DESIGN WITH OFF THE SHELF INTEGRATED CIRCUITS \$12.95 AB016

This practical handbook enables you to take advantage of the vast range of applications made possible by integrated circuits. The book tells how, in step by step fashion, to select components and how to combine them into functional electronic systems. If you want to stop being a "cookbook hobbyist", then this is the book for you.

See order form in this issue.

Electronics Today Bookshelf

RADIO AND COMMUNICATIONS

BP96: CB PROJECTS \$7.60

R.A. PENFOLD
Projects include speech processor, aerial booster, cordless mike, aerial and harmonic filters, field strength meter, power supply, CB receiver and more.

222: SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS \$4.70

R.A. PENFOLD
In this book, R.A. Penfold has designed and developed several modern solid state short wave receiver circuits that will give a fairly high level of performance, despite the fact that they use only relatively few and inexpensive components.

BP91: AN INTRODUCTION TO RADIO DXing \$7.60

This book is divided into two main sections one to amateur band reception, the other to broadcast bands. Advice is given to suitable equipment and techniques. A number of related constructional projects are described.

BP105: AERIAL PROJECTS \$7.60

R.A. PENFOLD
The subject of aerials is vast but in this book the author has considered practical designs including active, loop and ferrite aerials, which give good performances and are reasonably simple and inexpensive to build. The complex theory and math of aerial design are avoided.

BP125: 25 Simple Amateur Band Aerials \$7.60

E.M. NOLL
Starting from simple dipoles through beam, triangle and even mini-rhombics (made from TV masts and 400ft of wire) this title describes several simple and inexpensive aerials to construct yourself. A complete set of dimension table are included.

BP46: RADIO CIRCUITS USING IC's \$5.40

J.B. DANCE, M.Sc.
This book describes integrated circuits and how they can be employed in receivers for the reception of either amplitude or frequency modulated signals. The chapter on amplitude modulated (a.m.) receivers will be of most interest to those who wish to receive distant stations at only moderate audio quality, while the chapter on frequency modulation (f.m.) receivers will appeal to those who desire high fidelity reception.

BP92: ELECTRONICS SIMPLIFIED—CRYSTAL SET CONSTRUCTION \$6.80

F.A. WILSON
Aimed at those who want to get into construction without much theoretical study. Homewound coils are used and all projects are very inexpensive to build.

BP70: TRANSISTOR RADIO FAULT-FINDING CHART \$1.90

CHAS. E. MILLER
Across the top of the chart will be found four rectangles containing brief descriptions of various faults, viz—sound weak but undistorted; set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

AUDIO

205: FIRST BOOK OF HI-FI LOUDSPEAKER ENCLOSURES \$3.05

B.B. BABANI
This book gives data for building most types of loudspeaker enclosure. Includes corner reflex, bass reflex, exponential horn, folded horn, tuned port, klipschorn labyrinth, tuned column, loaded port and multi speaker panoramic. Many clear diagrams for every construction showing the dimensions necessary.

HOW TO BUILD A SMALL BUDGET RECORDING STUDIO FROM SCRATCH... \$15.95

TAB No. 1164
The author, F. Alton Everest, has gotten studios together several times, and presents twelve complete, tested designs for a wide variety of applications. If all you own is a mono cassette recorder, you don't need this book. If you don't want your new four track to wind up sounding like one, though, you shouldn't be without it.

BP51: ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$7.75

M.K. BERRY
Electronic music is the new music of the Twentieth Century. It plays a large part in "pop" and "rock" music and, in fact, there is scarcely a group without some sort of synthesiser or other effects generator.

This book sets out to show how electronic music can be made at home with the simplest and most inexpensive of equipment. It then describes how the sounds are generated and how these may be recorded to build up the final composition.

BP81: ELECTRONIC SYNTHESISER PROJECTS \$6.80

M.K. BERRY
One of the most fascinating and rewarding applications of electronics is in electronic music and there is hardly a group today without some sort of synthesiser or effects generator. Although an electronic synthesiser is quite a complex piece of electronic equipment, it can be broken down into much simpler units which may be built individually and these can then be used or assembled together to make a complete instrument.

ELECTRONIC MUSIC SYNTHESIZERS \$10.95

TAB No. 1167
If you're fascinated by the potential of electronics in the field of music, then this is the book for you. Included is data on synthesizers in general as well as particular models. There is also a chapter on the various accessories that are available.

TEST EQUIPMENT

BP75: ELECTRONIC TEST EQUIPMENT CONSTRUCTION \$6.80

F.G. RAYER, T.Eng. (CEI), Assoc. IERE
This book covers in detail the construction of a wide range of test equipment for both the Electronics Hobbyists and Radio Amateur. Included are projects ranging from an FET Amplified Voltmeter and Resistance Bridge to a Field Strength Indicator and Heterodyne Frequency Meter. Not only can the home constructor enjoy building the equipment but the finished projects can also be usefully utilised in the furtherance of his hobby.

THE POWER SUPPLY HANDBOOK \$15.95

TAB No. 806
A complete one stop reference for hobbyists and engineers. Contains high and low voltage power supplies of every conceivable type as well mobile and portable units.

REFERENCE

BP85: INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE \$11.75

ADRIAN MICHAELS
This book will help the reader to find possible substitutes for a popular user-orientated selection of modern transistors. Also shown are the material type, polarity, manufacturer selection of modern transistors. Also shown are the material type, polarity, manufacturer and use. The Equivalents are sub-divided into European, American and Japanese. The products of over 100 manufacturers are included. An essential addition to the library of all those interested in electronics, be they technicians, designers, engineers or hobbyists. Fantastic value for the amount of information it contains.

BP108: INTERNATIONAL DIODE EQUIVALENTS GUIDE \$8.95

ADRIAN MICHAELS
This book is designed to help the user in finding possible substitutes for a large user orientated selection of the many different types of semiconductor diodes that are available today. Besides simple rectifier diodes also included are: Zener diodes, LEDs, Diacs, Triacs, Thyristors, Photo diodes and Display diodes.

BP1: FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES \$5.75

B.B. BABANI
This guide covers many thousands of transistors showing possible alternatives and equivalents. Covers transistors made in Great Britain, USA, Japan, Germany, France, Europe, Hong Kong, and includes types produced by more than 120 different manufacturers.

BP14: SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES \$6.75

B.B. BABANI
The "First Book of Transistor Equivalents" has had to be reprinted 15 times. The "Second Book" produced in the same style as the first book, in no way duplicates any of the data presented in it. The "Second Book" contains only additional material and the two books complement each other and make available some of the most complete and extensive information in this field. The interchangeability data covers semiconductors manufactured in Great Britain, USA, Germany, France, Poland, Italy, East Germany, Belgium, Austria, Netherlands and many other countries.

TOWER'S INTERNATIONAL OP-AMP LINEAR IC SELECTOR \$12.95

TAB No. 1216
This book contains a wealth of useful data on over 5,000 Op-amps and linear ICs — both pinouts and essential characteristics. A comprehensive series of appendices contain information on specs, manufacturers, case outlines and so on.

CMOS DATABASE \$9.45

There are several books around with this title, but most are just collections of manufacturers' data sheets. This one, by Bill Hunter, explains all the intricacies of this useful family of logic devices... the missing link in getting your own designs working properly. Highly recommended to anyone working with digital circuits.

ROBOTICS

THE COMPLETE HANDBOOK OF ROBOTICS \$15.95

TAB No. 1071
All the information you need to build a walking, talking mechanical friend appears in this book. Your robot can take many forms and various options — light, sound, and proximity sensors — are covered in depth.

HOW TO BUILD YOUR OWN SELF PROGRAMMING ROBOT \$13.95

TAB No. 1241
A practical guide on how to build a robot capable of learning how to adapt to a changing environment. The creature developed in the book, Rodney, is fully self programming, can develop theories to deal with situations and apply those theories in future circumstances.

BUILD YOUR OWN WORKING ROBOT \$10.95

TAB No. 841
Contains complete plans — mechanical, schematics, logic diagrams and wiring diagrams — for building Buster. Buster is a sophisticated experiment in cybernetics you can build in stages. There are two phases involved: first Buster is leashed, dependent on his creator for guidance; the second phase makes Buster more independent and able to get out of tough situations.

VIDEO

BP100: AN INTRODUCTION TO VIDEO \$7.60

D.K. MATHEWSON
Presents in as non-technical a way as possible how a video recorder works and how to get the best out of it and its accessories. Among the items discussed are the pros and cons of the various systems, copying and editing, international tape exchange and understanding specifications.

Tab1519: ALL ABOUT HOME SATELLITE TELEVISION \$22.95

Covers such aspects as where to buy, problems in setting up your TVRO station and how to solve them, antenna siting and equipment selection.

Tab1490: VIDEO CASSETTE RECORDERS: BUYING, USING AND MAINTAINING \$14.95

A complete handbook for the video enthusiast. You'll learn about how the systems work and how to choose as well as take a technical look at the inside workings. There are also sections on making your own video recordings.

MISCELLANEOUS

PH255: COMPLETE GUIDE TO READING SCHEMATIC DIAGRAMS, 2nd Edition \$9.95

J. DOUGLAS-YOUNG
Packed with scores of easy-to-understand diagram and invaluable troubleshooting tips as well as a circuit finder chart and a new section on logic circuits.

BP107: HOW TO IDENTIFY UNMARKED IC'S \$2.20

K.H. RECOR
Originally published as a feature in "Radio Electronics", this chart shows how to record the particular signature of an unmarked IC using a test meter, this information can then be used with manufacturer's data to establish the application.

BASIC TELEPHONE SWITCHING SYSTEMS \$15.50

TALLEY HB27
The Revised Second Edition of this book, for trainee and engineer alike, includes updated statistical data on telephone stations, and new and improved signaling methods and switching techniques. It also includes E & M signaling interface for electronic central offices and automatic number identification methods used in step-by-step, panel and crossbar central offices.

PH252: DIGITAL ICs: HOW THEY WORK AND HOW TO USE THEM \$10.95

A. BARBER
The dozens of illustrations included in this essential reference book will help explain time-saving test procedures, interpreting values, performing voltage measurements, and much more!


AUDIO AND VIDEO INTERFERENCE CURES \$8.95

KAHANER HB21
A practical work about interference causes and cures that affect TV, radio, hi-fi, CB, and other devices. Provides all the information needed to stop interference. Schematic wiring diagrams of filters for all types of receivers and transmitters are included. Also, it supplies simple filter diagrams to eliminate radio and TV interference caused by noisy home appliances, neon lights, motors, etc.


BP121: How to Design and Make Your Own PCBs \$7.60

R.A. Penfold
The emphasis is on practical rather than theoretical techniques. Starts by giving simple methods of copying from magazines, carries on with photographic methods of producing PCBs and continues with layout design.

See order form in this issue.

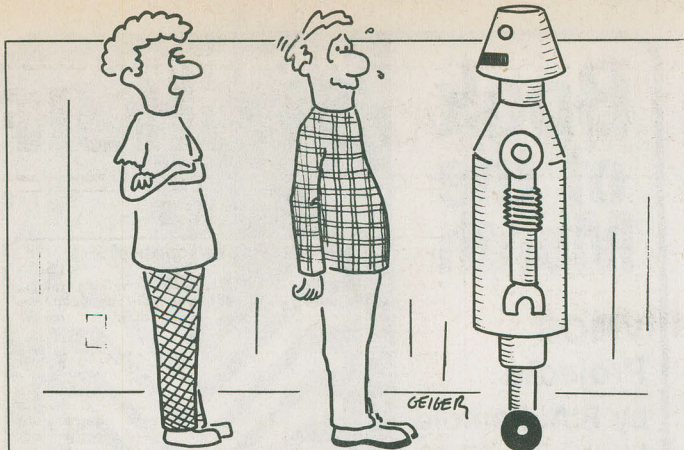

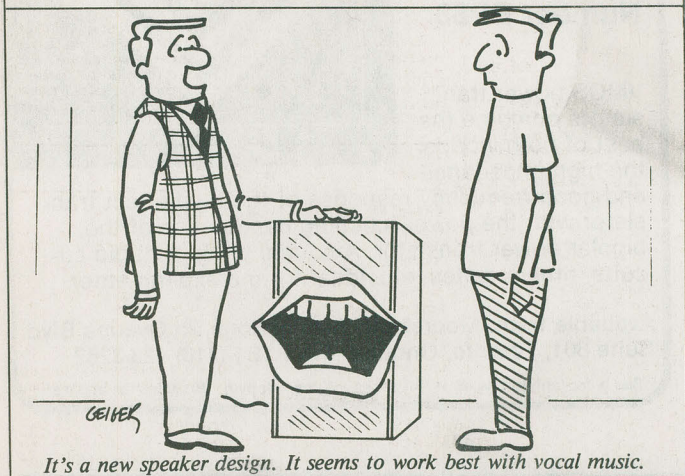Go ahead and answer his question, dear. If he's smarter and stronger than you, how come you're giving the orders?



It's a new speaker design. It seems to work best with vocal music.

ETI NEXT MONTH

Robots

Roger Allan looks at the new robotics: small, affordable robots for home and educational uses.

Model Railway Switch Controller Project

Turn out those turnouts with a capacitive discharge system that runs signal lights as well



Projects

by R.A. Penfold
List Price \$7.70

Number BP83

VMOS power transistors combine the best of both worlds: the high impedance and good frequency response of the field-effect transistor with the power handling capabilities of the bipolar power transistor. A source book of audio circuits, timers, gates, etc. Ideal for the experimenter.

Available from: Moorshead Publications 25 Overlea Blvd.
Suite 601, Toronto, Ontario M4H 1B1 (416) 423-3262

See order form in this issue. All prices include shipping. No sales tax applies.



ETI Car Ramp/Magazine Binder

It's spring again, and time to change the oil and find out what's causing that annoying rattle when the engine's idling. We know what a drag it can be, especially when your head gets stuck between the ground and the oil pan, so we're offering our incredible new ETI CAR RAMPS!

Covered in black vinyl, these amazing devices not only support up to 1 kg (2.2 lb.), they also happen to hold 12 issues worth of our magazines: Electronics Today, Computing Now!, and Special editions from Moorshead Publications. The world's top inventors were hired at enormous expense to design the spring gadget that holds the magazines without cutting or punching.

Sturdily made from the finest materials, the Car Ramp/Magazine Binder offers you a lifetime of enjoyable use, unless of course you actually try to drive your car up onto them. They're available for \$9.25 each — don't forget to specify which one you'd like — and Ontario residents, sadly, must add 7% Provincial Sales Tax. Order from:

Electronics Today Binders
Suite 601 25 Overlea Blvd.,
Toronto, Ontario M4H 1B1

Timing long periods has always been a problem because of the high leakage characteristics of the timing capacitor. This is no longer true. The XR-2240 IC is a programmable timer capable of producing ultra-long time delays without sacrificing accuracy.

THIS IC CAN generate time delays from microseconds up to five days, and with a little ingenuity can generate a delay of a couple of years! A functional block diagram of the IC is shown in Figure 1.

The circuit consists of an internal timebase generator, a programmable 8-bit counter and a control flip-flop. The time delay at the output is set by an external CR network and can be any period from $1 \cdot CR$ to $255 \cdot CR$. Herein lies the secret. The CR timebase generator can be set to give a very accurate short period, and binary multiples of this short period are then programmed and taken from the output. Each output is capable of sinking approximately 5 mA of load current.

The features of the IC are:

1. Timing from microseconds to days.
2. Programmable delays: $1 \cdot CR$ to $255 \cdot CR$
3. Wide supply voltage range: 4 V to 15 V
4. TTL compatible inputs and outputs
5. High accuracy: 0.5%
6. Excellent temperature stability
7. Period $T = C \times R$

Circuit Operation

The timing cycle is initiated by a positive-going pulse on pin 11. This trigger pulse performs three functions:

1. Activates the timebase generator
2. Enables the counter
3. Sets all counter outputs to the low state

The timebase generator produces timing pulses with a period, T , equal to $1 \cdot CR$. These clock pulses are counted by the binary counter inside the IC and the timing period is complete when a positive-going pulse is applied to pin 10 (i.e., the circuit is reset). In most applications, one or more of the output terminals are connected back to the reset input. The circuit will commence timing when the trigger pulse is applied, and automatically reset on the completion of the timing period.

Remember, the outputs are normally high and are set to low when timing is initiated, returning again to the high level on completion of the timing period.

DESIGNER'S Notebook

**Super Timer —
The XR-2240**



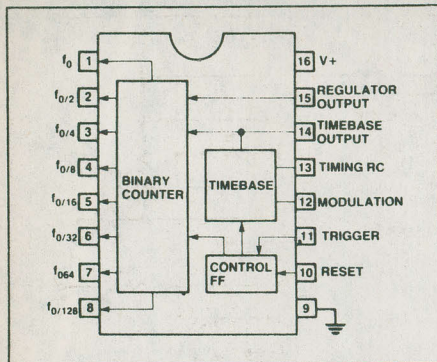


Fig. 1. Functional block diagram of the XR-2240.

Circuit Construction

The binary outputs, pins 1 to 8, are open collector and can be connected together to a common pull-up resistor. The output of the timer will be low as long as any one output is low. In this manner the time delays associated with each output can be added by simply connecting them together to a common bus. The outputs can be used individually or wired together.

For example, the output at pin 4 is $8 \times CR = 8T$. If pins 4 and 3 are connected together, the output will become $12 \times CR = 12T$.

Figure 3 shows the actual connections for a practical circuit. When the power is applied with no trigger or reset inputs, the circuit sets up to the initial state of all outputs high. Once triggered, the circuit is totally immune to any additional trigger inputs until the timing period is completed, or a reset pulse is applied.

Choice of Timing Components

Once a signal timing period, T , is

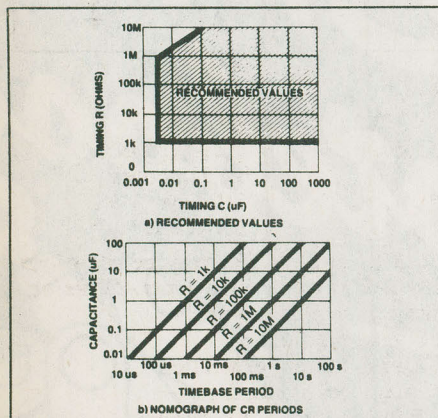


Fig. 4. Graphs to assist in the choice of values of C and R .

established, the output can be determined by 'wiring-in' periods of T following a binary progression. However, the procedure may have to be reversed when a certain accurate output period is required.

For example, if a timing period of 6 hours 30 seconds is required, first convert the time to seconds:

$$= 6 \times 60 \times 60 + 30 \\ = 21630 \text{ seconds.}$$

The maximum number of timing periods available with one IC is:

$$(1 + 2 + 4 + 8 + 16 + 32 + 64 + 128)T = 255T.$$

Therefore the period of T can be calculated:

$$T = 21630/255 \\ = 84.82 \text{ seconds}$$

With a low-loss capacitor (such as tantalum) as one timing component, R can be

$T = CR = 100 \mu F \times 1 M = 100 \text{ seconds}$		
T	Period of Output	
T	100 secs = 1.7 min	
2T	200 secs = 3.3 min	
4T	400 secs = 6.7 min	
8T	800 secs = 13.3 min	
16T	1600 secs = 26.7 min	
32T	3200 secs = 53.3 min	
64T	6400 secs = 1.8 hours	
128T	12800 secs = 3.6 hours	
255T	25500 secs = 7.1 hours	

Table 1. Example of accurate time available using the XR-2240.

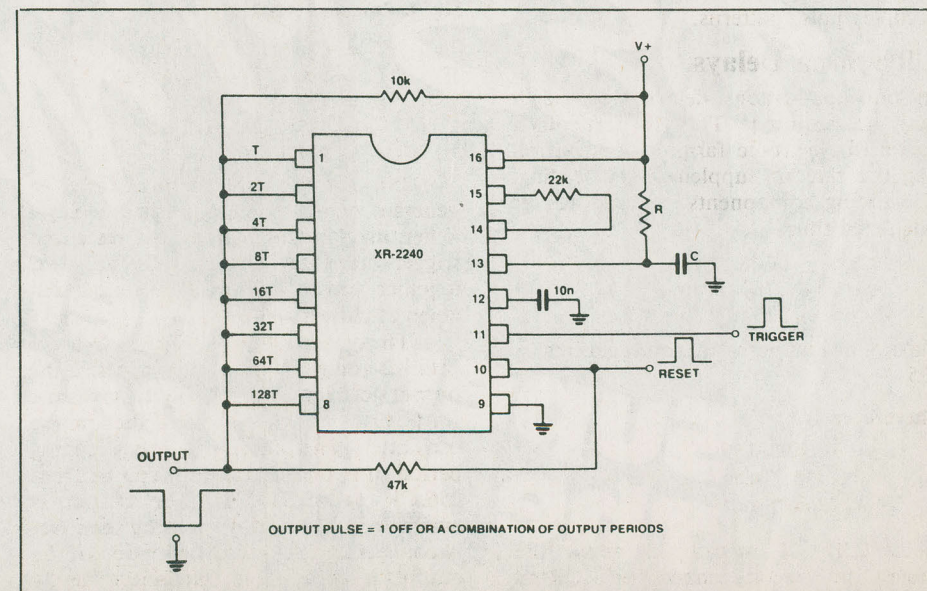


Fig. 3. Connections for a practical circuit.

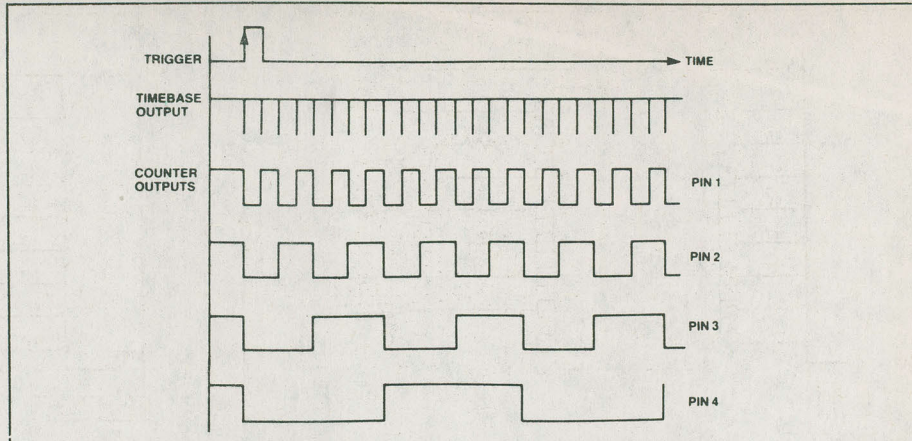


Fig. 2. Output waveforms and timing diagram.

calculated. If $C = 100 \mu F$:

$$T = CR$$

Therefore:

$$R = T/C \\ = 84.82/(100 \times 10^{-6}) \\ = 848.24 \text{ kilohms}$$

This can be tailored precisely for very accurate timing with a resistive network or potentiometer, or simply rounded off to 850k.

Figure 4 shows two graphs which will assist you in choosing:

1. The recommended range of timing component values.
2. The time period, (T), up to 100 seconds, to be expected from combinations of C and R values.

An example of output periods to be expected using a $100 \mu F$ capacitor (tantalum) and $1M$ resistor as the timing components is shown in Table 1.

The type of circuit operation discussed to this point has been monostable i.e.,

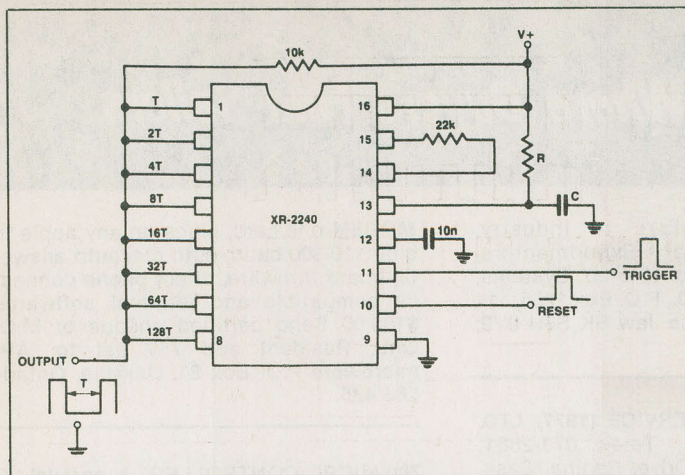


Fig. 5. Astable operation under control of external trigger and reset controls.

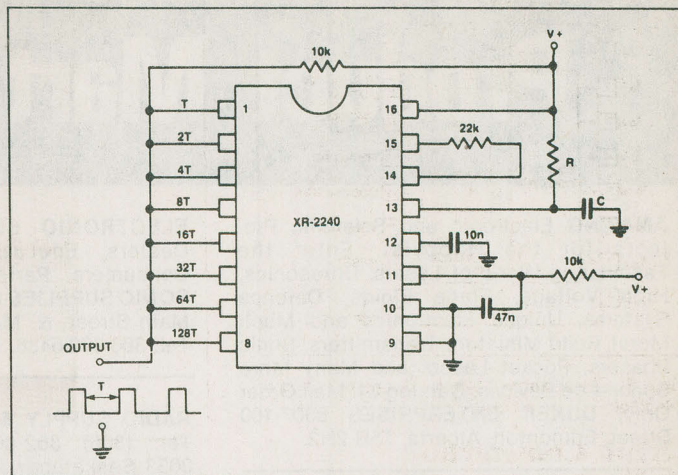


Fig. 6. Free-running circuit.

the output goes low on triggering, stays low for the timing period and returns to a high level. It will not time again until it is retriggered. An XR-2240 can also be used in a free-running or astable mode.

Astable Operation

To operate in this mode, the reset line to pin 10 is disconnected from the output.

Figure 5 shows an astable circuit under the control of the external trigger and reset signals. It will start timing when an external trigger pulse is applied, and will not stop until a reset pulse is applied.

Alternatively, the circuit can be made truly free running. The circuit in Figure 6 self-tiggers automatically when the power is switched on, and continues to operate in its free running mode indefinitely.

When the timer is used in this mode, each counter output can be used individually as synchronized oscillators, or they can be connected together to provide complex pulse patterns.

Ultra-long Delays

In some applications, delays of four days may be required. This is particularly useful in electronic farming for controlling the rate of supplementary feeding. The timing components required can be calculated thus:

$$\begin{aligned} 4 \text{ days} &= 96 \text{ hours} \\ &= 5760 \text{ minutes} \\ &= 345,600 \text{ secs.} \end{aligned}$$

Maximum number of T combinations = 255

Therefore:

$$\begin{aligned} T &= 345600/255 \\ &= 1355.3 \text{ secs} \\ &= 22.6 \text{ minutes} \end{aligned}$$

Incidentally, 20 minutes is about the longest time recommended for 1.CR as anything beyond this suffers from leakage problems.

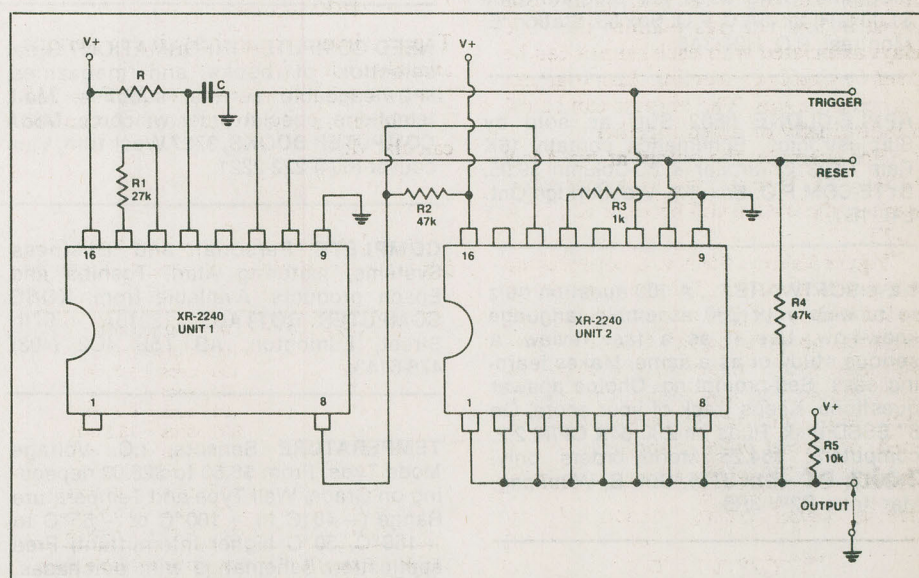


Fig. 7. Cascaded XR-2240s.

$$\begin{aligned} T &= CR \\ \text{if } C &= 500 \mu\text{F (low leakage)} \\ R &= T/C \\ &= 1355.3/(500 \times 10^{-6}) \\ &= 2M7 \end{aligned}$$

Two XR-2240 ICs can be cascaded to generate extremely long time delays. When used in this format, the reset and trigger terminals of the ICs are tied together and the timebase of unit 2 disabled as shown in Figure 7.

The output is normally high. When a positive-going trigger pulse is applied, the output goes low and stays in the low state for $(256)^2 = 65,536$ periods of the timebase oscillator. Therefore, the total timing period of two cascaded units can be from $256 \cdot CR$ to $65,536 \cdot CR$. The output is available in 256 discrete steps by selectively connecting one or a combination of the outputs from unit 2 to the output bus.

With $T = 20$ minutes an example of an ultra-long delay can be given.

$$\begin{aligned} CR &= T &= 20 \text{ mins.} \\ 65,536T &= 1,310,720 \text{ min.} \\ &= 21,845 \text{ hours} \\ &= 910 \text{ days} \\ &= 2.5 \text{ years!} \end{aligned}$$

This article highlights the use of an XR-2240 as a precision timer. Other application suggestions are:

1. Sequential timing
2. Binary pattern generation
3. Frequency synthesis
4. Pulse counting or summing
5. A/D conversion
6. Digital sample and hold

Further information on the IC can be obtained from Exar Integrated Systems or their agents (Active Component Sales).

This article was made possible by the courtesy of Exar Integrated Systems. Data was taken from their publication 'XR-2240/2340 Programmable Timer Counter.'

ETI

Product Mart *Where Buyers Find Sellers*

AMAZING Electronic and Scientific Projects for the Hobbyist. Enter the Fascinating World of Lasers, Ultrasonics, High Voltage, Force Fields, Defence Systems, Unique Electronics and Much More! Build Miniature Transmitters, Sonic Phasers, Pocket Lasers and Many More Space-Age Devices. Catalog \$1. Mail Order Only. **DUKER ENTERPRISES** 8307-160 Street, Edmonton, Alberta, T5R 2H2.

SOFTWARE evaluation club. No membership fee. Apple™ games, utilities & CP/M™ programs. Send \$8.00 per program (plus \$1.00 S/H) to: **J.A.C.** P.O. Box 83, Station 'E' Montreal, P.Q. H2T 3A5.

APPLE-CLONE 6502 Surf as sold by Surplustronics. Schematics contain 16K Ram Disc. Controller & 80-Column \$9.95. **BYTE-COM** P.O. Box 245, Woodbridge Ont. L4L 1B1.

NEW SOFTWARE . . . A 100 question quiz to tune-up your Z80 assembly language know-how. Use it as a fast review, a serious study or as a same. Makes learning easy. Self-prompting. Choice answer questions. Keeps track of your score. On 8" SSSD disk. Runs on Z80 64K CP/M 2.2. computers. \$64.25 Money-orders only. **Z-QUIZ**, P.O. Box 3775, Stn. B, Winnipeg, Manitoba R2W 3R6.

ELECTRONIC Parts and Supplies for Industry, Students and Dealer Trade. We can special order. Stereo Components, Satellite Supplies, Television, V.H.F. Radios and all Antennas. **G.W. COLOR-TRONICS LTD.**, 616 Cheadle Street, West. Swift Current, SK. S9H 3X4 Tel: (306) 773-3672.

APPLE™, Apple Clones, 6502 users. Want more out of your present 6502, then be first on the list for the new 6502 PCB. Limited quantity. Send Name, Phone, Address. No obligation. **BYTE-COM**, P.O. Box 245, Woodbridge, Ont. L4L 1B1.

AUTODIAL-CARD for Apple II+//Ile. Features pulse dialing and software supplied on modem. \$49.95 VISA/MASTER-CARD. **W.H.S. ENTERPRISES**, 34 Epsom Cres., Winnipeg, Manitoba, R3R 0X2.

ELECTRONIC Suppliers to Industry, Dealers, Educational, Experimenters, Consumers. Parts for Stereo Systems, **SONIC SUPPLIES LTD.**, P.O. Box 1265, 111 Main Street, N. Moose Jaw SK S6H 0V9, Tel: 306-692-6486.

RADIO SUPPLY & SERVICE (1977) LTD. Tel: (306) 352-8642, Telex 071-2661, 3033 Saskatchewan Drive, Regina, Sask. S4T 1H5. Distributors of Radio T.V. Electronic Parts and Industrial Components, Ham Radio Specialists.

NEED COMPUTER INFORMATION? Great selection of books and magazines, knowledgeable service, supplies. Mail, telephone, special order welcome. **MICA COMPUTER BOOKS**, 3727 West 10th, Vancouver (604) 222-2221.

COMPLETE Personal and Business Systems, featuring Atari, Toshiba and Epson products. Available from: **KOBE COMPUTER COTTAGE**, 12913A - 97th Street, Edmonton, AB T5E 4C2 (403) 478-6143.

TEMPERATURE Sensors, I.C. Voltage Mode Type. From \$5.50 to \$26.00 depending on Grade, Well Type and Temperature Range (-40°C to +100°C or -55°C to +150°C, 50°C higher intermittent) Free application Schematics with purchases. Digital Thermometer with 8 Sensor inputs and 4 Alarm positions \$125.00 **DUNDER ELECTRONICS LTD.**, P.O. Box 117, Carleton Place, Ont. K7C 3P3.

DOUBLE-SPEED '6502B' Apple II compatible motherboard, includes dual floppy interface, 64K DRAM, FP/INT ROMs, plus many extras. Build your own fast Apple or upgrade existing machine by reusing components. Blank PCB, schematics, instructions \$100.00 (certified or M.O.) **MITINA ENTERPRISES**, Box 13055, Kanata, Ontario K2K 1X3

ALARM System. Perimeter professional equipment: Sturdy control panel, battery, outside bell, contacts, wire. Everything needed. Only \$175.00 postpaid. **POLYGRAFF SECURITY**, P.O. Box 276, Sherbrooke, Que. J1H 5J1.

MODEM one card, plugs on any apple tm slot, 110-300 baud, auto dial/auto answer, on-board firmware, direct phone connect, //e compatible and terminal softwares. \$180.00 Send certified cheque or M.O., Ont., Resident add 7% pst to: **APL microware** P.O. Box 21, Oakville, Ontario L6J 4Z5.

Z80 MICRO-CONTROLLER. . . parallel I/O ports. Runs XYZ motors with encoders via keypad commands. An introduction to automation. Schematics, X-Y grid wiring lists, and software monitor in ROM, \$110.00 Source & doc on 8" SSSD disk for further software customizing via your 64K CP/M 2.2 computer, \$84.00. Do-it-yourself. Money-orders only, **Z80-CONTROLLER**, P.O. Box 3775, Stn. B, Winnipeg, Manitoba R2W 3R6.

DATAPORT COMPUTER CENTRE, P.O. Box 3607, 712 Main Street, Melfort, Sask. S0E 1A0 Tel: 306-752-5577. Specializing in Business and Home Software and Hardware — Corona — Franklin-Hyperion, and Altos Computers, Epson, Okidata, Daisy Writer Printers.

TRS-80 OWNERS. IBM COMPATABILITY with MICROMERLIN. 128K RAM, MS-DOS or CPM-86. Run DBII, Wordstar, etc. Need TRS-80 with one DD/SS. Simple plug-in. Really works! \$1495.00. MDX disc drive upgrade. One DD/DS \$699. Two DD/DS \$1099. **JRT**, 1192 Bucke St., London, Ontario, N5Y 3S3, 519-451-3154.

FOR \$10 per kit \$2 handling, receive free flyer and any of the following. #1: 1000 asst'd pcs, choke - capacitor - resistor - transistor - hardware - etc. Capacitor specials: #2: 200 asst'd ceramic - #3: 100 asst'd silver mica - #4: 100 asst'd mylar ! #5: 50 asst'd tantalum - #6: 50 asst'd electrolytic - #7: 50 asst'd feed-through - #8: 50 asst'd metallic silver mica (Elmenco) - #9: 25 asst'd variable. All new material. Unconditional guarantee. **SURPLUS ELECTRO QUEBEC**, 2264 Montee Gagnon, Blainville, Quebec J7E 4H5.

AUDIO Kits: graphic equalizers, 12-24 bands/channel \$89-200 (U.S.); noise filters, many others — **SSS 856T** Lynnrose, Santa Rosa, CA 95404, U.S.A.

Advertising in the **Product Mart** section allows you to reach over 30,000 Canadian readers nation wide for \$1.00 per word (minimum 25 words). Please contact us for further details on the various sizes and styles available. Moorshead Publications, Suite 601, 25 Overlea Blvd., Toronto, Ontario M4H 1B1, (416) 423-3262

FREE COMPUTER SOFTWARE CATALOGUE. Save \$\$\$\$ by Direct Mail on Flight Simulation, Games, Trivia, Educational and Home/Business Software for your Apple, Atari, Commodore-64, VIC-20, IBM. **THE SOFT WAREHOUSE**, Dept. 14, P.O. Box 1983, Winnipeg, Man. R3C 3R3.

8088 BOARD IC's. Plus more at competitive prices. New price list free. HN482764(300NS) — \$10.00. **M.O. ENTERPRISES**, Box 2066, Bramalea, Ont. L6T 3S3

PAY TV Descramblers. Manuals and PC's for all types used in Canada. Send self-addressed stamped envelope for free details. **STEEL CITY ELECTRONICS**, Box 887, "A", Hamilton, Ont., L8N 3P6.

CARDINAL INDUSTRIAL ELECTRONICS, 10-5920-11 Str. S.E. Calgary, AB. T2H 2M4, Canada's foremost Electronic Supply House. Featuring quality product lines in every category of Electronics. Tel: (403) 259-6817.

DIGITAL Logic kits. Each one builds on previous. Introductory package includes wire-wrap tool, wiring board, IC's, hardware, manual and more. Send \$37.95 + \$3.00 P&H for package or \$1.00 for more info. **LAMANTIA PRODUCTS**, P.O. Box 690, Lindsay, Ont. K9V 4W9

J&J ELECTRONICS Ltd., P.O. Box 1437E, Winnipeg, Manitoba R3C 2Z4. Surplus and Semiconductor Specialists. Do you get our bargain flyer? Send \$1.00 to receive the current literature and specials and to be placed on the mailing list for future publications.

APPLE™ builders need "APPLE-SEED" I-MOTHERBOARD ASSEMBLY MANUAL, \$9.95: for the novice; simple-to-follow guide to assembling the 6502. II-PERIPHERAL CARD ASSEMBLY MANUAL, \$12.95: parts list, component layout, instructions for assembling fifty peripheral cards. BOTH MANUALS ONLY \$21.00. Send cheque or M/O to **NuSCOPE ASSOCIATES**, P.O. Box 742, Stn. B. Willowdale, Ont. M2K 2R1.

1984 WORLD RADIO-TV HANDBOOKS \$23 + \$2 S&H, WSI 1984 Catalogue, \$2.00, **WSI RADIO**, Box 400, Kitchener, Ontario N2G 3Y9.

TEST-EQUIPMENT. High quality reconditioned Tektronix, H.P., scopes, generators, analysers, etc. \$50 ± \$5000. Calibrated to original specifications. Free illustrated catalogue **ALDONIC** Box 2980, Dept. ETI, Ottawa, "D", Ont. K1P 5W9.

TI-99/4(A) OWNERS! — We offer a fine variety of original games on cassette. Send for free list. **GIGO SOFTWARE**, P.O. Box 673, Niagara Falls, Ontario L2E 6V5 Canada.

MUSIC SYNTHESIZER & accessories for your Apple — digital oscillator, interface card; hardware & software compatible with Soundchaser & alphaSyntauri systems. 61N keyboards from \$195. Write for list. Dealer inquiries invited. **CLASSIC ORGAN CO.**, 300-12 Don Park Road, Markham, Ont. L3R 3A1 (416) 475-1263.

Product Mart *Where Buyers Find Sellers*

NAME _____ COMPANY _____

ADDRESS _____

CITY _____ PROVINCE _____

POSTAL CODE _____ TELEPHONE _____

NO. OF WORDS _____ AMOUNT ENCLOSED _____

Please print the following in the next available issue of ☐ **ELECTRONICS TODAY**, ☐ **COMPUTING NOW**,
or ☐ **BOTH**. My cheque is enclosed. SIGNATURE _____

NOTE: A 3 line heading can be added to your advertisement for \$30. Also, the whole advertisement can be reversed for effective presentation also for \$30.

VLFs and the Magnetosphere

A process of wave interaction in the magnetosphere can amplify very low frequencies.

by Roger Allan

THE PROCESS of dumping electrons from the magnetosphere into the ionosphere goes on all the time and is a mechanism that helps maintain the equilibrium of the radiation belts, particularly the Van Allen belts, which surround the earth. The dumping process is due to natural processes and transmitted waves from the ground. Very often, high-power transmitters induce over half of the wave energy that exists in the magnetosphere. This process, known as field-effect/wave interaction results in the deflection of free electrons from the magnetosphere down into the ionosphere in a process identical to that caused by sunspot activity. When the freed electrons enter the ionosphere they create a miniature aurora borealis — small light emissions — that can be detected. In addition, it is felt that X-rays are released which should be discernable.

For some years, scientists have believed theoretical calculations which indicated that such ground based generation of Very Low Frequency (VLF) radio waves could result in these waves not only being transmitted thousands of kilometers but also amplified by the dumping process.

Acting under the sponsorship of the U.S. Office of Naval Research, Lockheed Palo Alto Research Laboratory and Stanford University recently released the results of an experiment, known as SEEP (Stimulated Emission of Energetic Particles), which indicates that such a process in fact takes place, and further, that the amplification produced by the dumping process increases power factors by between 1,000 and 10,000 times (30-40 db).

The discoveries of this research program could lead to the improvement of radio communication by using magnetic field lines to capture and amplify VLF





Part of the SEEP experiment carried aboard the S 81-1 satellite. Circular objects in the foreground are thermal radiators, used as part of the cooling system for the electron sensors which must operate at low temperatures for best sensitivities.

radio waves by utilizing that very large volume of space surrounding the earth that up until now hasn't been fully explored for its communication potential. Further, it provides a basis for improved minimization of deleterious heavy sunspot activity throughout the world.

Essentially, the experiment used a 1-Mw U.S. Navy VLF transmitter at Cutler, Main, Annapolis, Maryland and Jim Creek, Washington (used to com-

municate with submarines), and a 4 kw transmitter operated by Stanford University for the National Science Foundation at Siple, Antarctica, along with detectors mounted on the S 81-1 satellite — part of the USAF Space Test Program. Further, other satellites, specifically the Dynamics Explorer 1 and the International Sun-Earth Explorer flying at a higher altitude than the S 81-1, also carried VLF receivers to measure the intensity, frequency and

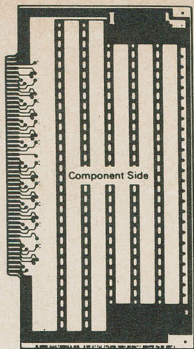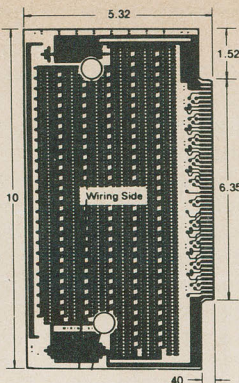

S100 Universal
Microprocessor Board

Designed to be compatible with the
S100 Microprocessor Bus System

For the Professional Amateur

Vero can offer a complete package to
help you build your product to a
truly professional standard.

Full range of veroboards,
accessories and
housings.

BICC

vero



Electronic Packaging Systems Limited
P.O. BOX 481, 613 O'CONNOR DRIVE
KINGSTON, ONTARIO, K7L 4W5
TELEPHONE 613-384-1142 TELEX: 066-3243

Circle No. 5 on Reader Service Card

Advanced PAL & EPROM CAD System

- PAL & EPROM programming system
- Program PAL's from standard logic equations
- On line manual available at all times
- Full screen editor for entering PAL equations
- Interactive PAL logic simulator
- Standard PAL assemblers for 20 & 24 pin PAL's
- Programs MMI, NATIONAL, TI, AMD PAL devices
- Programs all 5-volt JEDEC pin-out EPROMs (2716 through 27256)
- Uses new fast programming algorithm for larger EPROMs (2764 to 27256)
- New devices can be added to library through software updates
- Allows user to blow verify-protect fuse for PAL design security
- Includes card, diskette and external box with Zero Insertion-Force sockets

Requires IBM® PC® or XT® with 128k, 1 drive
Compatible with all PC DOS releases

\$659.00

PROGGER by
Locust Computer Systems Corporation
622 Gladstone Avenue
Ottawa, Ontario
CANADA K1R 5P4 (613) 235-2294

send \$3.00 for demonstration diskette
Ont. res. add you-know-what for you-know-who.

© IBM, PC and XT are registered trade marks of IBM Canada Ltd.

Circle No. 18 on Reader Service Card

BIPLEX SYSTEMS INC.

4 Osmund Court, Willowdale Ontario M2H 1P6
Tel: (416) 491-3162

10% OFF FOR ALL P/O BEFORE JULY 31, 1984

Look at our Low Price Special
for your "FRUIT" Computer!!

	128K	8088
Bare Board	19.95	26.95
Full Kits	160.00	call
Assembled		
& Tested	199.50	call
Proto-Board		8.50

Power Supply Special
(Limited Qty.)

Output: +5V 25A, +12V 6A,
-12V 6A, -5V 4A,
DIM. 38x12.50x6.50cm
Only \$139.50
9 Pin Sub-D Connector
(FEMALE) For Only \$3.00

Voltage Regulator

78M08	0.85
78M12	0.85
78M15	0.85
78L12	0.70

Linear

TDA2002A	3.50
TDA1190Z	4.50
uA3089	1.95
uA739	0.79
uA741	0.29

8088
8031
8251

4116	16K Dram 150NS	1.50
4164	64K Dram 150NS	8.00
2764	64K Eprom 450NS	11.50
27128	128K Eprom 450NS	37.95

MAN2815	8 Digit Alpha-Num. Display	call
DL1414	4 Digit Alpha-Num. Intelligent	call
TIL311	7 Segment Display	5.00
MM5387	Clock LSI	4.50

Mail Order Only

Send Cheque or Money Order (Allow 2 weeks for personal cheque).
Min. Order \$10.00 Add 5% for shipping and handling. Ontario
Residents Add 7% P.S.T.

Price subject to change without notice.

Call For Quantity Discount

Circle No. 9 on Reader Service Card

EMP MODEMS



Available
in
September

- Bell 103/212A compatible
- interface: EIA RS232C
- 0 to 300/1,200 bps Full Automatic

- Full duplex, Auto dialer, Auto-answer
- compatible, IBM and most personal computers.

Modem MM101 only \$89.95

- 300 Baud - Full Duplex • Bell 103 compatible • Direct connection between microcomputer and telephone.

We also feature EMP Telephone products (Hand-held models — Emergency models — Cordless models) Sales Agents for ELEC PCB Boards, Multi layer — double and single sided.

DISTRIBUTORS AND DEALERS

INQUIRIES WELCOME

MARK GEE ENTERPRISES LTD.

P.O. Box 249, Station "G", Toronto, Ont. M4M 3G7

Tel: (416) 862-8887

Telex 06-218808


Mail Orders:

Send certified cheque or money
order, plus \$5.00 for shipping
and handling. Ont. residents
add 7% P.S.T. to


MCS MICROTRONICS INC.
483 Queen St. West,
Toronto, Ont. M5V 2A9

Circle No. 1 on Reader Service Card

VLFs and the Magnetosphere

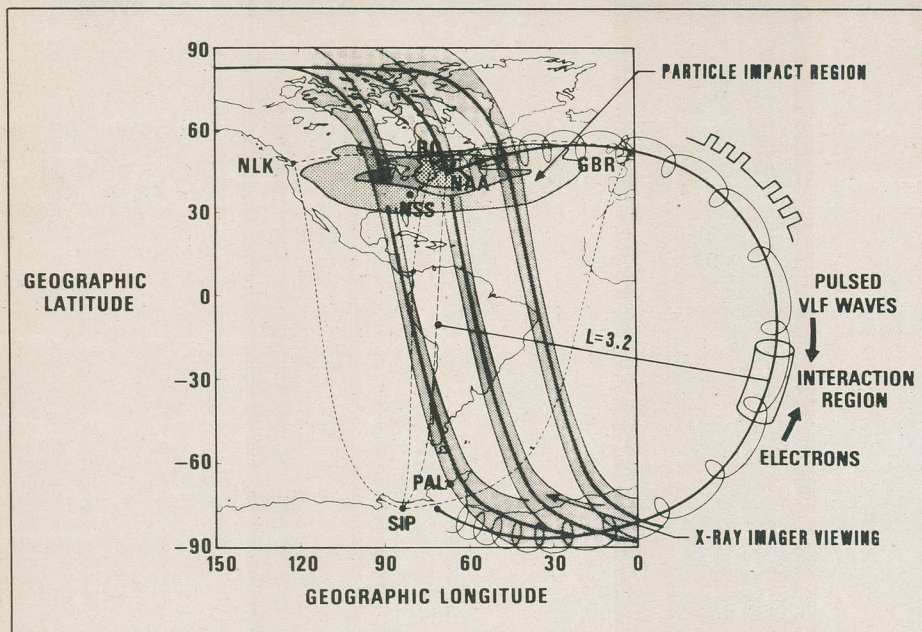

Location of high-power VLF Transmitters used in the SEEP experiment, along with a schematic representation of the interaction between pulse-coded very low frequency waves and the electrons spiralling around a magnetic field line connecting the Earth's northern and southern hemispheres. The high-power transmitters were turned on when the satellite was traversing regions (shaded areas) through which the displaced electrons moved. The interaction region marked in the diagram is at an altitude of approximately 8,500 km.

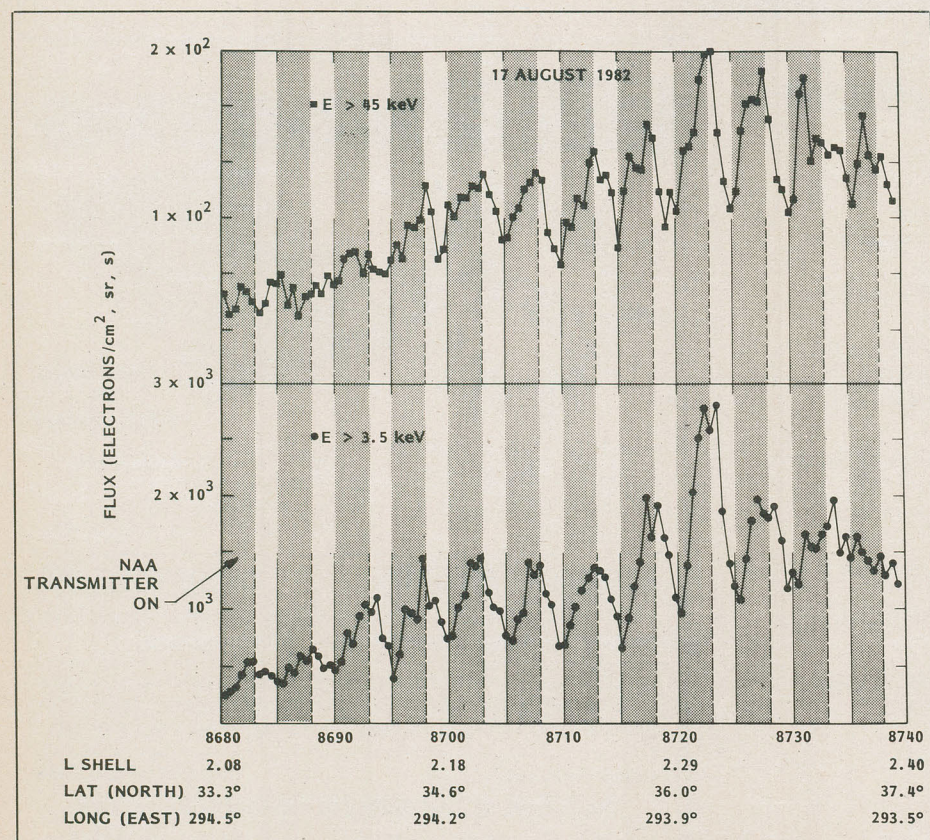

Example of Modulated Electron Beams

modulation timing of the transmitted waves above the interaction region — with such data being recorded at Siple and Palmer Antarctica, and Roberval Quebec, to correlate the data.

The transmitters were modulated in ten different on-off patterns, and evidence was sought in the output of cooled silicon detectors on board the S 81-1 while it was in low orbit of approximately 250 kilometers while the satellite was passing under a region exposed to interactions initiated by one of the four ground stations. Analysis shows that, for example, using a 3-sec on, 2-sec off format results in a 32 db increase in power, the amplification being due to the magnetosphere.

In addition to the particle detectors, the S 81-1 also carried an airglow photometer and X-ray mapping spectrometer to record expected side effects resulting from collisions between the displaced electrons and the constituents of the atmosphere. No data was generated in this part of the experiment due to an apparent lack of sensitivity on the part of the equipment.

While the experiment was deemed a success, several questions remain, such as why amplification seems to occur only at certain times, and how the waves penetrate the ionosphere and enter the magnetosphere. These sorts of questions may be answered by two follow up experiments. The first, involving what was originally known as the Waves in Space Plasmas (WISP) instrument, now known as the RPD (Particle Interactions Recoverable Plasma Diagnostic Package), is currently under development by the Centre for Research in Experimental Space Science (CRESS) at York University in Toronto. Expected to be launched on the Shuttle as part of the Spacelab 6 mission in 1986 or 87, it will be used to study the effect of radio waves in the frequency of 0.3 MHz to 30 MHz on the Earth's ionosphere and magnetosphere. A second experiment, also under development by CRESS for the same Spacelab 6 mission, known as the Energetic Ion Mass Spectrometer (EIMS), may also answer some of these questions. It will allow scientists from the Herzberg Institute of Astrophysics in Ottawa to investigate the properties of charged ions and molecules in the earth's atmosphere. By taking advantage of the large weight carrying capacity of the Shuttle, EIMS will have a sensitivity and precision far superior to those of previous space-borne instruments. It will be used to measure the composition and energy distribution of ion species occurring naturally in the magnetosphere as well as tracer ions injected as a result of other NASA experiments.

ETI


Armstrong

Few of us are aware of the enormous contribution Edwin Armstrong made to the development of radio. Sadly, like many famous inventors, he was bedevilled by legal wrangling over his patents.

THERE'S A VERY hallowed place in radio history not far outside New York City. After you escape from the confusion of Kennedy Airport, you cross the George Washington Bridge and take the green and pleasant Palisades Parkway, which points you towards upper NY State. Not far out, yet in wild, forested country, you'll see a transmitting aerial. Ask, and you'll be told that it is Edwin Armstrong's radio station.

Edwin Armstrong was born in Manhattan, New York, in 1890. His folks were well-to-do: his father a publisher, his mother a former schoolteacher, and between them they fostered in their son a fascination for the mechanical and electrical gadgets with which he was constantly surrounded. The turn of the century in New York was the age of the inventor. A steady stream of inventions were being registered at the US Patent Office, and each was eagerly seized on to be marketed and advertised. In many ways it was an inventor's paradise, but as many were to find out, the paradise had a few traps in it. Young Edwin caught the mood and at the age of 14, decided that he would be an inventor. The newest thing around was radio, and it was this field that Edwin chose, surrounding himself with coils and crystals, earphones and morse keys.

We know very little of what he did in those days, because like many inventors, he was shy and secretive. The next milestone in his career was his entry to Columbia University to study science and engineering — and to chalk his name on the list of radio pioneers long before his studies were complete. Radio at the time (about 1910) had very limited uses, mainly because of the very low sensitivity of receivers. Lee de Forest had just invented his Audion, a three electrode tube of the type we now call a triode, and this permitted some amplification of the feeble signals from a tuned circuit. At university, Armstrong, was able to lay his hands on one of the first of these tubes, and to start making use of it. Within a few months, he had made one of the major discoveries in radio, that of positive feedback.

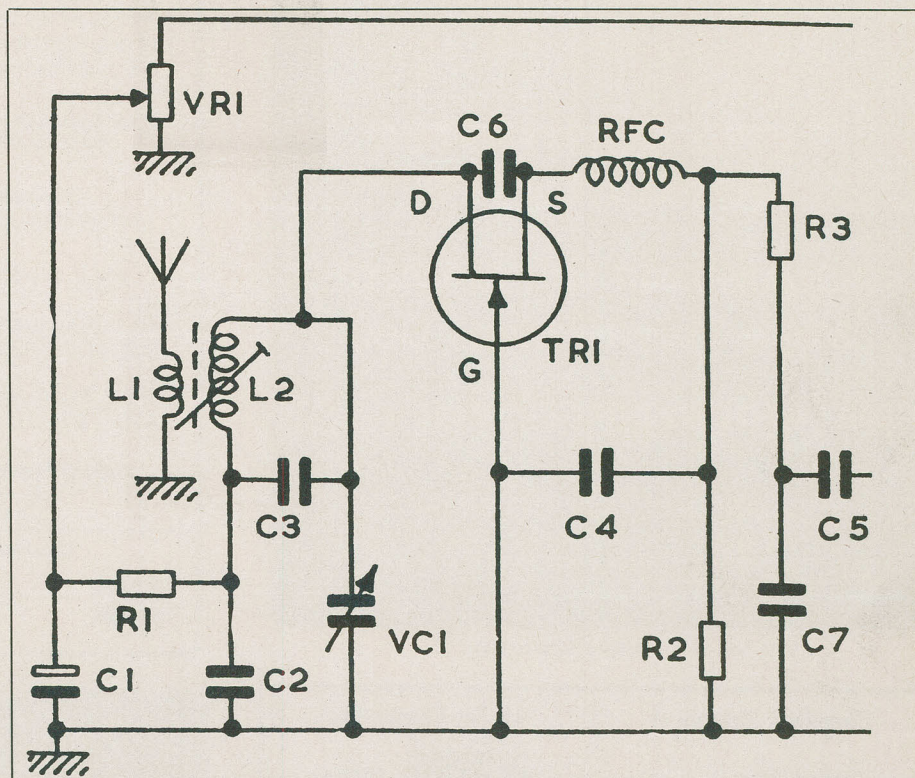

A modern FET superregenerative receiver similar in operation to Armstrong's circuitry. VR1 controls the regenerative effect, increasing the gain by using positive feedback.

First Milestone — Regeneration

The idea was simple enough. The primitive tube had a very low gain at radio frequencies. Armstrong hit on the idea of feeding the signal back to be amplified again, and he called the idea regeneration. A regeneration receiver was hundreds of times more sensitive than the average receiver of the day, so that Armstrong's invention was undoubtedly one of the milestones in radio progress. It was immensely successful and every radio, from then on, with any pretensions to sensitivity, incorporated regeneration. Armstrong himself had already found out that excessive positive feedback could cause oscillation, and so paved the way for all electronic radio transmitters to replace the crude spark-coil or alternator types which were then used.

It could have, and should have, been the moment of his greatest triumph, but it was soured in a way that was to haunt him for the rest of his life. His patents were challenged by de Forest, and the judges and lawyers, ignorant of the principles involved, ruled that Armstrong's patents were invalid. To its great credit, the scientific community

never accepted the legal judgement, and recognised Armstrong with every honour they could bestow. Many inventors from that day on, however, have regarded patent rights as a playground for lawyers and have preferred to get in first with the manufacturing of an invention rather than trust to their ability to profit from licensing agreements.

Second Milestone — The Superheterodyne

At the outbreak of war in 1914, Armstrong was appointed to the US Army Signal Corps to research into improved radio communications. Details of his work are not easy to obtain even now, because of the secrecy which surrounded the 'back-room boys', but one invention of this period is outstanding, and will probably remain so as long as radio is used. Until then, all radio receivers were either crystal sets, using no radio frequency amplification, or tuned radio frequency (TRF) receivers which used coils and capacitors to tune each amplifying stage to the frequency which was being received. TRF receivers are useful up to a point, but they have great

Need Test Equipment?

We Have It!

**We Are Different. We Specialize.
Outstanding Price!
Teach You How To Use It.**

**2 yrs. Guarantee
Good Stocks**

**Satisfaction Guaranteed!
We're Very Serious. Call.**

TRADEPORT ELECTRONICS

1179 Finch Ave. W. #11 Downsview, Ont. M3J 2G1

MEASUREMENT IS OUR BUSINESS

Tel: (416) 736-0866

TLX 06-217828 TRDPRT TOR.

DEALER INQUIRIES INVITED

Circle No. 23 on Reader Service Card

Complete System +



for
\$875.00

• Fully AppleTM compatible • 48K memory • Disk drive • Disk controller card • Upper/lower case • Hi-res Amber monitor • Color graphics • 90 days warranty

Complete System Model 2200



for
\$999.00

• Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • 80 or 40 column soft switch • controller card • disk drive • Hi-res amber monitor • color graphics • detachable keyboard • 90 days warranty

I.B.M. Compatible



ECS1
\$1895.00

• 8088 processor • optional Intel 8087 numeric coprocessor • 64K memory exp. to 256K on board • double sided double density disk drive • detachable keyboard • colour-graphic board • support IBM® software • 90 day warranty

ECS2 Systems



\$1195.00

• Fully Apple // compatible • dual processor 6502 and Z80 • 64K RAM • 24K ROM • controller card • disk drive • Hi-res lilt amber monitor • color graphics • detachable keyboard with special function • 90 days warranty

ELECTRONIC CONTROL SYSTEMS

1890 Meyerside Drive, Mississauga, Ontario L5T 1B4
(416)673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

Circle No. 6 on Reader Service Card

COMPUTER ORDER INTERNATIONAL

*Canada's most convenient source for
computer hardware & software.*

WHY ARE YOU

- ordering from the U.S. when prices are cheaper here?
- paying higher prices just because you live outside a major city?
- waiting weeks for your order to arrive?
- paying expensive shipping costs?
- being charged extra for using credit cards?

WE OFFER . . .

FREE QUICK DELIVERY ANYWHERE IN CANADA. NO PENALTY FOR USING CREDIT CARDS. UNBEATABLE PRICES.

WE CARRY . . .

- Thousands of programs for most machines.
- Peripherals (printers, modems, monitors, drives, cards)

AND MUCH, MUCH MORE.

. . . and if we don't stock what you want, we can special order it!

GRAND OPENING SPECIAL

- NASHUA DISKS SS/DD IN LIBRARY CASE . . ONLY \$25.95
- BUF-PRINT 32 32K buffered parallel in/f. card w. cable ONLY \$159.00
- T.E.O. Px-80 dot matrix printer ONLY \$419.95
- ATOM AT-1 1/2 height disk drive (Apple comp.) ONLY \$299.95

...AND REMEMBER, FREE DELIVERY CANADA WIDE!

Product Shipped within 48 hrs. on receipt of order
Circle Reader Service Card for our free catalogue

Corporate, Educational and Dealer Enquiries Invited.



Post Office Box 36,
Station W, Toronto, Ontario
M6M 4Y9 (416) 633-8681



Circle No. 25 on Reader Service Card

BRUNELLE presents THE Commander SERIES Model 4060 Digital ALL THAT THE NAME IMPLIES

The Multimeter you've been waiting for...
at the price you've been hoping for!

\$99.00

- Handheld 7-function, 35 ranges with 200 uA AC and DC. Hi-low ohms diode check.
- Built-in transistor test function.
- Overload protection. 2 amp fuse protects all meter ranges.
- Safety designed input jacks and test leads, tilt stand for bench use. Easy external battery access.
- Calibration certificate traceable to NRC supplied with meter.
- 1 year parts/labor guarantee.

SEE IT, TEST IT, COMPARE IT!

BRUNELLE INSTRUMENTS INC.

826 Belvedere St., Sherbrooke,
Quebec. J1H 4B8
1-819-569-1335 Telex 05-836266

Mail Orders accepted: Send certified cheque or money order. Quebec residents add 9% P.S.T. add \$3.00 for shipping.



Circle No. 17 on Reader Service Card

disadvantages when large amounts of gain are needed. One disadvantage is that the tuning of each circuit has to be changed whenever a different frequency is wanted. Another is that even very small amounts of signal, if fed back from the output to the input, can make the receiver oscillate and so radiate interference. All this was solved by Armstrong's invention of the superheterodyne (superhet) receiver.

In a superhet receiver, each incoming frequency is tuned, amplified and then converted to an intermediate frequency (IF) by mixing it with a signal from an oscillator. The same IF is used no matter what the input frequency on that particular range happens to be. Tuning becomes easier because there are fewer variable tuned circuits, feedback is less of a menace because the signal which is most likely to feedback (the IF) is not at the same frequency as the input. It's difficult nowadays to imagine radio without superhet receivers: from the pocket transistor radio right through to the mighty radar receiver, all use Armstrong's superhet principle.

This work earned Armstrong more than fame. During the 1914-18 war, he had met David Sarnoff, founder of the Radio Corporation of America. (Armstrong had, in fact, married Sarnoff's secretary). Sarnoff was utterly convinced of the entertainment possibilities of radio, and he bought many of Armstrong's patent rights. In the

early twenties, the sudden blossoming of radio as an entertainment medium meant a boom in radio manufacture, and made Armstrong a dollar millionaire because of the royalties which were paid by radio manufacturers.

Third Milestone — Frequency Modulation

Despite his new wealth Edwin Armstrong remained withdrawn, and continued to work at Columbia University. His theme now was the elimination of radio interference, a topic which was to occupy him to the day he died. His work was fruitful: in 1933 he took out patents on the frequency modulation system — FM. The idea of modulating the frequency rather than the amplitude of a radio wave makes it possible to design receivers which are completely insensitive to the amplitude modulation caused by interference. At the time, though, only the Army Signal Corps really saw the usefulness of FM. Armstrong found himself with an uphill struggle to convince even his friends that his new system was capable of providing broadcasting of a quality totally unknown at the time. He began the construction of an FM transmitting station, using his own personal wealth. It swallowed over \$300,000 and was completed in 1939 — just in time for the wartime economy drive to make it

out of the question to operate the station, or for manufacturers to switch to making FM receivers. Frequency modulation was to prove its value in World War II, however, and once again, Armstrong worked in military research projects.

After the war, FM started to be accepted slowly. The problem was mainly cost, and what boosted sales more than anything else was the new craze for hi-fi which suddenly brought in its wake an appreciation of better quality radio broadcasting. These could have been the days of triumph for Armstrong, but the nightmare which had haunted him from his early years was to recur. Once again, his patents were challenged in the courts, and he was put under the strain of trying to prove technical points to an audience of people who were technically ignorant and antipathetic to the quiet unassuming inventor. To add to his worries, his vast expenditure on FM was not yielding him any return, and in 1954, with his fortune spent and his brilliant invention being tossed about the courts by lawyers, Edwin Armstrong committed suicide.


He left behind him a monument as vast as any man can ever hope for. Every radio receiver and every FM transmitter in the world is the result of Edwin Armstrong's patient and little-publicised achievements. Only his name deserves to be better known.

ETI

AUDIOVISION

COMPUTING/ELECTRONICS

MAIL ORDER: Certified cheque, money order, VISA or Master Card plus 5% delivery charge. Ontario residents add 7% P.S.T. We send Canada Post, or Purolator freight collect.



6502 COMPUTER SYSTEMS

PACKAGE 1: \$949.00 **PACKAGE 2: \$1,550.00**

- 64K Computer with Multi-Function Keyboard, Upper/Lower Case and Numeric Keypad
- Disk Drive (Shugart)
- Controller Card
- Zenith 12" Green or Amber Monitor
- All items in package 1.
- Z80 Card.
- 80 Column Card
- Gemini 10X Printer
- Parallel Printer Card with cable

PACKAGE 3: \$1,700.00

- Same as package 2 but with IBM look-alike case and Multi-Function detachable Keyboard


(We send Computer Systems via Purolator Freight Collect)

ACCESSORIES

1. 128K Card \$195.00	8. Delux Self Centered Joystick 45.00
2. 300 Baud Modem 155.00	9. Disk Drive (Quentin) 299.00
3. Talk Card 40.00	10. Disk Drive (Shugart) 259.00
4. Musician Card 155.00	11. Light Pen System 225.00
5. RS232 Card 70.00	12. Graphic Tablet 109.00
6. RF Modulator 15.00	13. Nashua Diskette, SS/DD 25.00
7. Joystick (Self-Centered) 20.00	

ELECTRONIC KITS

DIGITAL DESIGNER FOR COMPUTER TECHNOLOGY

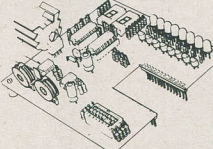

Supplies all necessary signals, voltages and read-outs to design or construct any digital circuit.

Kit \$54.95

REGULATED POWER SUPPLY KITS

(Transformer not included)

Variable Voltage:

0-15V, 5A. **Kit \$14.50**

0-35V, 3A. **Kit \$14.50**

Variable Voltage & Current

0-50V, 0.5-3A. **Kit \$21.50**

SUPER FM WIRELESS MIKE

Complete unit fits into a plastic cigarette case. Picks up and transmits sound up to 300 ft. through a FM Radio

Kit \$9.50

SOUND/LIGHT ACTIVATED SWITCH

Selectable Sound/Light Control. Works as an On/Off switch activated by intensity of light or sound. Can control up to 200 watts.

Kit \$11.50

ELECTRONIC CLOCK

Green Led Display with dual tone alarm. Runs on 12VDC (0.2A) or 18VAC.

Kit \$19.50

COLOR ORGAN/LIGHT CHASER

Features variable speed 3 sequence light chaser, or direct hook up to speaker as color organ for Control up to 1500 watt lights.

Kit \$79.50

TELEPHONE CONVERSATION RECORDING UNIT

Easy hook up to Telephone and Recorder for automatic recording of telephone conversation. No battery required.

Not A Kit \$14.50

LOGIC PROBE

For Quick servicing and checking of integrated logic system. Features unique Multi-Lamp readouts, pulse detection, and input overload protection. Max. input Freq. display: 30 MHz. Min. detachable pulse width: 20 ns.

\$29.50

LOGIC PULSER

Allows injection of pulses into circuit nodes without cutting traces, removing ICs; and monitoring circuit response with a logic probe.

\$33.50

DESOLDERING TOOL

Makes parts removal from PC Board a Breeze.

\$14.50


I.C. EXTRACTION TOOL

Extracts all LSI, MSI and SSI devices from 8 to 40 pins.

\$2.50

1984 Catalogue

\$1.00

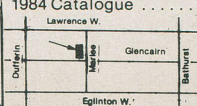

MINI-DRILL WITH STAND

Operates on 4 penlite batteries or a AC adaptor (6-12V, 2A)

Speed 2200 RPM
Ideal for Drilling and Grinding P.C. Boards, Aluminum and Copper Sheets.

\$45.00

POWER TRANSFORMERS

110VCT, 0.5A	13.50
64 VCT, 0.5A	8.70
30 VCT, 2A	9.50
18VCT, 3A	12.50

TRANSISTORS

MOSFET 2SK134	\$12.95
MOSFET 2SJ49	12.95
MJ15003	6.50
MJ15004	6.50
2N3055	1.45
MJ2955	1.45

ELECTROLYTIC CAPACITORS

10,000 MFD 50V	\$ 8.50
10,000 MFD 80V	15.00

BOOKS

Apple II & IIe User's Guide	\$17.50
Apple II Circuit Description	27.00
DOS Manual	15.00

RACK MOUNT CABINETS

Black Anodized Aluminum Front Panel with Steel Box, Hardware, Ventilation Slots and Instruction.

Panel Size (inch)	Box Size (inch)	Price
19 x 7	17 x 6.5 x 12	\$43.50
19 x 6	17 x 5.5 x 12	42.50
19 x 5	17 x 4.5 x 12	38.50
19 x 4	17 x 3.5 x 12	38.50
19 x 3	17 x 2.5 x 10	33.50
19 x 2.5	17 x 2 x 10	32.50
17 x 6	15.5 x 5.5 x 9	37.50
17 x 4	15.5 x 3.5 x 9	32.50
17 x 2	15.5 x 1.5 x 9	30.50
12 x 6	11.5 x 5.5 x 7	26.50
12 x 4	11.5 x 3.5 x 7	22.50
12 x 2	11.5 x 1.75 x 7	21.50

While Audiotapes for Cabinets \$2.50

EASTERN CANADA
578 MARLEE AVE.
TORONTO, ONT. M6B 3J5
TEL: (416) 781-3263

WESTERN CANADA
P.O. BOX AMF23581
VANCOUVER, B.C.
TEL: (604) 271-7539



New Printers

Centronics Canada Inc. has announced the new Horizon series of high-quality dot matrix printers for small systems and personal computer applications. Two models are currently available. Model H80 is a 160 cps dot matrix printer, with paper handling ability that includes fully adjustable tractors, A4 cut sheet for letters, single part roll paper and a true typewriter-style font plus interfacing

capability with most other IBM PCs and popular personal computers. Model H136 is a wide carriage printer with a 15.6 inch print line capable of printing 156 characters at 10 cpi. In the condensed print mode, 266 characters per line can be printed, satisfying the widest of spreadsheet applications. Centronics Canada Inc., 5170B Timberlea Blvd., Mississauga, Ont., L4W 2S5.

Circle No. 50 on Reader Service Card

Looking for another source of wire and cable? Amecan Industries stock audio cable, station wire, communications cables, various hookup wires, high voltage cables, cords and more. They have an outlet in Montreal at 4747 Bourg St., St. Laurent, Que. H4T 1H9, and outlets in Mississauga and Edmonton.

Circle No. 49 on Reader Service Card.

The Honourable Donald Johnston, Minister of State for Science and Technology and for Economic and Regional Development and Minister responsible for Space Policy (his friends call him 'Don') has announced a 38% increase in the Space Expenditure Plan to \$446 million over the next two years. Electronics manufacturers will no doubt profit from the budget increase.

for your information

The first equation processor ever developed for personal computers, TK!Solver[®], has been made more useful for architects, building designers and construction engineers. Software Arts, creator of the VisiCalc[®] and TK!Solver programs, is now offering a TK!SolverPack[™] for Building Design and Construction. For people who use equations, formulas and modeling for analysis, design and planning, TK!Solver is a tool that saves time and increases efficiency by solving equations automatically. The program features a unique backsolving capability, which allows users to solve for any variable in an equation without reformatting the problem. In addition, TK!Solver performs iterative and list solving, produces tables and graphs, contains an automatic unit conversion feature, and has 15 models for solving design problems in residential construction.



2.78 MB for Apple

Data Technology has announced an Apple-compatible disk drive using the new Kodak 2.78 megabyte drive. It uses special 5 1/4 inch floppy disks at about \$15-\$20 each; one of these replaces about 25 of the 126K Apple disks. The drive will also read standard floppies. It's available in single, dual, or single-plus-hard disk. The single drive lists at \$1,295 U.S. Contact Data Technology, 2775 Northwestern Parkway, Santa Clara, CA 95051 (408) 496-0434.

Circle No. 48 on Reader Service Card.

SPECIAL SALE

RX 6600
For
\$479.00



- 64K Ram
- Z80 (CP/M)
- Special Function Keys
- User's Defined Keys
- Apple II + compatible

DISK DRIVE
For **\$239.00**



- Apple II Compatible Shugart 390L
- Slim Line Teac \$249.00
- IBM Slim Line Double Side DD \$249.00


CARDS & PERIPHERALS

- Z80 \$49.00
- 16K Ram \$55.00
- Disk Controller \$45.00
- 80 Column \$69.00
- Light Pen \$199.00
- Joy Stick \$38.00
- 5 Amps Power Supply \$79.00

PRINTERS

- Mannesmannally Sprit 80 \$425.00
- TTX Daisy Wheel \$575.00

IBM MAIN BOARD
For **\$479.00**

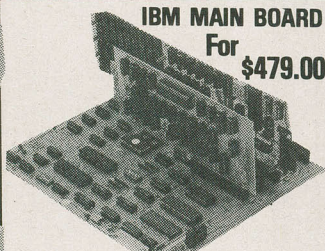

- IBM Compatible bare Board \$39.00
- Multi function card \$225.00
- IBM Compt. Case \$99.00
- IBM Compt. Power Supply 10 amps 100 watts \$119.00
- IBM Compt. Drive DSDD \$249.00

IBM PC COMPATIBLE
KEYBOARD
\$179.00



Enhance your IBM PC* Compatible Computer System with K150 Keyboard.

Use Cherry TS-M0001 switch with life time 20 million operations.


- *IBM is Trade Mark of International Business
- *Apple is a registered Trade Mark of Machines Apple Canada Inc.

ELECTRONIC CONTROL SYSTEMS

1890 Meyerside Drive, Mississauga, Ontario L5T 1B4
(416)673-1302 Hours — Mon. to Fri. 10-7, Sat. 10-2

Circle No. 21 on Reader Service Card

METER PROBLEMS?

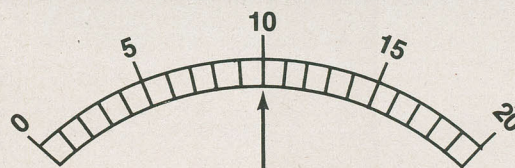

ANALOGUE OR DIGITAL
INSTRUMENTS
BY

TRADEPORT ELECTRONICS

WE SERVICE & SELL

ELECTRONIC & ELECTRICAL MEASURING INSTRUMENTS OF EVERY TYPE. DISTRIBUTOR/AGENTS FOR GRUNDIG - ITT METRIX - HITACHI - HAMEG - BLACKSTAR - CONWAY - MARCONI - PYE - SENCORE - HEATHKIT - MILLIVAC.

TRADEPORT ELECTRONICS

1179 Finch Ave. W. #11 Downsview, Ont. Canada M3J 2G1

MEASUREMENT IS OUR BUSINESS


Tel: (416) 736-0866

TLX 06-217828 TRDPRT TOR.

DEALER INQUIRIES INVITED

Circle No. 22 on Reader Service Card

for your information

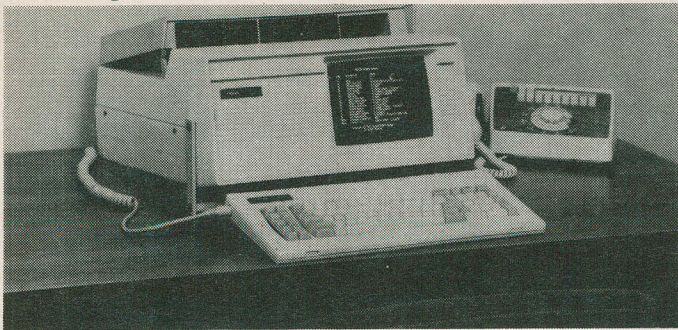

Heath Portable


The IBM-compatible Heath HS-161 Portable PC is available in single or dual 5.25-inch floppy disk drive configurations with each drive having a storage capacity of 360 kilobytes. Both versions are available in either kit form or fully assembled. All have 128 kilobytes of RAM memory that's expandable to 320 kilobytes on the main memory board and to 640

kilobytes by an added memory expansion board. All HS-161's have two RS-232C serial ports, one Centronics-compatible parallel port, color monitor output, four open IBM-compatible expansion slots and a built-in 9-inch amber monitor with an eight level "gray scale" feature. Contact: Heath Co., 1020 Islington Ave., Dept. 3100, Toronto, Ont. M8Z 5Z3.

Circle No. 47 on Reader Service Card.

Electrical Testing Instruments Ltd., announces a solid state dielectric strength tester. The Model HVA-2.5/100C is housed in a portable aluminum case and is used in production, acceptance, design and repair testing of all types of equipment requiring CSA, ASTM, NEMA, UL and IEEE testing standards. The features of this instrument are solid state transient free switching in zero crossing, breakdown and leakage indication, secondary metering of test voltage and positive manual reset on breakdown. The HVA-2.5/100C has been designed for use as a simple tool for dielectric strength, "HIPOT" or breakdown testing of all electrical or electronic equipment and appliances. Contact them at 3015 Kennedy Rd., Unit 12, Scarborough, Ont., M1V 1E7 (416) 292-8181.

Circle No. 45 on Reader Service Card.

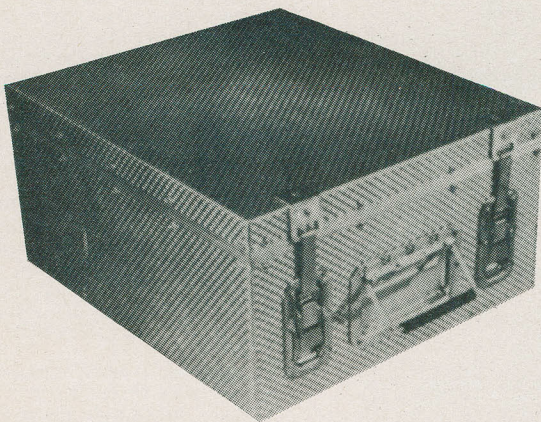

Custom Strongboxes


If you need protection for portable test gear, computers, cameras, musical instruments, etc., North American Strongbox will custom-build a shockproof, waterproof

aluminum box to suit your needs. Various shock-absorbing linings are chosen to optimise the required protection. Contact them at 43 Britain St., Toronto, Ont. M5A 1R7 (416) 364-8447.

Circle No. 44 on Reader Service Card.

HAMEG® Oscilloscopes

*For Field Service
and Laboratory*

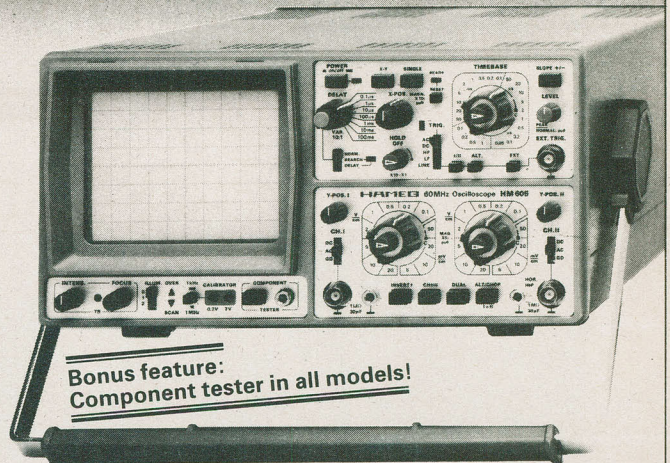

**Bonus feature:
Component tester in all models!**

HM 605 60 MHz Dual Trace - \$1550,-

Sensitivity 5mV-20V/div at 60 MHz, 1mV at 15 MHz • Automatic peak-value or normal triggering to 80 MHz • Delay line • Variable sweep delay from 100ns-1s • Timebase range from 2.5s/div to max. 5ns/div • Unique fast-rise-time 1kHz/1MHz calibrator • Bright high-resolution 14kV CRT.

HM 204 20 MHz Dual Trace - \$1120,-

Sensitivity 2mV-20V/div • Timebase range 2s/div-20ns/div • Automatic peak-value triggering to 50 MHz • Variable sweep delay • Single sweep mode • Y-Output • Z-modulation • Over-scan indicator.

HM 203 20 MHz Dual Trace - \$835,-


Western Europe's best selling 20MHz-Scope! • Sensitivity 2mV-20V/div • Triggerbandwidth 40MHz • Timebase range 0.2s - max. 40ns/div

HM 103 10 MHz Single Trace - \$550,-

Small, compact service scope • Sensitivity 2mV-20V/div • Timebase range 0.2µs-0.2s/div • TV-V and TV-H triggering.

»Modular System« HM 8000

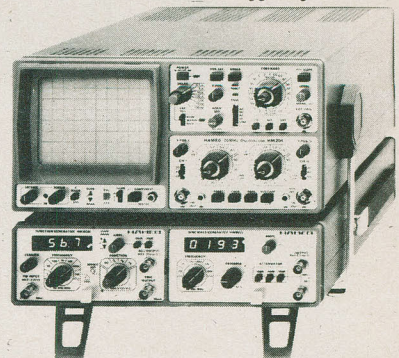An expanding range of signal generators, multimeters, counter/timers, etc. ...




**For more details
write or call collect:**

BCS
ELECTRONICS
LIMITED

980 Alness St. Unit 7,
Downsview, Ontario.
M3J 2S2
(416) 661-5585
TELEX 065-28169


for your information

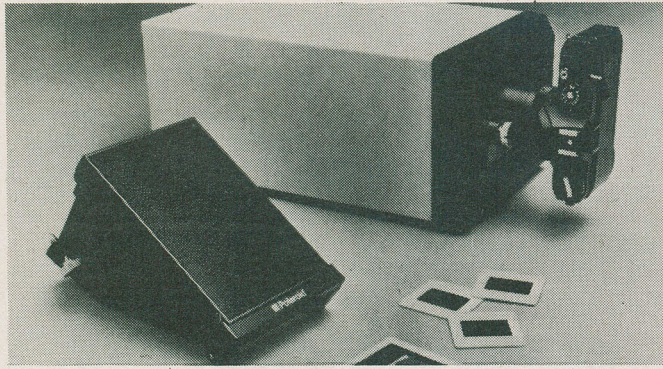

Screen Photos

Systems for producing presentation-quality instant color photographic hard copy have been announced by Polaroid Canada Inc. The hard copy system features a recorder for personal and small business computers. Called the Palette computer image recorder, the new system makes Polaroid 35mm Autoprocess color slides and 3 1/4 x 4 1/4-inch instant color prints of color or black and white computer graphics. Contact: Communications Dept., 350 Carlingview Dr., Rexdale, Ontario (416) 675-3680.

Circle No. 43 on Reader Service Card.

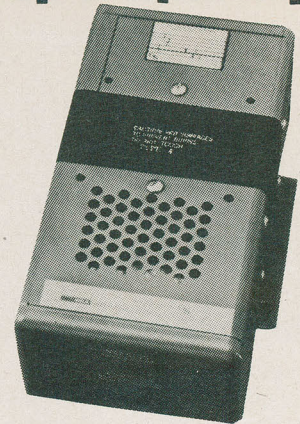

Computer Regulator

For sensitive electronic equipment requiring single-phase, 208 V output, an expanded line of hardwired Micro/Minicomputer Regulators featuring a new 208 V output in addition to standard 120-240 V outputs, is now available from Sola Electric, a unit of General Signal. For use primarily with mid-size computer installations, the new Micro/Mini models are available in 60 Hz designs rated for 500 VA to 15000 VA loads. Among these, 7.5 kVA, 10 kVA and 15 kVA Micro/Mini units will also accept 208 V input. Contact Sola Electric, 377 Evans Ave., Etobicoke, Ontario (416)255-6465.

Circle No. 42 on Reader Service Card.

The new Gladstone Electronics Spring/Summer catalogue is obtainable free of charge from 1736 Avenue Road, Toronto, Ont. M5M 3Y7 (416) 787-1448. It includes CB, a new Sinclair computer, robot kits, software, hardware, etc.

Circle No. 41 on Reader Service Card.

High speed MOSFETS

A new family of small signal Mosfets is now available from Ferranti Semiconductors. This ZVN33 transistor series has been designed with extremely compact geometry to permit switching times under 10 nanoseconds. As a result, these devices are ideally suited to applications such as telecommunication switching circuits and other designs requiring superfast switching. Noted specifications are breakdown voltages — 20 to 200V, low thresholds (VGSth) — 2.4V max, and input capacitances as low as 35pf. Available in the hi-rel E-Line (TO-92) and TO-39 packages, the ZVN33 Mosfets are priced at 30¢ each in 1K quantities. Leadtime is 4-6 weeks. For additional information, contact Ferranti Semiconductors, 87 Modular Avenue, Commack, NY 11725; (516) 543-6200.

Circle No. 40 on Reader Service Card.

Looking for a wide range of indicator lights, LEDs, and so forth? Len Finkler and Co., 80 Alexdon Rd., Downsview, Ont. M3J 2B4 offer their comprehensive 44-page technical guide and catalogue, "The Source for Indicator Lights."

Circle No. 39 on Reader Service Card.



The One Stop Shop For All Your Electronic Needs!

Conveniently located across Canada

Montréal
5651 Rue Ferrier
Montréal, Québec
H4P 1N1
(514) 731-7441

Ottawa
1023 Merivale Road
Ottawa, Ontario
K1Z 6A6
(613) 728-7900

Toronto
14 Carlton Street
Toronto, Ontario
M5B 1K5
(416) 977-7692

Calgary
3220-5th Ave. N.E.
Bay 2
Calgary, Alberta
T2A 5N1
(403) 235-5300

Downsview
86 St. Regis Cr. N.
Downsview, Ontario
M3J 1Y8
(416) 630-0400

Vancouver
3070 Kingsway
Vancouver, B.C.
V5R 5J7
(604) 438-3321

* Mail Orders to Montreal Address.

Visit your nearest Active store, call, write or circle the Reader Service Card for your copy of Active's new catalog.


Circle No. 4 on Reader Service Card

QCAL[®]

International

Peripherals for your IBM PC

- Colour Video Board \$339.00
- Floppy Controller Board \$299.00
- 128K Memory Expansion Board \$399.00
- w/2 Serial & Parallel Port
- LASER Disk Drive \$349.00
- (Teac FD55B Mechanism)
- IBM Compatible Keyboard \$189.00

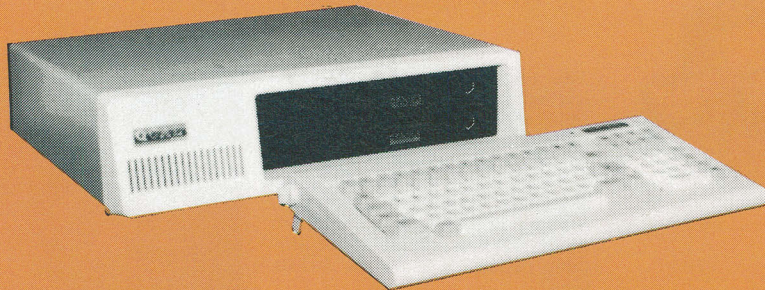

QCAL 8000

IBM PC-WORK-ALIKE

- 8088 Processor
- 128K RAM
- Detachable Keyboard
- One LASER Disk Drive (DSDD)
- w/Teac 55B Mechanism
- Disk Drive Controller
- Colour Video Board
- Heavy-Duty Power Supply
- w/Built-in Cooling Fan
- Five Expansion Slots

\$2295.00

(Does NOT include software or monitor) This is NOT a kit




*LASER HARD DRIVE

10 Mbytes 5-1/4" Winchester Hard Drive with Controller, Cable and Diskette for IBM PC

\$1,699

for Apple (with Power Supply and Case)

\$1,999

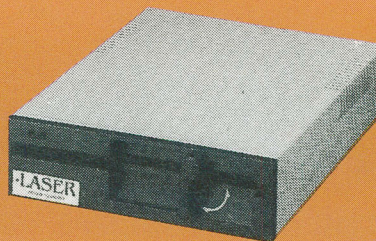

*LASER SLIM LINE

Teac FD55B Mechanism for IBM and IBM Compatibles. Access time 6 MSEC Storage capacity 40 Tracks 328 Kbytes

\$299.00

LASER Slimline for Apple and Apple Compatibles

\$279.00

Storage capacity 40 Tracks 163 Kbytes Access time 6 MSEC Controller \$55.00 with purchase of Disk Drive



*LASER \$269.00 FULL HEIGHT

Shugart SA-390 Mechanism for Apple and Apple Compatibles Access time 14 MSEC Storage capacity 40 Tracks 163 Kbytes Controller \$55.00 with purchase of Disk Drive

Call us about Disk Drives for Commodore

All QCAL, Laser and Mastone products are distributed exclusively in Canada by

PACIFIC RIM ELECTRONIC IMPORTS INC.

P.O. Box 7050, Station M, Edmonton, Alberta T5E 5S9 CANADA

Dealer Inquiries Call (403) 475-0855 or Telex 037-41683 PACIFICRIM

Write or call for QCAL Dealer nearest you

WRITE OR CALL TODAY FOR SUMMER DISCOUNT MAIL ORDER CATALOGUE

Apple, IBM (IBM PC) and LASER are registered trademarks of Apple Computer Inc., IBM Corp. and Laser Micro-systems Inc. respectively

Circle No. 30 on Reader Service Card

Series 600 Preamplifiers

According to Precision Filters Inc., their Series 600 high input impedance, differential preamplifiers feature "excellent" low noise and common mode rejection performance over a frequency response range of 0.5 Hz to 500 kHz. These preamplifiers are available in single-ended and differential versions. Standard fixed gains of 0, 10, 20, 30 and 40 dB or switched gains are available; gain deviation with power supply and temperature changes is typically 0.002 dB per volt or per °C respectively.



The Series 600 provides full output of ± 10 volts peak to 100 kHz. Full output response is main-

tained at up to ± 15 mA load current, with total freedom from peaking effects with complex loads.

The differential version can operate from ± 9 V DC to ± 18 V DC power supplies. Single supply versions, positive and negative, are available for supply range of 18 V DC to 36 V DC. Power supply noise rejection is excellent, greater than 80 dB over the entire frequency response range.

For more information, contact Precision Filters Inc., Dept. 600, 640 Cherry Street, Ithaca, NY 14850, (607) 277-3350, Telex 646846.

Circle No. 38 on Reader Service Card.

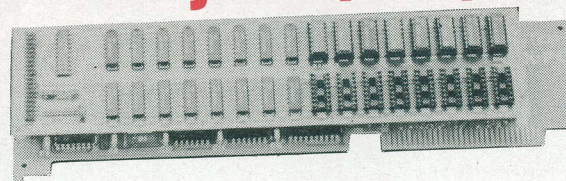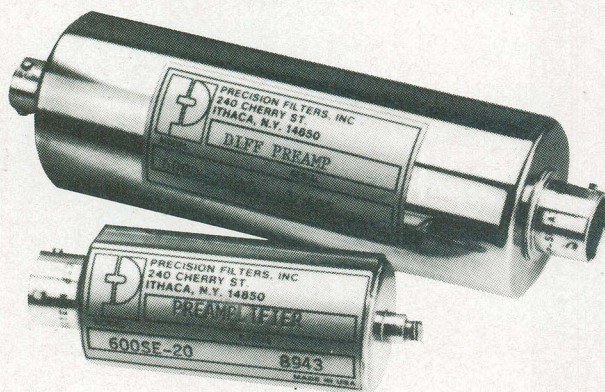


Epsom MS-DOS

A new plug-in board that allows the 8-bit Epsom QX-10 Personal Business Computer to run 16-bit MS-DOS™ and PC-DOS software is now available. Titled the QX-PC™, this board was developed and manufactured by Titan Technologies of Ann Arbor, Michigan. The QX-PC™ board converts the Z-80 based QX-10 to MS-DOS compatible 16-bit operation. Users can conveniently have access to CP/M™, MS-DOS and Valdcos software all on this same machine. The QX-PC operates at 5 MHz,

supporting the graphics, printer and serial port features of the QX-10, making them accessible from MS-DOS. The optional board is available with 192K or 256K bytes of memory. It can be populated to 512K bytes with a separate option card. The 192K version is immediately available through a national network of authorized ZX-10 dealers, with a suggested list price of \$1129. Contact Epsom Canada Ltd., 21 Progress Court, Unit 18, Scarborough, Ont., M1G 3V4 (416) 431-5588.

Circle No. 37 on Reader Service Card.

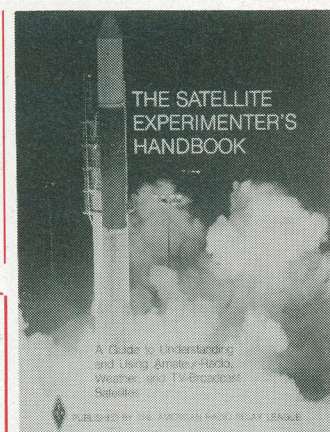This summer, NovAtel Communications of Calgary will begin field trials of Canada's first 800 MHz cellular communications network. A mobile test vehicle will be used to verify system parameters in the seven-cell Calgary test network. Success of the project will no doubt mean the possibility of portable phones in every car before long.



Satellite Book

The American Radio Relay League announces their Satellite Experimenter's Handbook, a collection of information on how to receive and use broadcasts from satellites; these broadcasts include amateur radio, weather, TV, etc. Chapters include orbits, tracking, antennas, and more. Contact: ARRL, 225 Main St., Newington, Connecticut 06111 (203) 666-1541.

Circle No. 36 on Reader Service Card.

The International Maritime Satellite Organization (INMARSAT) has sent letters to the bidders for its new series of satellites, inquiring as to the feasibility of the new satellites carrying 406 MHz transponders, which would be used for relaying distress alerts from satellite radio beacons. The 406 MHz transponder is also being carried on the satellites used in the COSPAS/SARSAT system, a search and rescue system developed by Canada, the United States, France and the Soviet Union, all of which are INMARSAT member countries. The COSPAS/SARSAT satellites have been credited as being instrumental in the saving of more than 180 lives, since the first satellite, a Soviet Cosmos satellite, was launched in June 1982.

PROBES FOR SALE

FROM THE BEST SOURCE FOR OSCILLOSCOPE PROBES AND DMM/VOM TEST LEAD SETS.



- Low cost
- High Quality
- Excellent Performance
- Slender, Flexible Cable

- Wide Range of Choice
- Switchable X1 and X10 Attenuation Factor
- 100 MHz Bandwidth

MODEL SP100
\$50¹⁰

Your Probe Specialists

Coline Canadian Sales & Stocking Source



980 Alness St. Unit 7,
Downsview, Ontario,
M3J 2S2
(416) 661-5585
TELEX 065-28109

Circle No. 2 on Reader Service Card

WINNER: Ultra-modern! Super-efficient! Fully Apple Compatible \$995.00




Please note the distinct features
Winner offers:

- *Dual microprocessors 6502 & Z-80A
- *RS-232 built in
- *Disk drive interface card built in
- *40/80 column text display and auto change video output port by soft switch
- *76K RAM with 4 expansion slots

- *16K ROM
- *DOS 3.2 & DOS 3.3 capability
- *Apple & CP/M compatible
- *ASCII keyboard with function keys and a numeric keypad
- *Upper/lower case
- *Streamline case
- *OS could be changed when desired without affecting other memory RAM


CP80 DOT MATRIX PRINTER

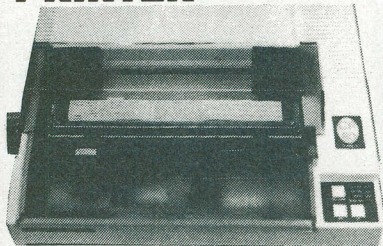

7X8 DOT MATRIX
80 CPS, 640 dots/line per second
Bidirectional
80 Column normal
142 Compressed
Friction & Tractor Feed
Standard Centronics Parallel
Same as EPSON 80

\$495.00

TTX™ 1014

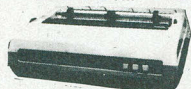

RELIABLE DAISY
WHEEL RO PRINTER

\$595.00

1014 FEATURES

- SERIAL AND PARALLEL INTERFACE
- WORDSTAR® COMPATIBLE
- QUIET OPERATION
- PROGRAMMABLE PITCH AND LINE SPACING
- COMPACT AND DURABLE
- MICRO, MINI, MAINFRAME COMPATIBLE
- INTEGRAL PIN FEED GUIDE (ADJUSTABLE)
- RIBBON CARTRIDGES AND PRINT-WHEELS READILY AVAILABLE.

SEE OR CALL ABOUT OUR EXTENSIVE LINE OF PRINTERS.

All above Systems with New IBM™ Styling 100.00 extra



- Detachable Keyboard
- Programmable Function Keys
- Built in Key Words for Apple™ Soft, DOS
- Room for two Slim Line Drives

**IBM™
STYLING**

Mini Modem \$99.45

Parts

DB-25P Connector	\$ 4.95
DB-25S Connector	\$ 5.95
Covers for 25's	\$ 2.25
DB-9P	\$ 3.95
DB-9S	\$ 4.95
Covers for 9's	\$ 1.98
2716 EPROMS	\$ 6.95
2764 EPROMS	\$14.95
4164 RAMS 200 N/S	\$ 9.75
4116 RAMS 200 N/S	\$ 1.75
2016 RAMS	\$ 9.75
EPROM ERASERS P.E. 14	
8 at a time	\$129.95


Disk Holders

Disk Bank (50 Disks)	\$39.95
DX 85 (55 Disks)	\$39.95
Data Defender (70 Disks)	\$39.95
Flip "N" File 10	\$ 8.95
Flip "N" File 15	\$13.95
Flip "N" File 25	\$34.95
Flip "N" File 50	\$44.95
Flip "N" File Original 50	\$29.95

Diskettes

Xidex SS/DD	\$29.95
Xidex (Plain Box) SS/DD	\$24.95
Xidex DS/DD	\$39.95
3M Diskette SS/DD	\$29.95
Verbatim (DataLife) SS/DD	\$34.95
Maxell MD 1-DS/DD	\$34.95
Maxell MD 2-DD/DD	\$49.95
Dysan SS/SD 104-1	\$29.95
Dysan SS/DD 104-2	\$34.95
Dysan DS/DD 204-2	\$49.95
Disk Cleaning Kit Recoton	\$34.95

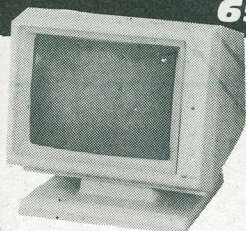6502 BOARDS & ACCESSORIES Timex Sinclair 1000



**Swivell
Monitor
Amber
GM 1211 \$165.00**

More Monitors


Roland CB 141 Colour	\$395.95
Amdek Colour	\$395.95
GM 1201 Green 12"	\$149.95
GM 1201 Amber 12"	\$159.95
Zenith Green 12"	\$139.95
Zenith Amber 12"	\$149.95

More Available

Orion Electronic Supplies Inc.

40 Lancaster Street West
Kitchener, Ontario N2H 4S9
(519) 576-9902

ABB-1 \$45.00 APPLE II Compatible, Dual CPU Bare Board Comm Card \$99.00 Serial interface RS232C Card for APPLE II c/w Cable & Manual.	AKB-2 \$99.00 Keyboard: Numeric Keypad with Function Keys, replacement for APPLE II.
AC-1 \$89.00 Integer Card	AC-2 \$89.00 Beige APPLE II Case (for above Keyboard) Case & Keyboard Numeric \$175.00
AEC-1 \$89.00 80 Column Card	APS-2 \$99.00 Switching Power Supply for APPLE II; + 5V 5 amps. + 12V @33 amps. 5V @ 1/2 amp. 12V @ 1/2 amps; c/w on-off switch & connecting wires
AZC-1 \$79.00 Z80A (CPM) Card	AAA-2 \$99.00 Dis Drives 5 1/4" APPLE II Compatible, Excluding Controller Card \$299.00 With Controller \$365.00
APC-1 \$89.00 Parallel Printer Card	ADC-1 \$89.00 Disc Drive Controller Card for two drives; Apple II Compatible
ASC-1 \$89.00 Serial Printer Card	APPLE II is a registered trade mark of Apple Com- puter Inc.
ALC-1 \$69.00 16K RAM (Language Card Speech Card \$75.00 Wild Card \$89.00 Modem Card \$175.00 (Networker)	
40 Column Switch \$9.95 Colour RF Modulator Set \$25.00	

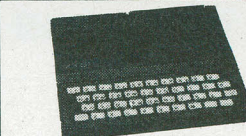

**Assembled
\$39.95**

**ZX81 Printer
\$99.00**

16K Sinclair Memory \$35.00 Books Hardware

COMPLETE ZX81 BASIC COURSE - Inc. 2 tapes	39.95
NOT ONLY 30 PROGRAMS: 1K	16.95
MACHINE LANGUAGE MADE SIMPLE	19.95
ZX81 ROM DISASSEMBLY PART A & PART B	24.95
UNDERSTANDING ZX81 ROM	19.95
TIS 1000: PROGRAMS, GAMES and GRAPHICS	16.95
LEARNING TIS BASIC	23.95
THE BASIC HANDBOOK	29.95
48 EXPLODING GAMES	16.95
COMPUTER FOR KITS SINCLAIR EDITION	9.95
MASTERING MACHINE CODE ON YOUR ZX81	24.95
TIS 1000 USERS GUIDE (Vol 1)	16.95
EXPLORERS GUIDE TO THE ZX81	16.95
ZX81 POCKET BOOK	16.95
GETAWAY GUIDE	16.95
GETTING ACQUAINTED WITH YOUR ZX81	16.95

Sinclair Printers	99.00
Timex Printer	125.00
64K RAM (Memotech)	149.00
32K RAM (Memotech)	79.00
16K RAM (Sinclair)	35.00
Memotech 16K RAM	39.95
500MA	8.95
Memopak Centronics Type	
Parallel Printer Interface	119.00
Memopak ZX81 Keyboard	119.00

**Additional Hardware & Software
for the SINCLAIR ZX81
AVAILABLE ON REQUEST.**

Master Charge & Visa, COD, Cheque,
Money Orders accepted. COD's, ship-
ping & insurance extra. Write for our
FREE FLYER.

Prices subject to change without
notice.

EXCELTRONIX (416) 921-8941

Bulletin Bd. (416) 624-5574 Telex 065-24218

319 College St., (416) 293-1796 Toronto, Ont. M5T 1S2

Toll-Free Number:

1-800-268-3798

The "BEST"

IBM Compatible Microcomputer

See the Review
in March 1984
Computing Now!

\$1995

Not a kit — a complete system

This price includes:

- 64K of RAM with pre-socketed provision for 256K
- One disk drive. SA455. Double Sided. Double Density
- Colour Video Board
- Floppy controller capable of handling up to four DS. DD 5 1/4" disk drives and real time clock
- Monitor not included

Warranty:
Full 120 day
Warranty

Prices does NOT include
IBM (Microsoft) BASIC



OR The Loaded "BEST"

Everything in our \$1995 System plus:

- Two DS. DD 5 1/4" Disk Drives
- On-board 256K of RAM
- RS232 Port

\$2595

OR 10 Meg Hard Disk Version

Everything in our \$1995 system plus:

- 10 Meg Hard Disk Drive & Controller
- On-board 256K of RAM
- RS232 Port

\$3995

SOFTWARE FOR YOUR IBM

- Lotus 1, 2, 3\$439
- Wordstar\$399
- Multiplan\$219
- dBASE II\$479
- Flight Simulator\$62.95

Great Selection of other software for your IBM available.

IBM is a Trade Mark of IBM Canada Limited

Mail Order: Call for shipping costs. Rate will depend on methods chosen and distance.

Call our TOLL-FREE number for more information.
1-800 268-3798

(Toronto area call 921-8941)

Call in and let us demonstrate the "BEST" to you at
319 College Street, Toronto. Store hours 9:30 to 6:00
Monday-Saturday: to 9:00 p.m. Friday.

PERIPHERALS FOR YOUR IBM

- Color Video Board\$299
- Floppy Controller Board\$299

Has provision optional RS232 port and real time clock.

- Parallel and Game Port Card\$149

Will also drive parallel printer

- 256K Memory Expansion Card and real time clock. Allows you to add a further 256K to your IBM's existing 256K capacity for 1/2 Megabyte of total memory.

- With 64K RAM on board\$289
- With 128K RAM on board\$369
- With full 256K RAM on board\$530

- EPROM Programmer\$149
- For 2716, 2732, 2764 and 27128.

- Disk Drive - SA455\$299
- IBM Compatible Case\$ 99
- IBM Compatible Keyboard\$189
- Super Heavy Duty Power Supply\$ 69

See our other ads for monitors, printers etc.,